



**Faculty Of Engineering and Technology**

**Electrical and Computer Engineering Department**

**CIRCUITS AND ELECTRONICS LABORATORY**

**ENEE 2103**

**Experiment #: 7**

**BJT Transistor As An Amplifier, CE, CC, CB Connection**

**Prepared by:** Rahaf Naser 1201319

**Instructor:** Dr. Mahran Quraan

**Teacher assistant:** Eng. Rafah Rahhal

**Date:** 8/15/2023

## **Table of contents**

1.COMMON EMITTER TRANSISTOR AMPLIFIER.....	1
2.COMMON COLLECTOR TRANSISTOR AMPLIFIER.....	5

## Table of Figures

Figure 1.1: Common-Emitter transistor amplifier.....	1
Figure 1.2: Common-Emitter transistor simulation.....	1
Figure 1.3: $V_o$ when $V_i=1v$ .....	2
Figure 1.4: $V_o=4v$ .....	3
Figure 1.5: $V_B$ and $V_o$ RMS.....	3
Figure 1.6: after remove the 100k resistor.....	4
Figure 2.1: Common-Collector transistor amplifier.....	5
Figure 2.2: Common-Collector transistor simulation.....	5
Figure 2.3: $V_o=2.04v$ .....	6
Figure 2.4: Input/Output Current.....	7
Figure 2.5: Common-Collector transistor simulation to find $Z_o$ .....	8
Figure 2.6: Output Voltage and Current.....	8

## **Table of Tables**

Table 1: Voltage and Current values.....	2
Table 2: Voltage and Current values.....	6
Table 3: Conclusion values.....	9

## 1.COMMON EMITTER TRANSISTOR AMPLIFIER

I connected the circuit in figure1.1, and set  $V_i(t)$  amplitude to 0, and set the potentiometer value to 10 k and its set value to 0. I set sinusoidal source to 1 kHz and amplitude to zero.

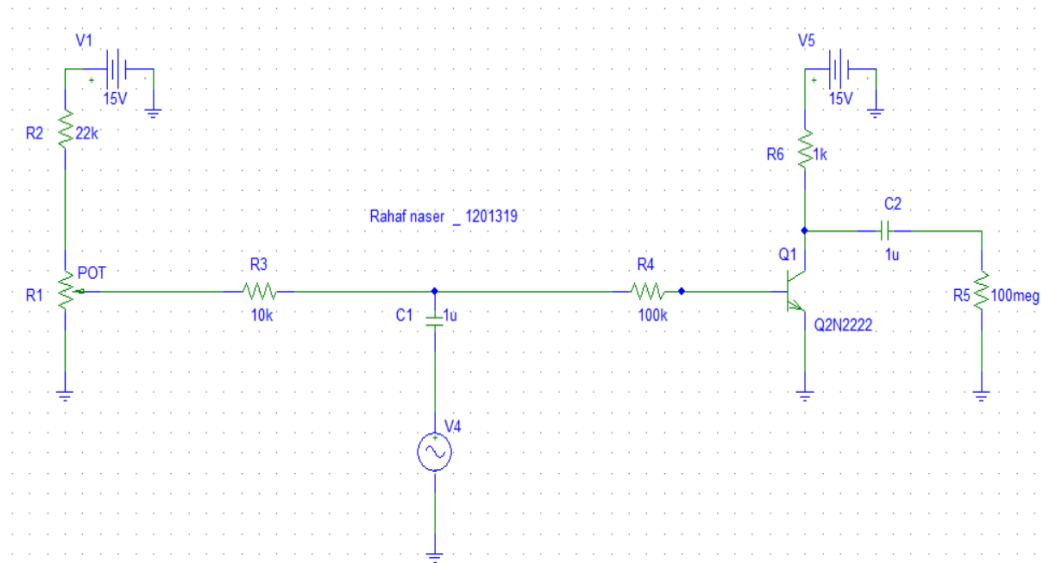


Figure 1.1: Common-Emitter transistor amplifier

Result of simulation

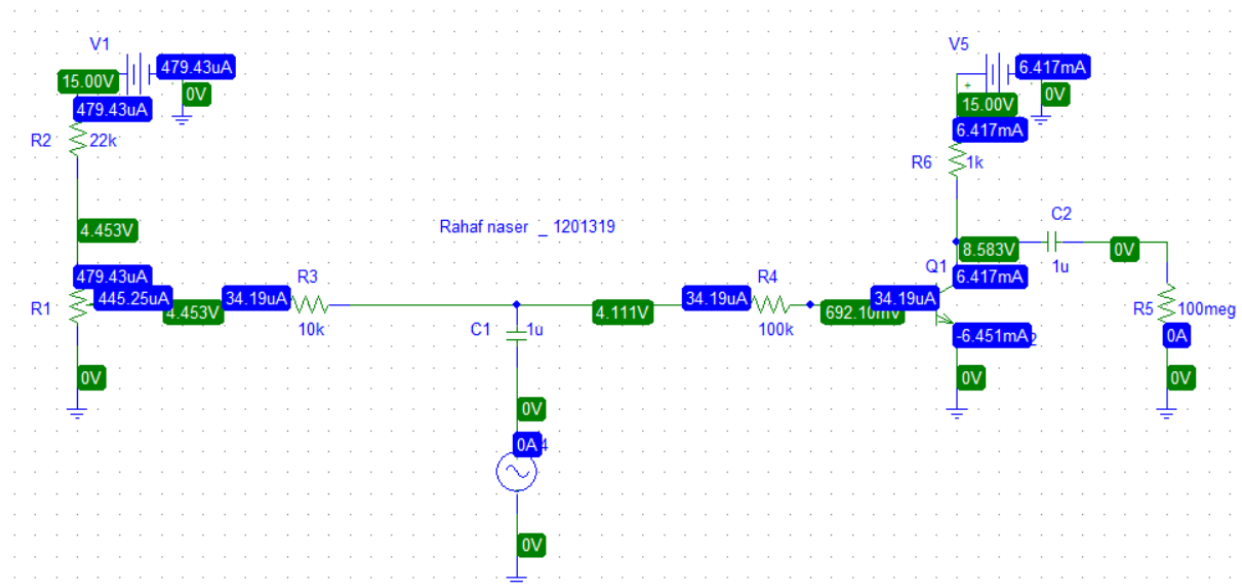


Figure 1.2: Common-Emitter transistor simulation

Measured values from figure 1.2 above:

V <sub>c</sub>	8.583v
V <sub>be</sub>	692.1mA
V <sub>ce</sub>	8.583v
I <sub>c</sub>	6.417mA
I <sub>b</sub>	34.19uA

Table 1: Voltage and Current values

Then I adjust amplitude of  $V_i(t)$  to 1 V and measured  $V_o(t)$ .

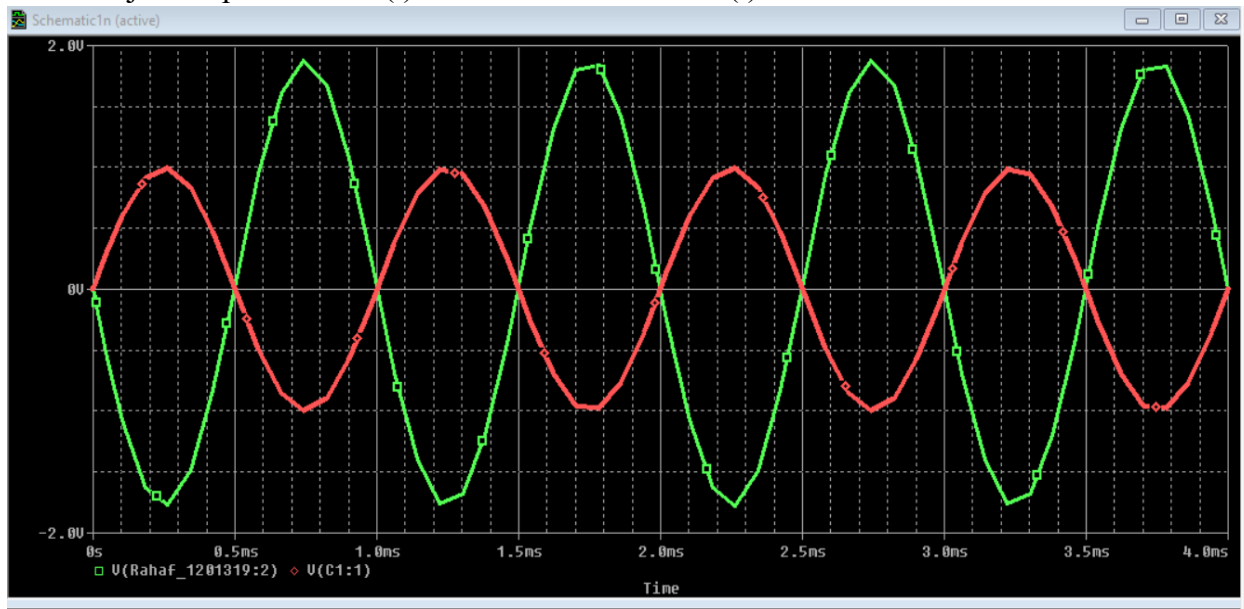


Figure 1.3:  $V_o$  when  $V_i=1v$

From figure 1.3 above :

$$V_o = 1.9v, A_v = 1.9/1 = 1.9$$

After change peak of  $V_i(t)$  such that  $V_o(t) = 4V$  peak and perform Transient analysis

$$V_{in} = 4/1.9 = 2.105v$$

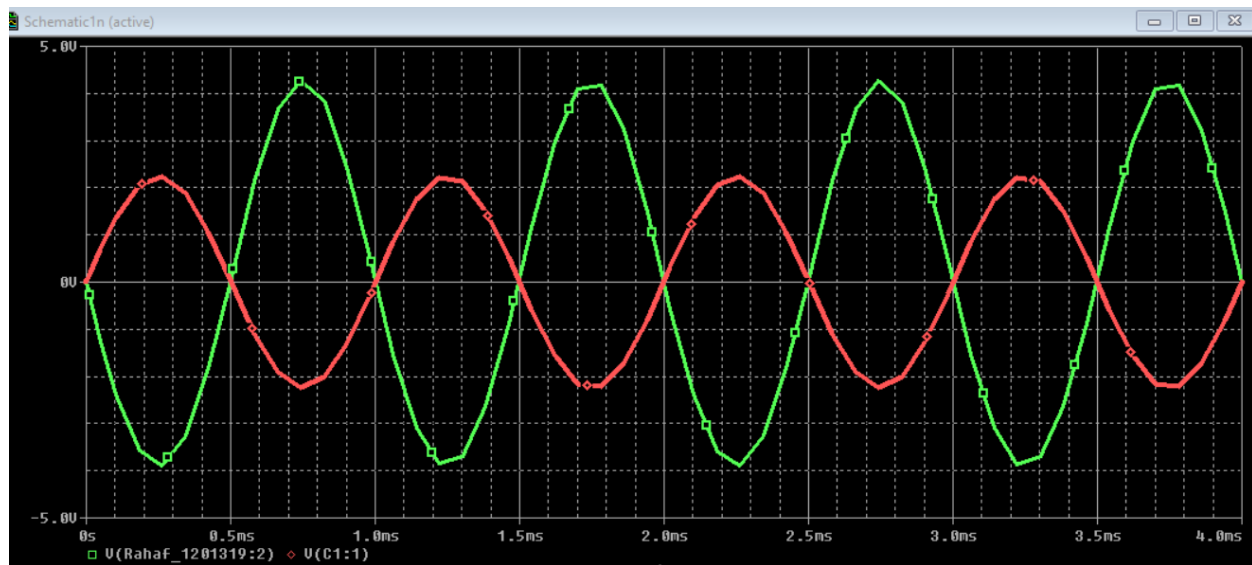


Figure 1.4:  $V_o=4v$

$$A_v = V_o/V_{in} = 4/2.105=1.9$$

To calculate  $A_{v1} = V_b / V_{in}$ , I used RMS waves:

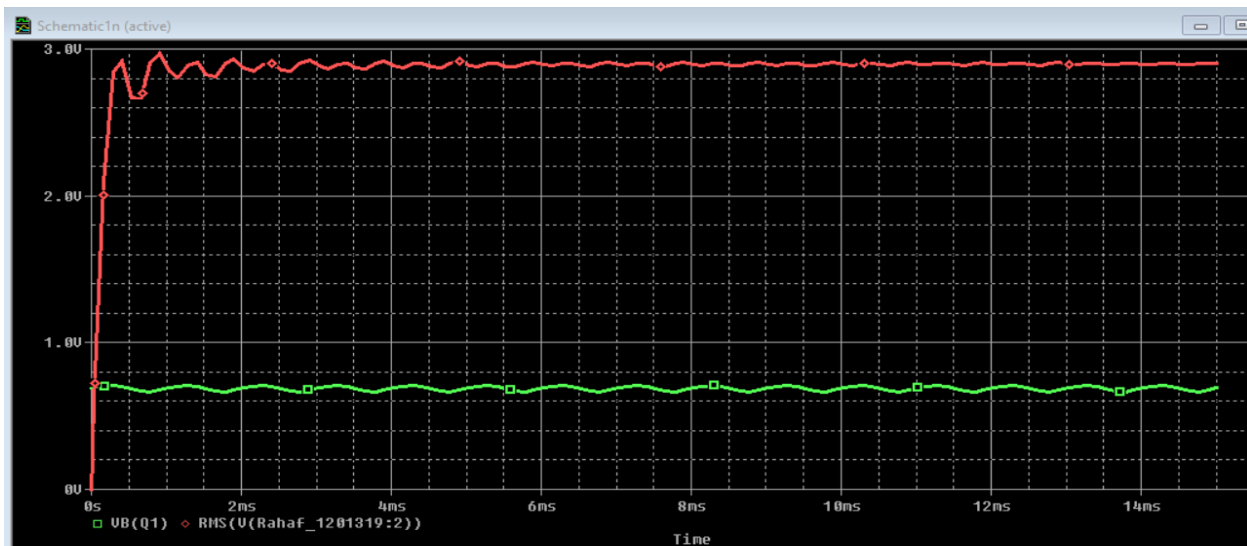


Figure 1.5:  $V_b$  and  $V_o$  RMS

From figure 1.5:

$$A_{v1} = V_o / V_b = 4 / 0.7 = 5.7$$

After remove the 100k resistor to see what happens to voltage gain

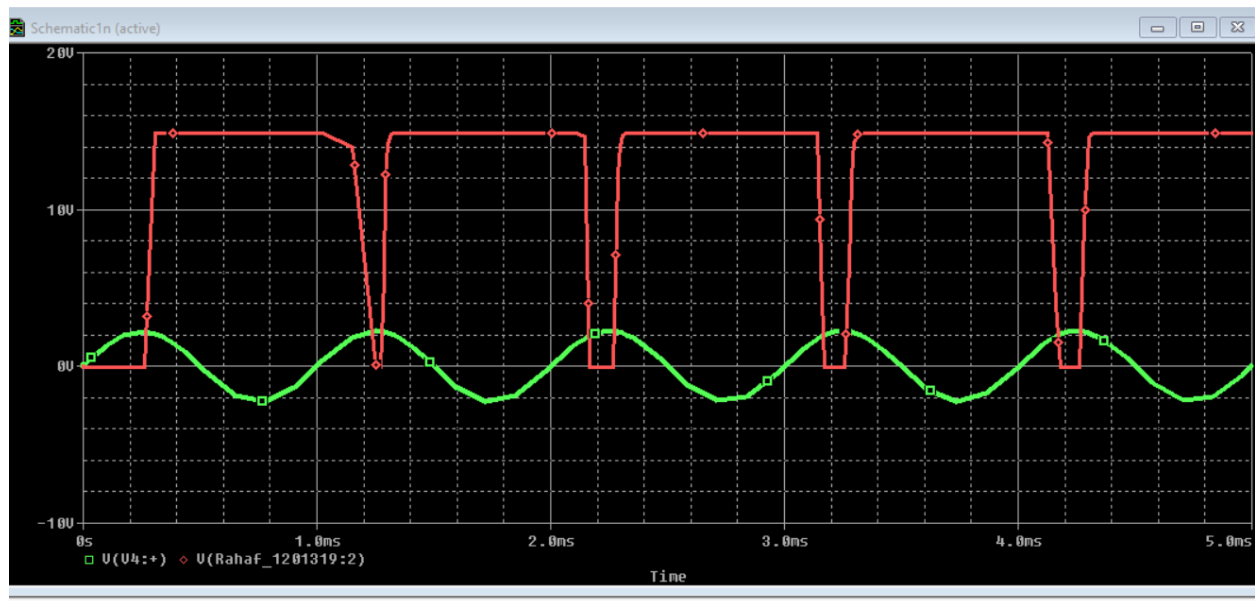


Figure 1.6: after remove the 100k resistor

We can see from the figure that the voltage gain will increase :

$$A_v = 15/2.2 = 6.8$$



## 2.COMMON COLLECTOR TRANSISTOR AMPLIFIER

I connected the circuit in figure 2.1. Set the sine wave generator to a frequency of 1 kHz, and its output amplitude to zero.

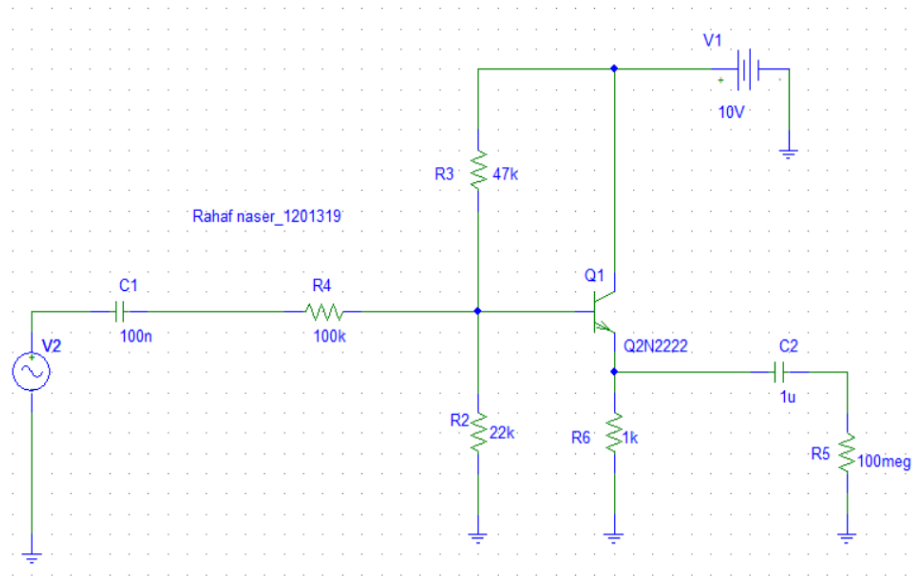


Figure 2.1: Common-Collector transistor amplifier

Simulation result->

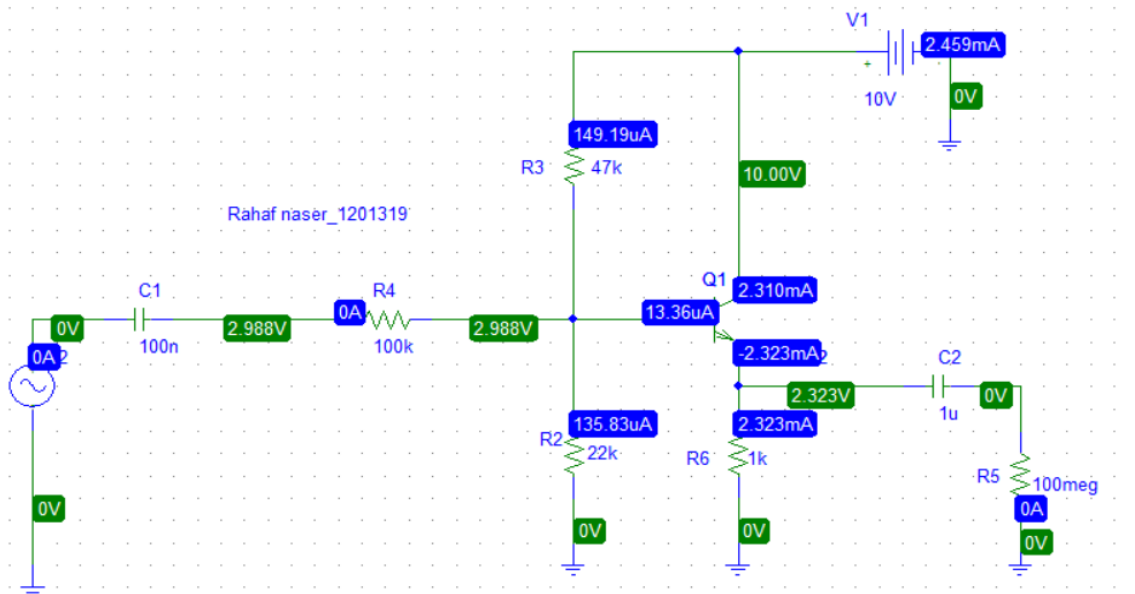


Figure 2.2: Common-Collector transistor simulation

Measured values from figure 2.2 above:

Vb	2.988v
Vc	10v
Ib	13.36uA
Ic	2.323mA

Table 2: Voltage and Current values

To get output amplitude from the amplifier is about 2volts peak-to-peak:

Vin amplitude =16.6v

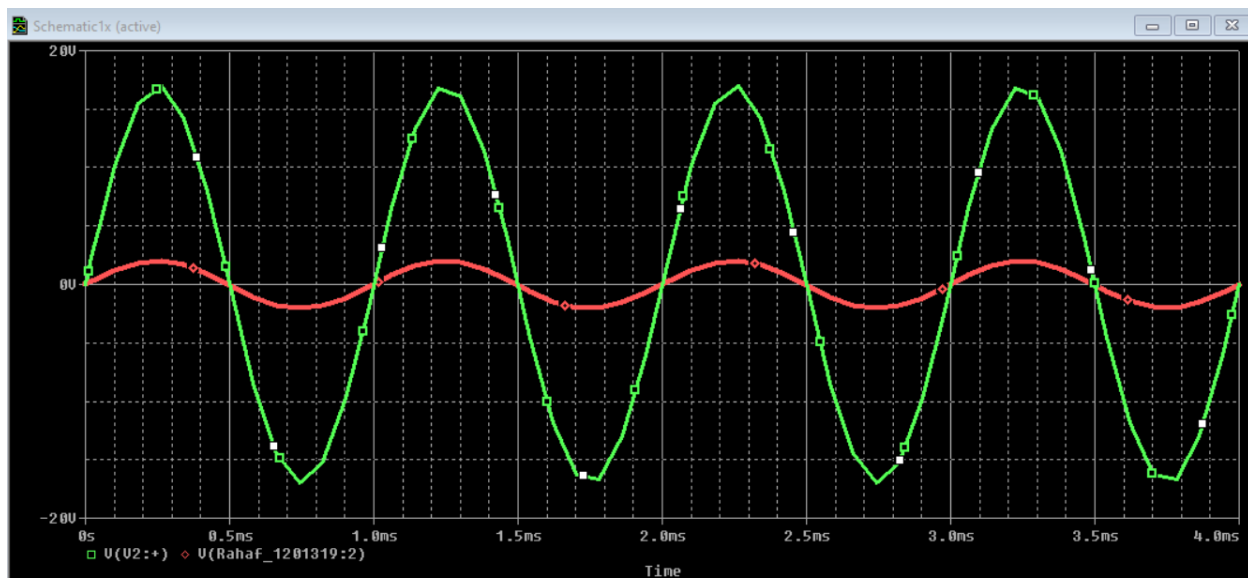


Figure 2.3: Vo=2.04v

$$A_v = 2.04/16.6 = 0.12$$

To calculate  $A_i = I_o / I_{in}$  and  $Z_i$  from figure 2.4 below:

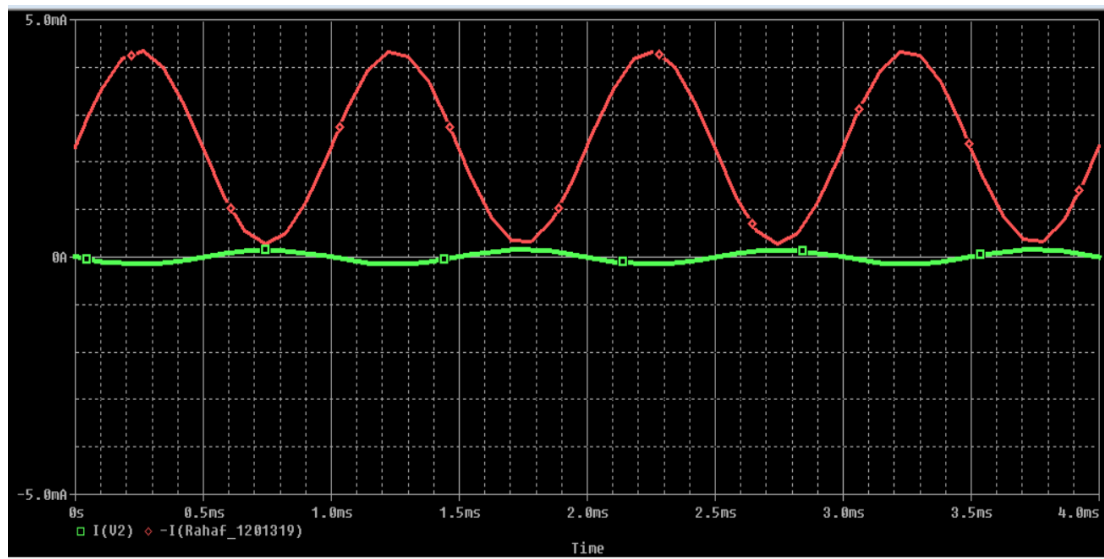


Figure 2.4: Input/Output Current

$$A_i = I_o / I_{in} = 2.03 / 0.15 = 13.53$$

$$Z_i = V_{in} / I_{in} = 16.6 / 0.15 = 110.66 \text{ kohm}$$

Now To find  $Z_o$ , I take off the input sine wave generator and replace it with a short circuit, then I connect the generator to the output (emitter) via a capacitor, and measure its output voltage and current, as shown in figure 2.5 below.

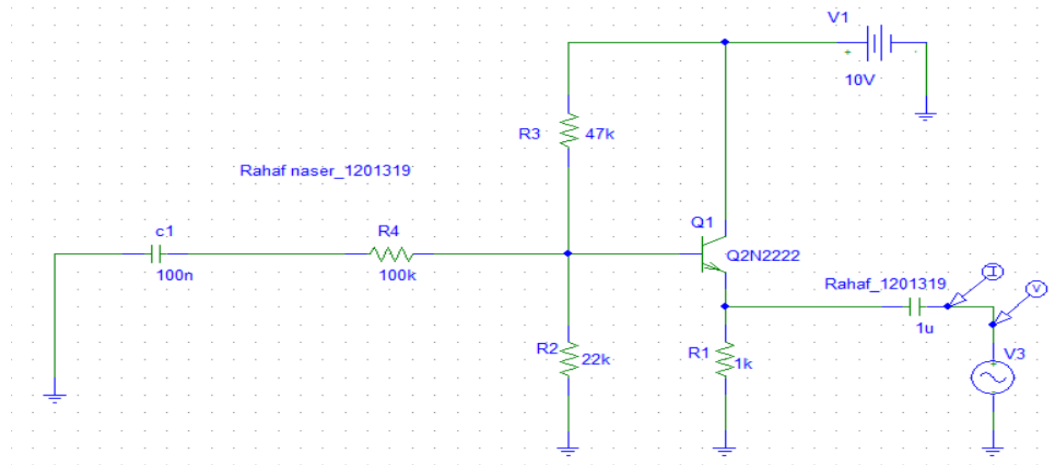


Figure 2.5: Common-Collector transistor simulation to find  $Z_o$

Simulation result->

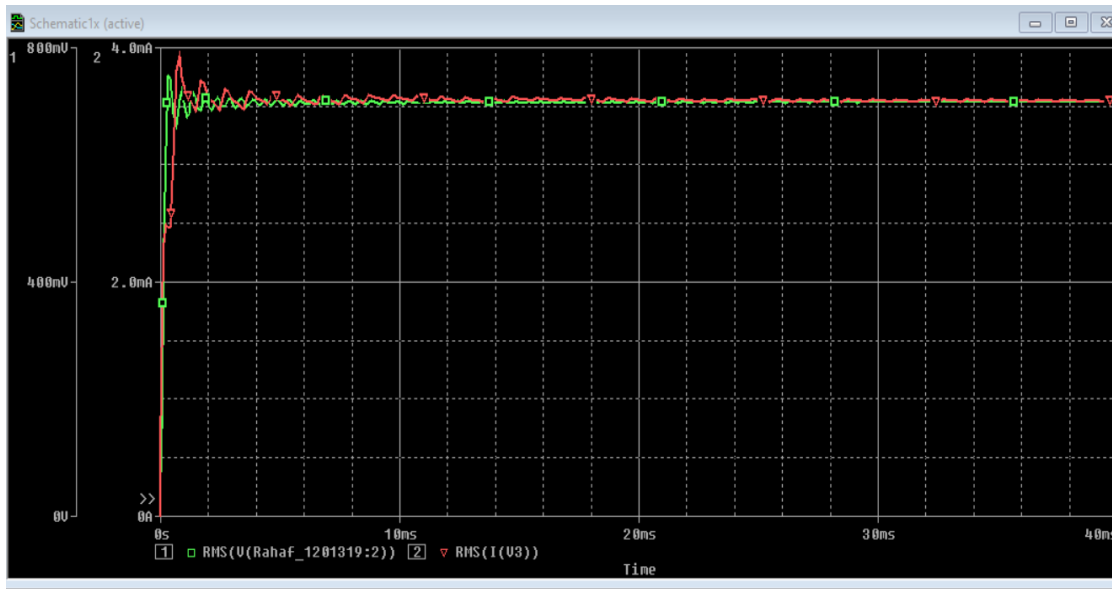


Figure 2.6: Output Voltage and Current

From figure 2.6 above:  $Z_o = V_o / I_o = 708 / 3.5 = 212.3 \text{ Ohm}$

Conclusion values:

Quantity	Measured value
V <sub>in</sub>	16.6v
V <sub>out</sub>	2.04
V <sub>100k_RMS</sub>	10
I <sub>out</sub>	2.03
	Calculated value
$A_v = V_{out}/V_{in}$	0.12
$I_{in} = v_{100k\_RMS}/100k$	0.15
$A_i = I_{out}/I_{in}$	13.5
$Z_{in} = V_{in}/I_{in}$	110.66k
$Z_{out} = V_t/I_t$	212.3

Table 3: Conclusion values