



Faculty Of Engineering and Technology
Electrical and Computer Engineering Department
CIRCUITS AND ELECTRONICS LABORATORY

ENEE 2103

Experiment #: 10

The Operational Amplifier

Prepared by: Rahaf Naser 1201319

Instructor: Dr. Mahran Quraan

Teacher assistant: Eng. Rafah Rahhal

Date: 8/20/2023

Table of contents

1. Adding Application.....	1
2. Voltage Follower Application.....	5
3. Comparator Application.....	7
4. To investigate the effect of adding hysteresis.....	10

Table of Figures

Figure 1.1: Adding application circuit1.....	1
Figure 1.2: Adding application circuit2.....	1
Figure 1.3: Adding application circuit3.....	2
Figure 1.4: calculated voltage theoretical.....	3
Figure 1.5: The expression of v_o	4
Figure 2.1: Voltage Follower Application circuit	5
Figure 2.2: Output voltage.....	5
Figure 2.3: Output current.....	6
Figure 2.4: Output current with $R=10k$	6
Figure 3.1: Comparator Application circuit when $v_6 = 0$	7
Figure 3.2: Input and Output voltage when $V_6=0v$	7
Figure 3.3: Comparator Application circuit when $v_6 = 1.1$	8
Figure 3.4: Input and Output voltage when $V_6=1.1v$	8
Figure 3.5: Comparator Application circuit when $v_6 = -1.1$	9
Figure 3.6: Input and Output voltage when $V_6= -1.1v$	9
Figure 4.1: The effect of adding hysteresis circuit.....	10
Figure 4.2: Input and Output circuit.....	10

Table of Tables

Table 1: output voltage for adding OpAmp.....4

1.Adding Application

The circuit was connected as shown in figures below.

- 1) When $v_1=0.5\text{v}$ and $v_2 = 2\text{v} \rightarrow v_o = -6.991\text{v}$

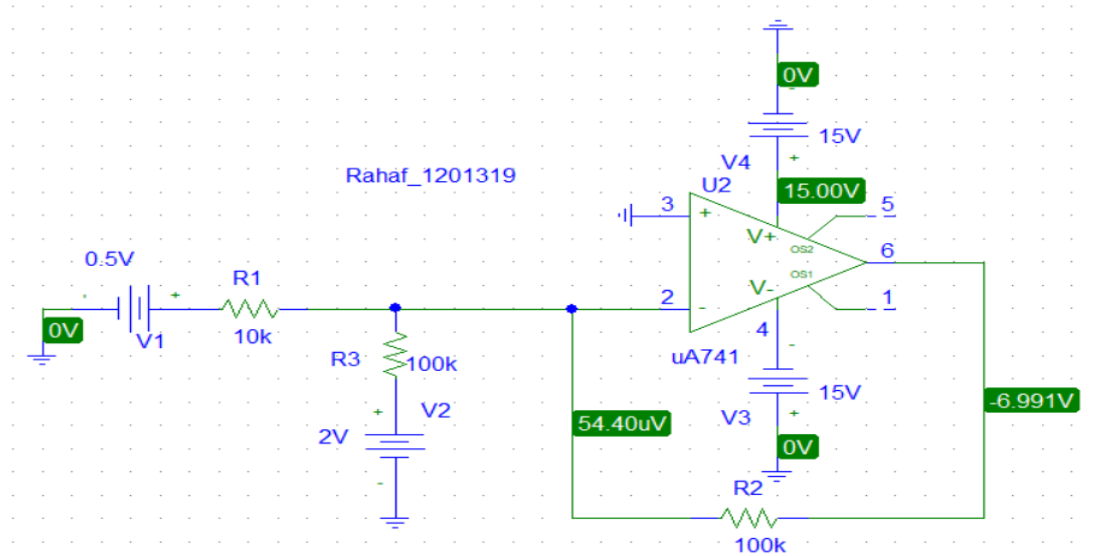


Figure 1.1: Adding application circuit1

- 2) When $v_1 = 0.3\text{v}$ and $v_2 = 4\text{v} \rightarrow v_o=-6.99\text{v}$

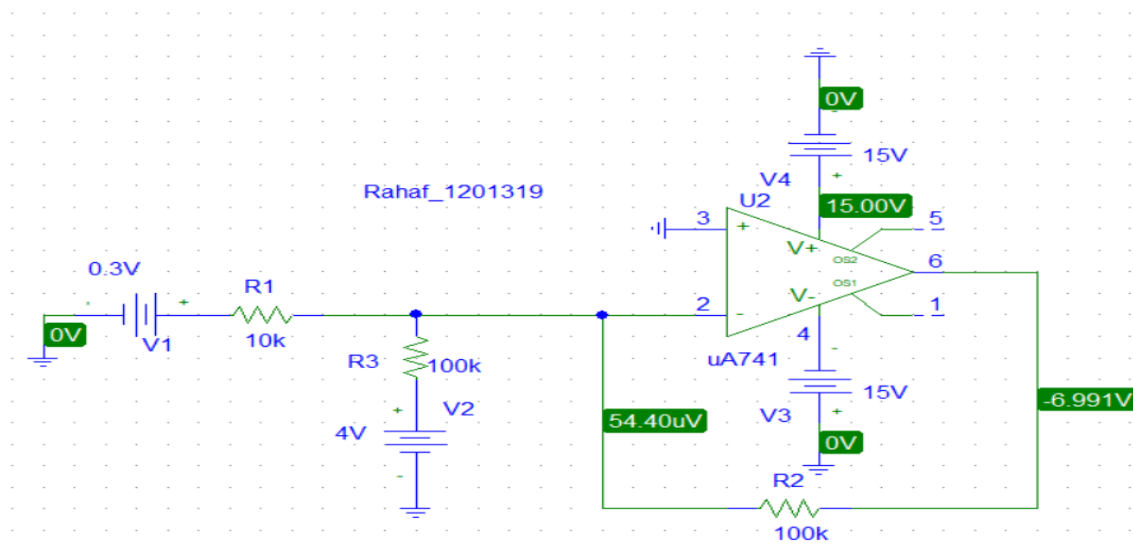


Figure 1.2: Adding application circuit2

3) When $v_1 = -1.5\text{V}$ and $v_2 = 6\text{V} \rightarrow v_o = 9.008\text{V}$

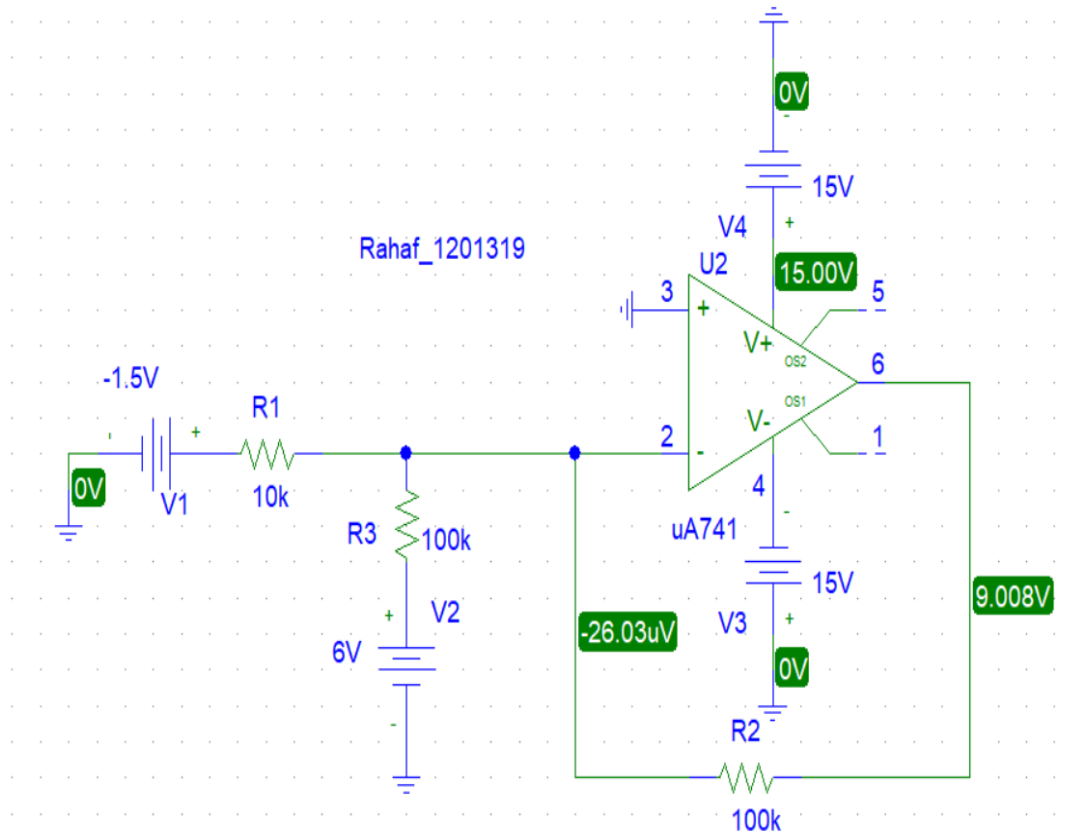


Figure 1.3: Adding application circuit3

Calculated voltage:

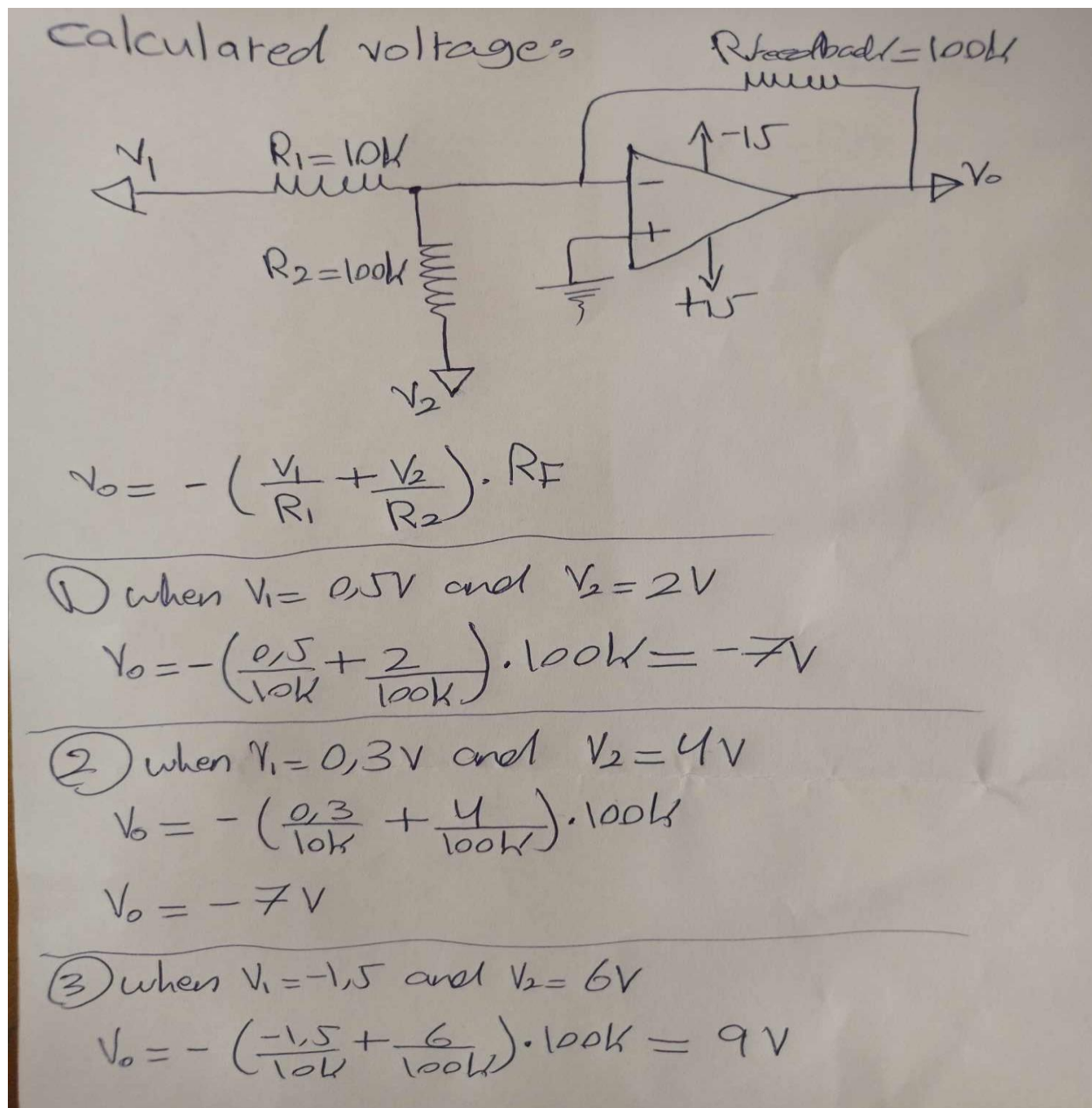


Figure 1.4: calculated voltage theoretical

Input voltage		Output voltage	
V1	V2	vo	Calculated voltage
0.5	2	-6.993	-7
0.3	4	-6.993	-7
-1.5	6	9.008	9

Table 1: output voltage for adding OpAmp

The expression relating vo to v1 and v2:

Handwritten derivation of the output voltage expression for an inverting summing amplifier:

$$V_o = - \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \cdot R_f$$

$$V_o = - \left[\frac{R_f \cdot V_1}{R_1} + \frac{R_f \cdot V_2}{R_2} \right]$$

$$V_o = - \frac{R_f}{R_1} \cdot V_1 - \frac{R_f}{R_2} \cdot V_2$$

$$V_o = X V_1 + Y V_2$$

$$\Rightarrow X = - \frac{R_f}{R_1} = - \frac{100k}{10k} = -10k$$

$$Y = - \frac{R_f}{R_2} = - \frac{100k}{100k} = -1k$$

$$\rightarrow V_o = -10 V_1 - V_2$$

Figure 1.5: The expression of vo

2. Voltage Follower Application

The circuit was connected as shown in figure 2.2 below. By Performing DC sweep For DC voltage source V_i from 0V to +20V using increment of 0.1V

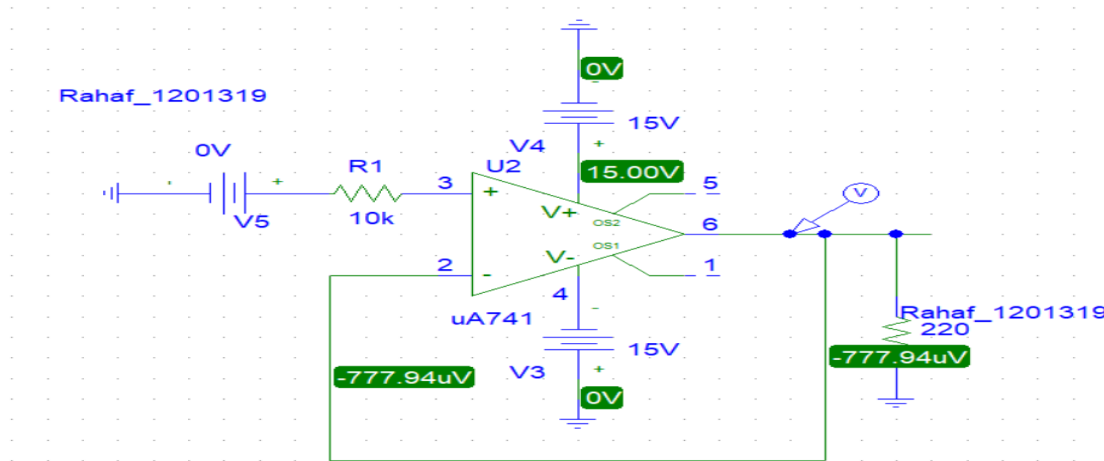


Figure 2.1: Voltage Follower Application circuit

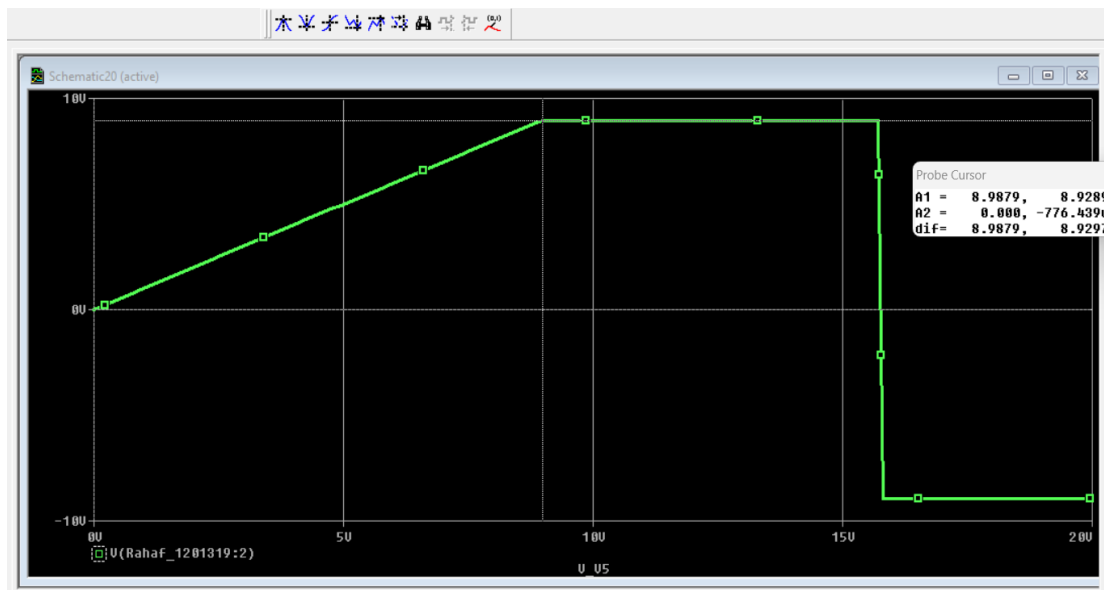


Figure 2.2: Output voltage

From the above figure, note that the output voltage (V_o) of the circuit closely follows the input voltage (V_i) without amplifying or attenuating it. The voltage follower, also known as a unity gain amplifier or buffer amplifier, has a voltage gain of approximately 1.

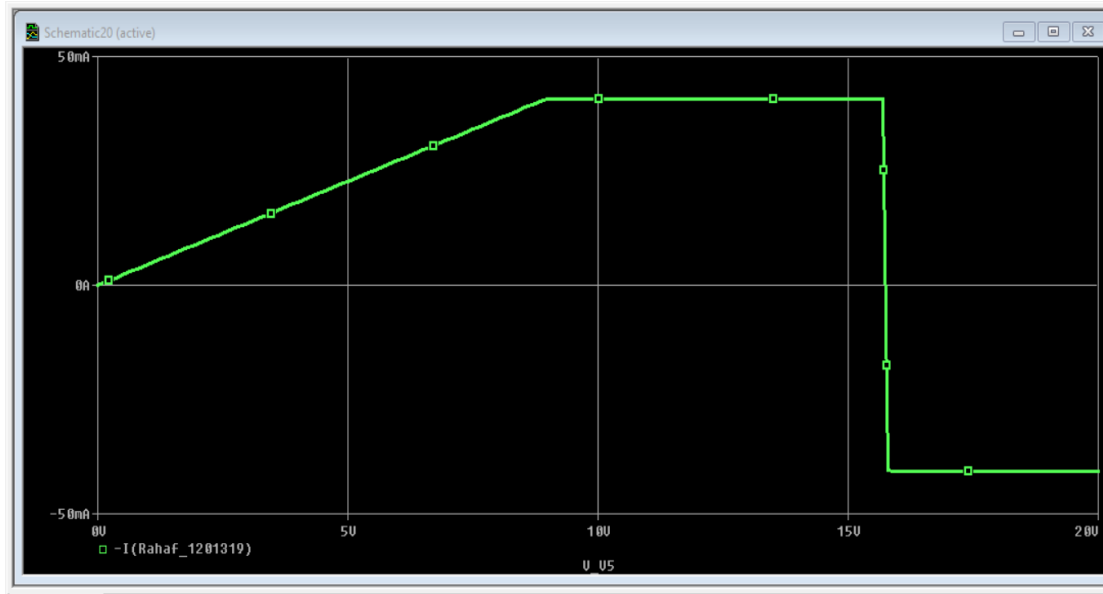


Figure 2.3: Output current

From the above figure, note that there is a current limit at the value 41mA, and this also leads to a voltage limit at the value 9 V.

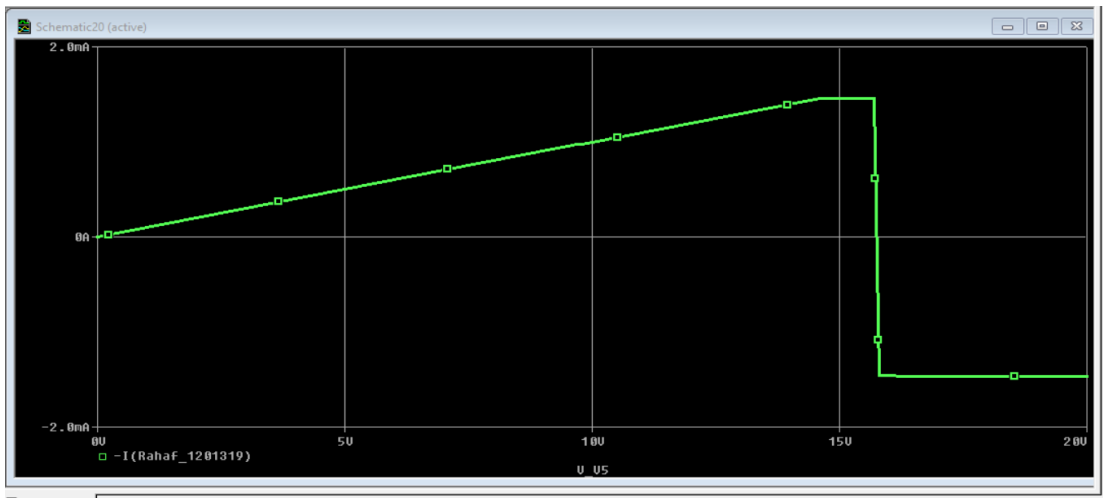


Figure 2.4: Output current with R=10k

From the above figure, note that there is a current limit at the value 1.46mA, and this also leads to a voltage limit at the value 14.5V

3. Comparator Application

The circuit was connected as shown in figures below. Uses 1 kHz triangular input signal to create a triangular wave form: $V_1 = -1V$, $V_2 = 1V$, $t_r = 0.5m$, $t_f = 0.5m$, $PW = 10n$, $Period = 1m$.

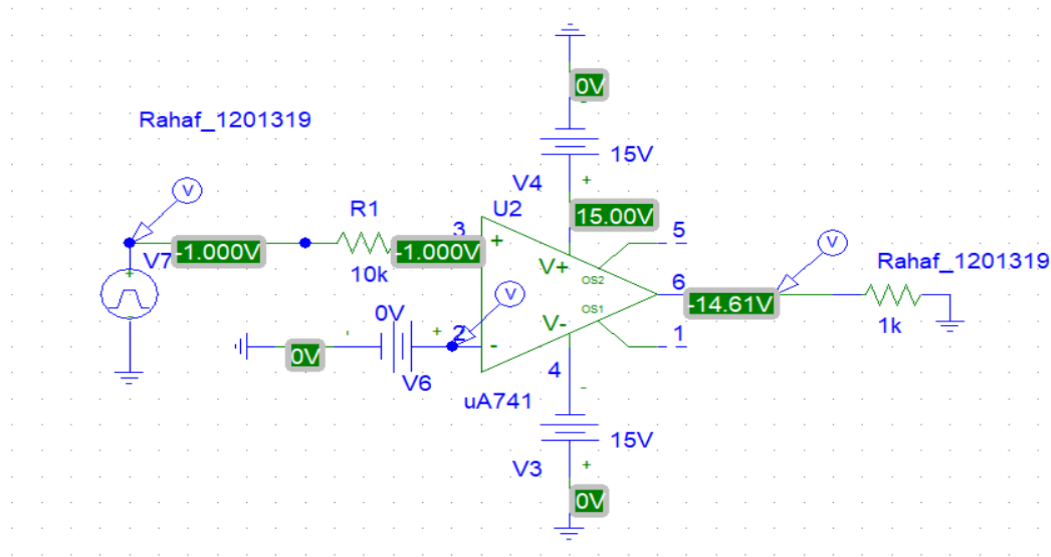


Figure 3.1: Comparator Application circuit when $v_6 = 0$

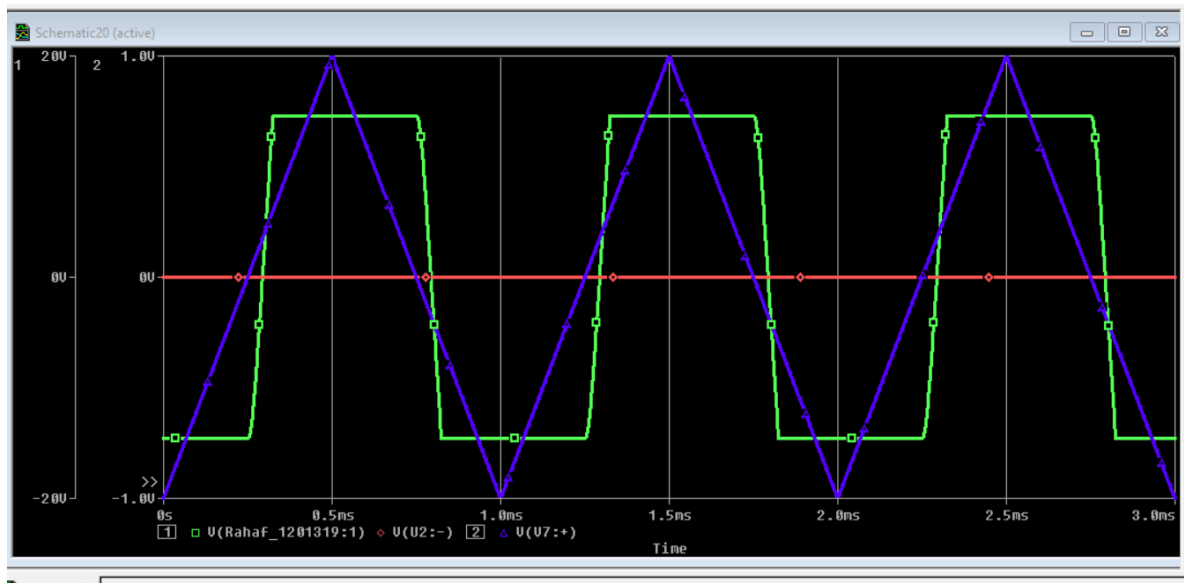


Figure 3.2: Input and Output voltage when $V_6 = 0v$

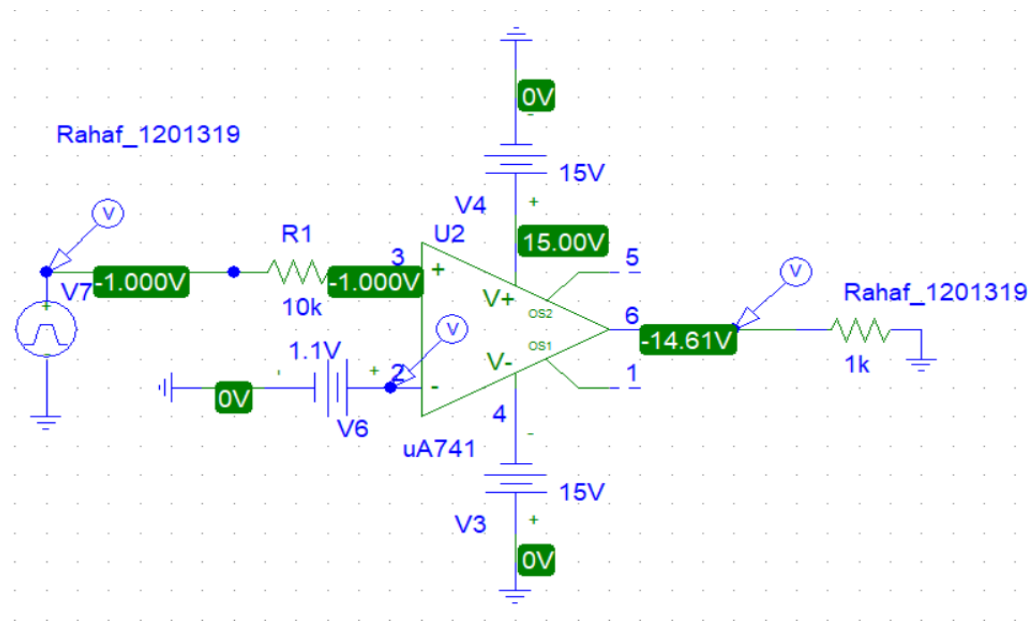


Figure 3.3: Comparator Application circuit when $v_6 = 1.1$

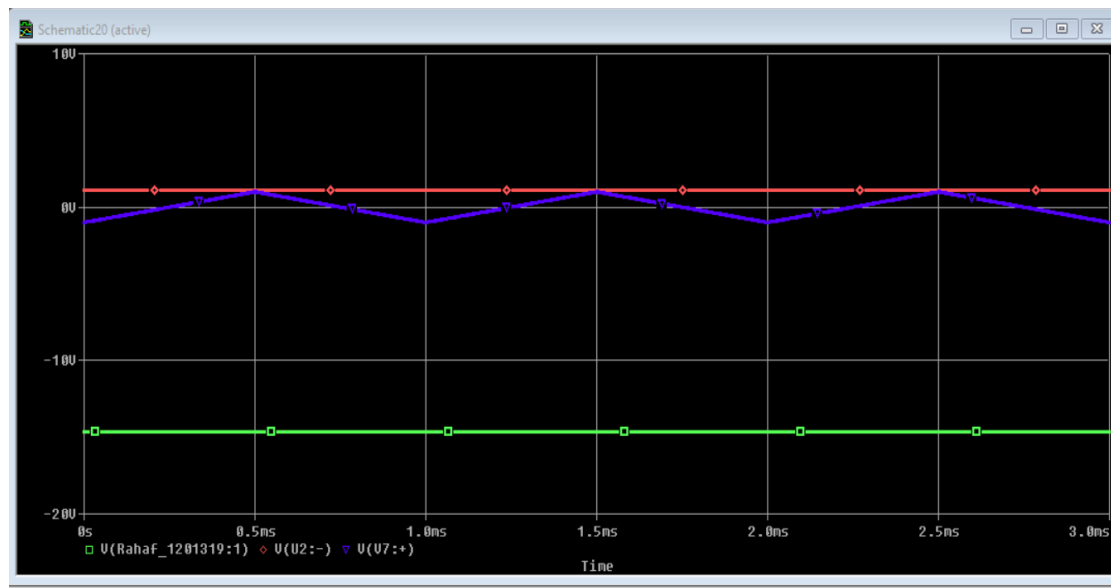


Figure 3.4: Input and Output voltage when $V_6 = 1.1v$

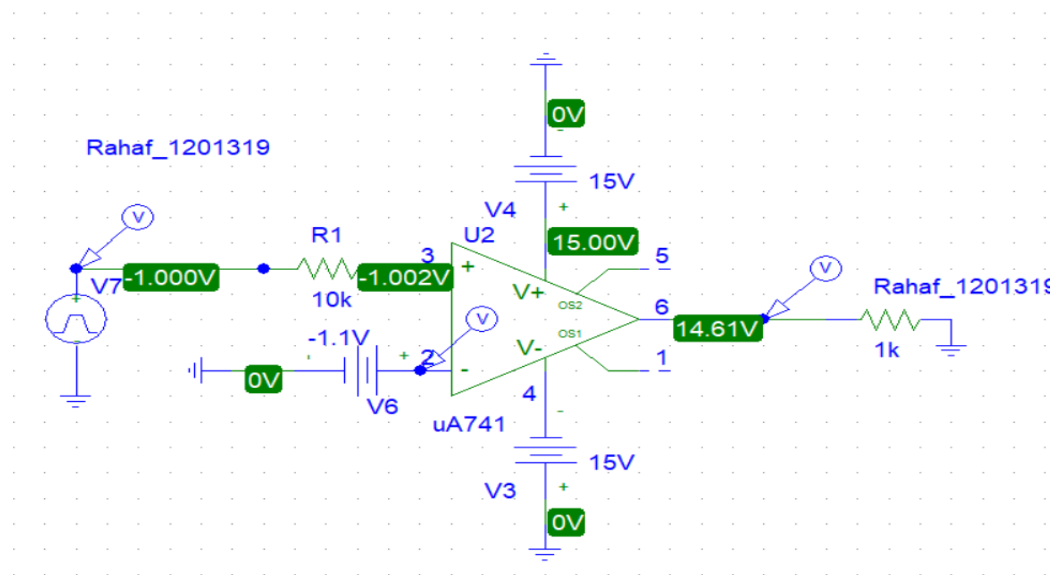


Figure 3.5: Comparator Application circuit when $v_6 = -1.1$

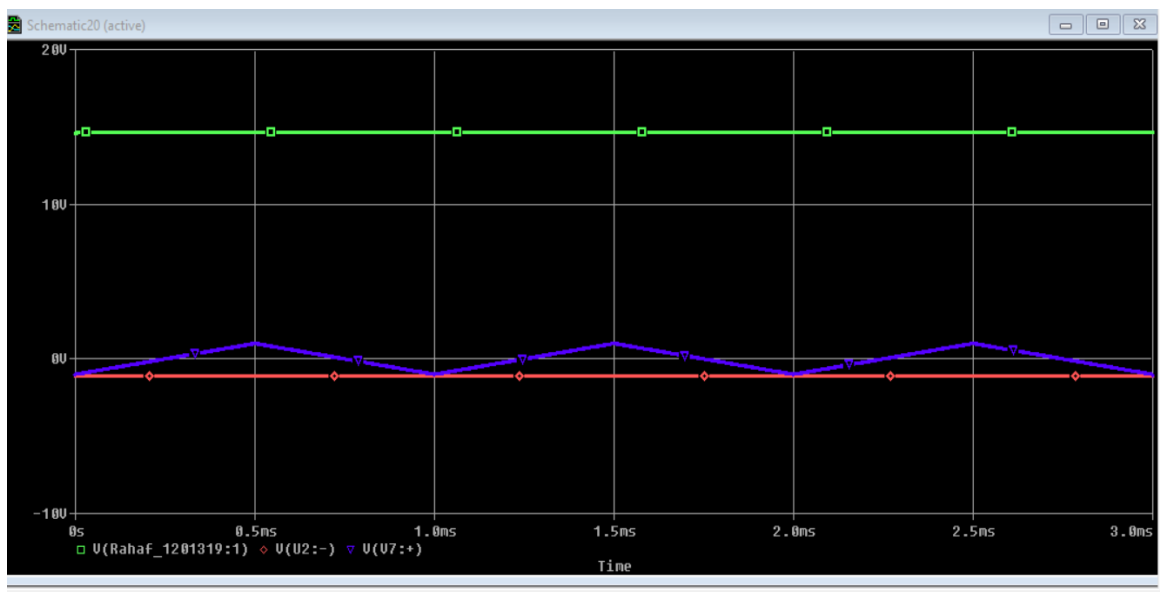


Figure 3.6: Input and Output voltage when $V_6 = -1.1v$

4. To investigate the effect of adding hysteresis

The circuit was connected as shown in figure 4.1 below, I Put $V_i(t) = 15V_{p-p}$ sine wave of frequency 1 kHz.

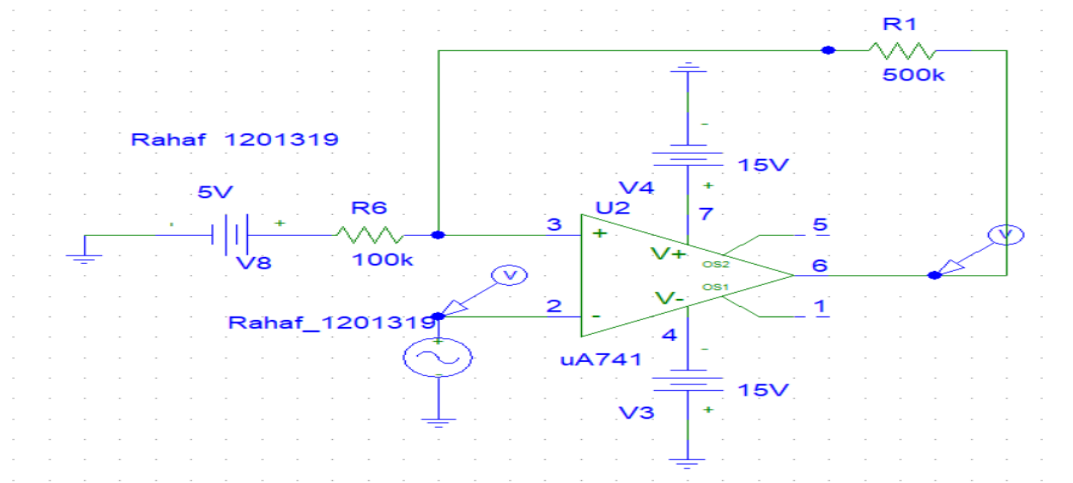


Figure 4.1: The effect of adding hysteresis circuit

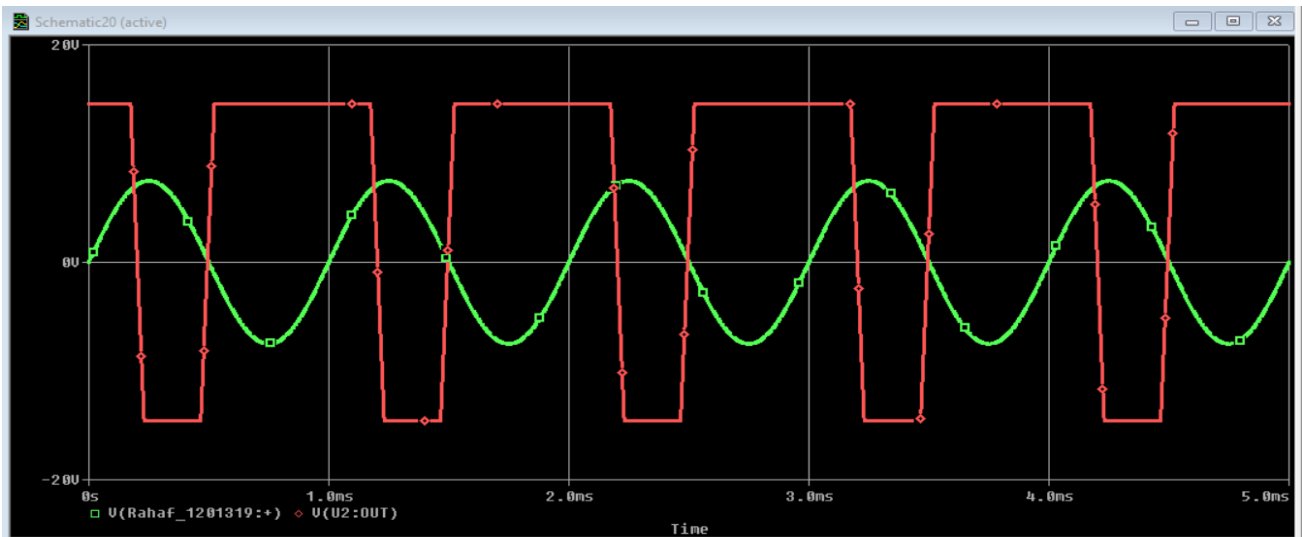


Figure 4.2: Input and Output circuit

The reference voltage at the non-inverting input changes creating two different reference voltage values and two different switching points. One point being called the Upper Trip Point (UTP), while the other is called the Lower Trip Point (LTP). The difference between these two trip points is known as Hysteresis.