



Faculty Of Engineering and Technology
Electrical and Computer Engineering Department
CIRCUITS AND ELECTRONICS LABORATORY

ENEE 2103

Experiment #: 3

First and Second Order Circuit

Prepared by:

Rahaf Naser 1201319

Instructor:

Dr. Mahran Quraan

Teacher assistant:

Eng. Rafah Rahhal

Date: 8/4/2023

Table of contents:


1.RC Circuit.....	1
2.RL Circuit.....	3
3.RLC Circuit.....	8
3.1.Response type.....	8
3.1.1.over damped response.....	8
3.1.2.critical damped response.....	9
3.1.3.under damped response.....	10
3.2.Response parameters.....	11

Table of Figures:

Fig(1.1).....	1
Fig(1.2).....	1
Fig(1.3).....	2
Fig(2.1).....	3
Fig(2.2).....	3
Fig(2.3).....	4
Fig(2.4).....	5
Fig(2.5).....	5
Fig(2.6).....	7
Fig(2.7).....	7
Fig(3.1.1.1).....	8
Fig(3.1.1.2).....	8
Fig(3.1.2.1).....	9
Fig(3.1.2.2).....	9
Fig(3.1.3.1).....	10
Fig(3.1.3.2).....	10
Fig(3.2.1).....	11


1.RC Circuits

Circuit using Pspice->

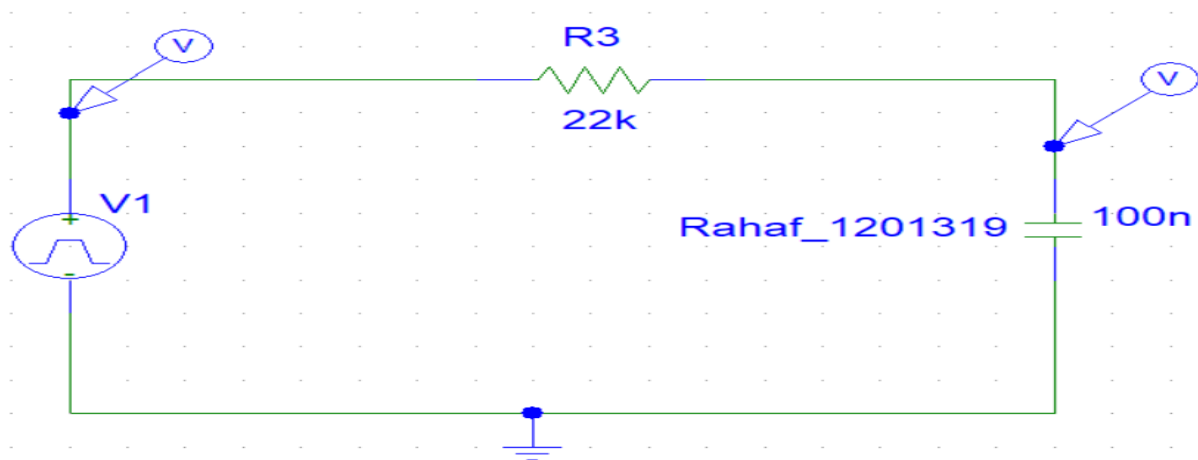


Fig(1.1)

Result->

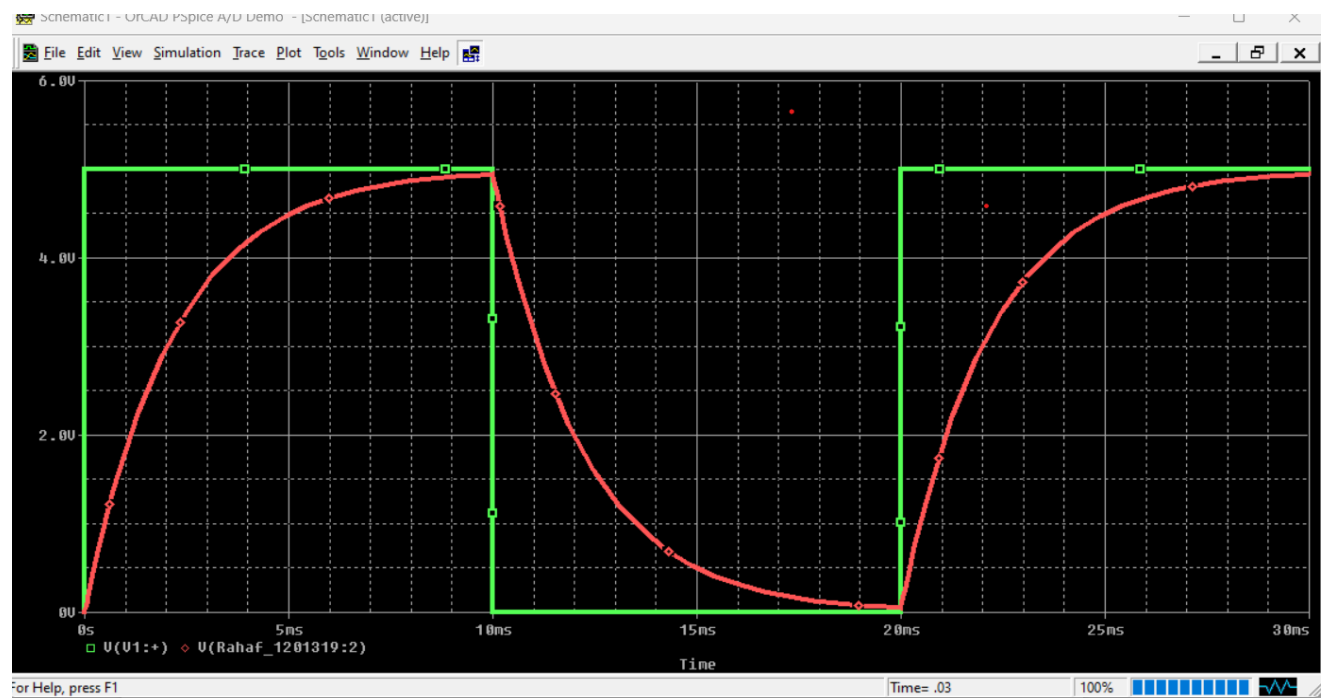

Fig(1.2)

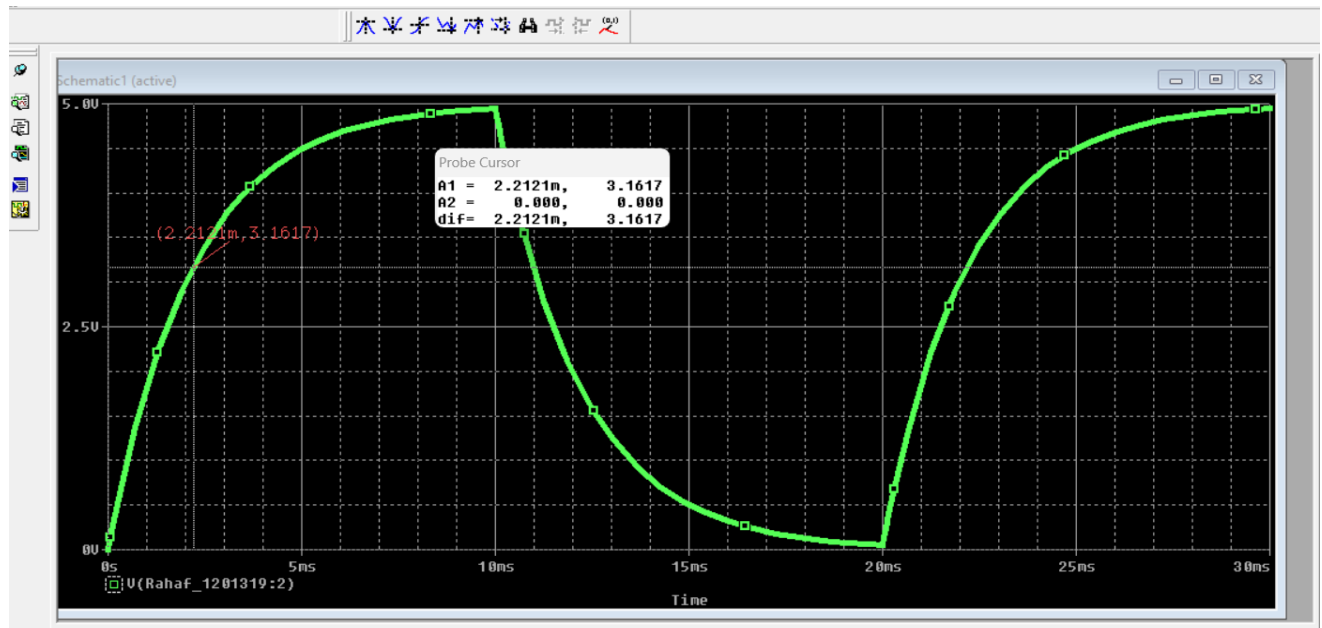

Fig(1.3)

To find T :

First we find that V_{max} (experimentally) = 4.9454 v

$$0.63 * 4.9454 = 3.1 \text{ v}$$

at $v = 3.1 \text{ v} \rightarrow t = 2.2 \text{ ms}$

so $T = 2.212 \text{ ms}$

To find the time constant theoretically, we have $R = 22 \text{ k}\Omega$, and $C = 100 \text{ nF}$

$$\rightarrow T \text{ (theoretically)} = RC = 22 * 10^3 * 100 * 10^{-9} = 2.2 \text{ ms}$$

▪ Steady state voltage value on the capacitor:

The capacitor voltage reaches its steady state value at $V_c(0)$, C appears as an open circuit.

$$\rightarrow V_c \text{ steady state} = 5 \text{ v}$$


▪ The value of the capacitor:

$$o C \text{ (experimentally)} = T \text{ (experimentally)} / R = 2.5814 \text{ ms} / 22 \text{ K} = 117.3 \text{ nF}$$

$$o C \text{ (theoretically)} = 100 \text{ nF}$$


2.RL Circuit

Circuit using Pspice->

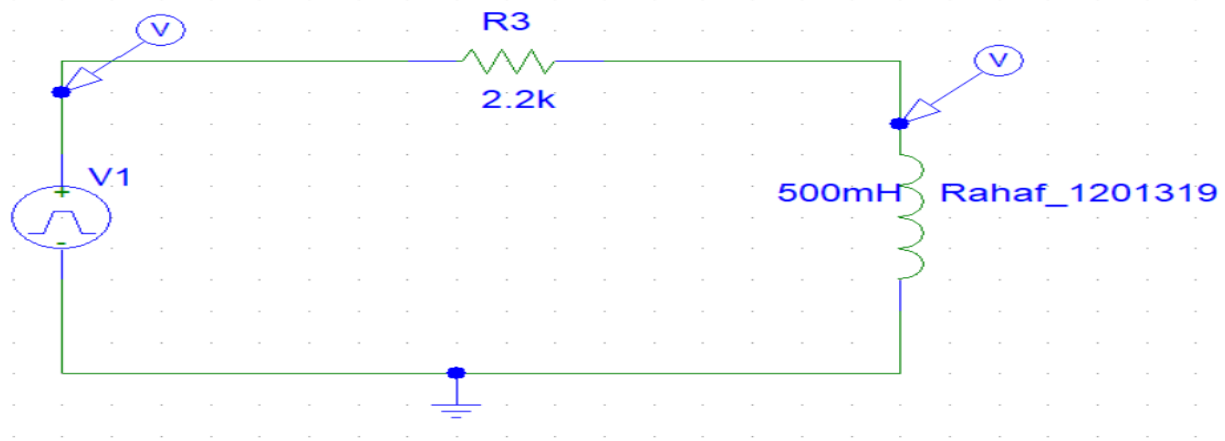


Fig(2.1)

Result->

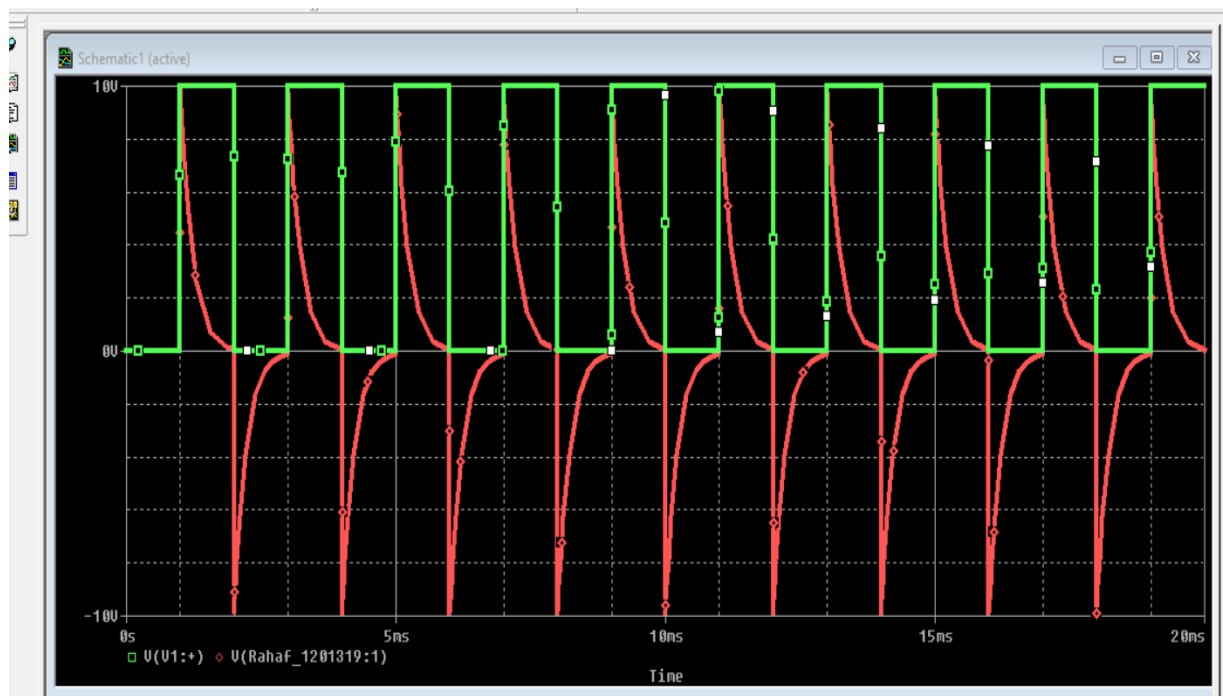

Fig(2.2)

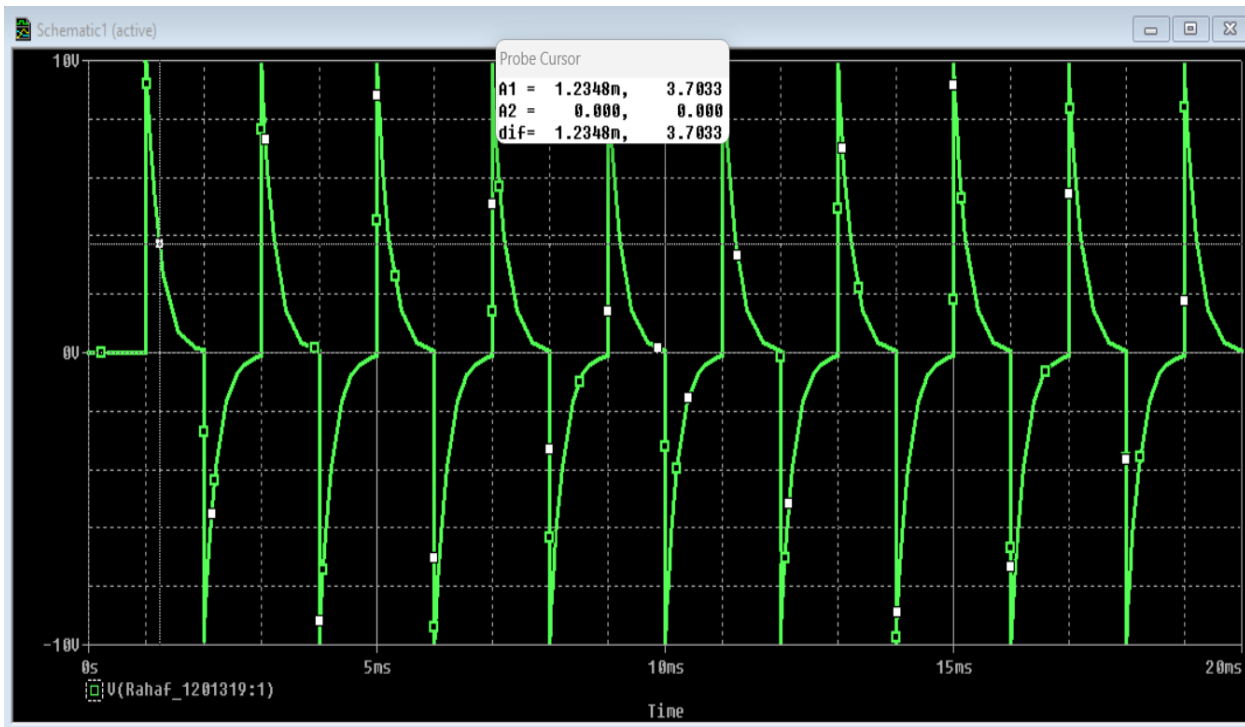

Fig(2.3)

$$V_{\max} = 9.879\text{v}$$

$$V(t) \text{ discharging} = 0.37 V_{\max} \rightarrow V(t) = 0.37 * 9.87 = 3.5619\text{v}$$

$$t \text{ when } v = 3.6519 = 1.2348\text{ms}$$

$$\text{so, } T = 1.2348\text{ms} - 1\text{ms} = 0.2348\text{ms}$$

To find the time constant theoretically, we have $R=2.2\text{k}\Omega$, and $L=500\text{mH}$

$$\text{so } \rightarrow T \text{ (theoretically)} = L/R = 500\text{m}/2.2\text{k} = 0.227\text{ms}$$

Steady state voltage value on the inductor:

The capacitor voltage reaches its steady state value $V_L(0)$, C appears as a short circuit.


$$\rightarrow V_L \text{ steady state} = 10\text{ v}$$

▪ The value of the inductor:


o $L(\text{experimentally}) = T(\text{experimentally}) * R = 0.2268\text{ms} * 2.2\text{K} = 498.96 \text{ mH}$

o $L(\text{theoretically}) = 500\text{mH}$

Current response:

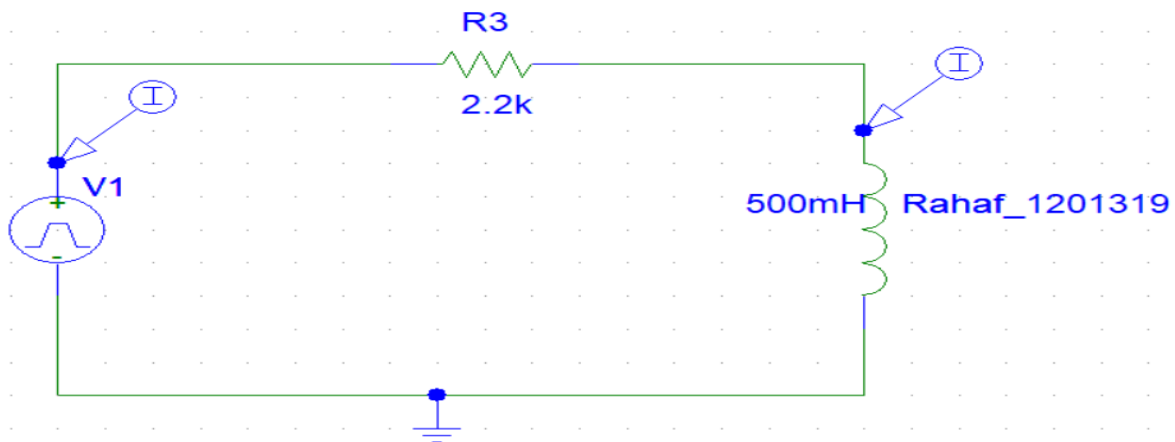

Fig(2.4)

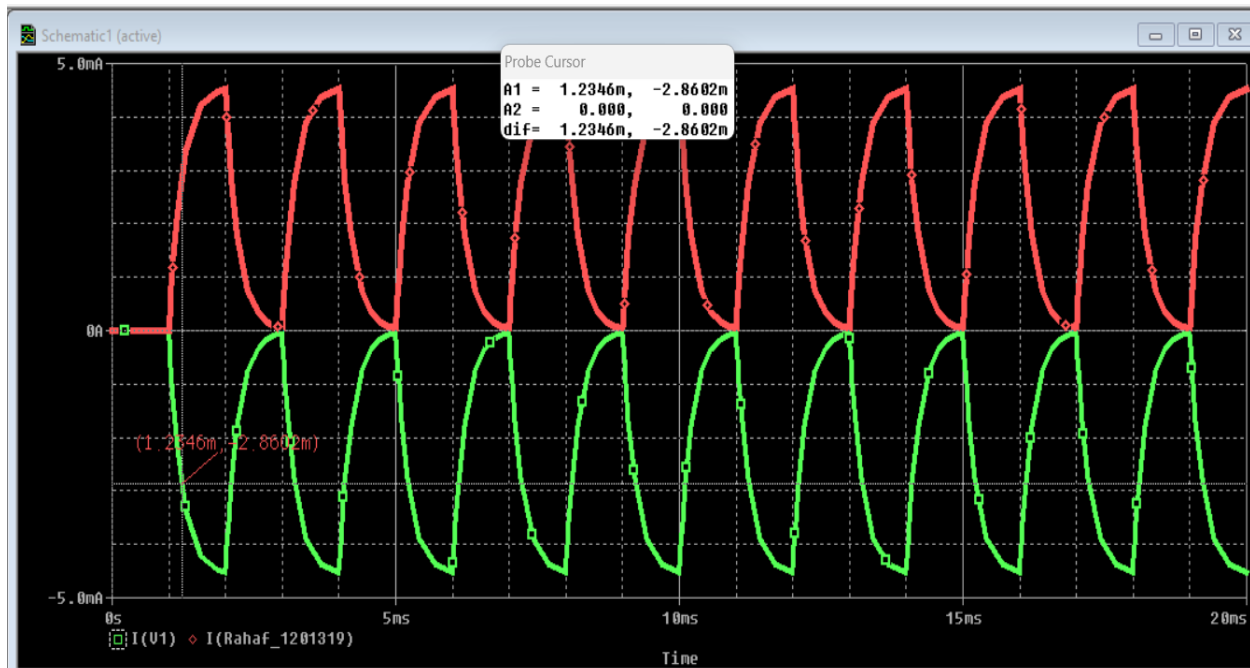

Fig(2.5)

$I_{\max} \text{ (experimentally)} = 4.4897\text{A}$

- Time constant:

- To find the time constant experimentally, we find the time at charging

$$I(t)_{\text{charging}} = 0.63 I_{\max} \rightarrow I(t) = 0.63 * 4.4897 = 2.8285\text{mA}$$

$$t \text{ (at } I = 2.8285\text{mA)} = 1.2230\text{ms}$$

$$\text{so, } T \text{ (experimentally)} = 1.2230\text{ms} - 1\text{ms} = 0.2230\text{ms}$$

- Steady state current value on the inductor:

The inductor current reaches its steady state value at $V_L(0)$, L appears as a short circuit..


$$\rightarrow I_L \text{ steady state} = 10/2.2\text{k} = 4.545 \text{ mA}$$

RL circuit after change the period of the periodic square wave to $T=2*$ time constant of inductor:

$$T = 2 * L/R = 500\text{m}/2.2\text{k} = 0.454\text{ms}$$


$$F = 1/T = 2.2 \text{ KHz.}$$

Voltage response->

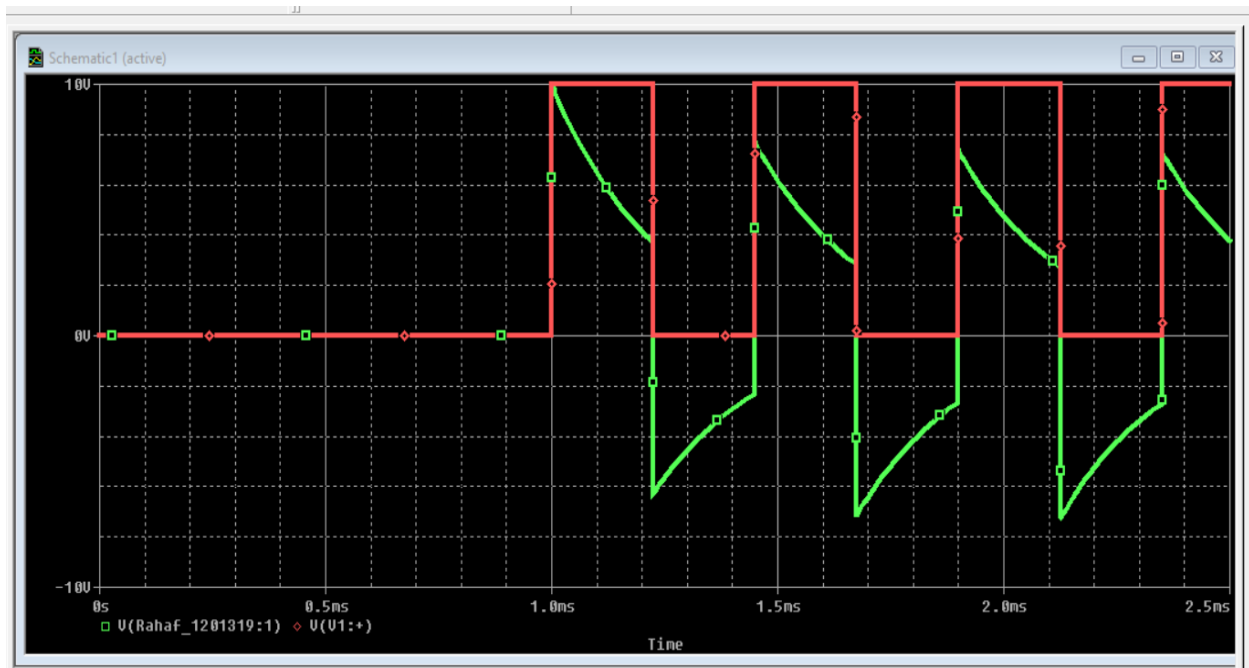

Fig(2.6)

Current response->

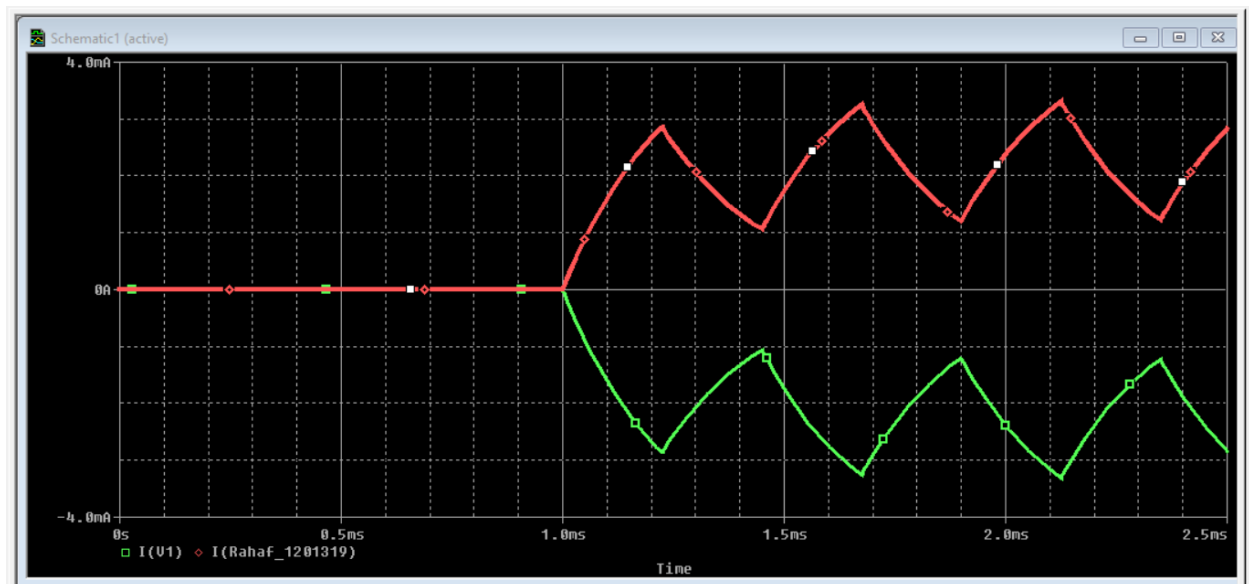


Fig(2.7)

3.RLC Circuits

3.1.Response type


3.1.1.over damped response

Circuit using Pspice->

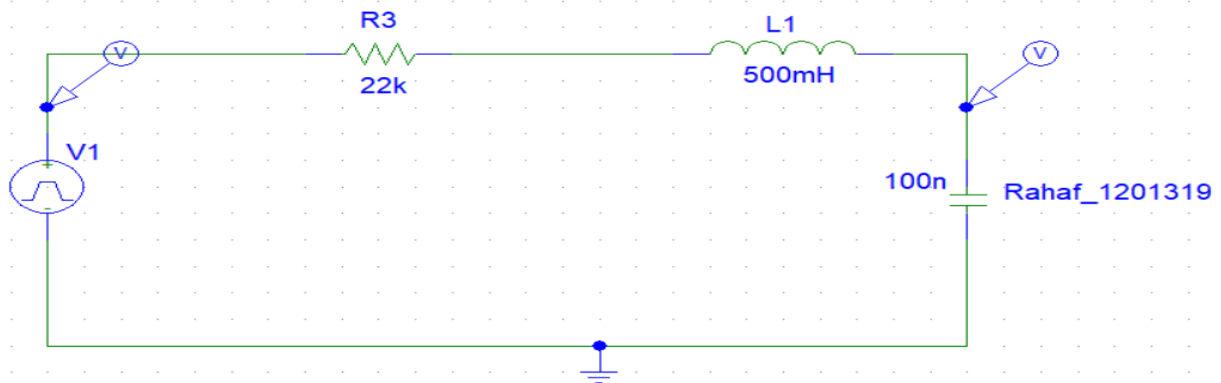

Fig(3.1.1.1)

Result->

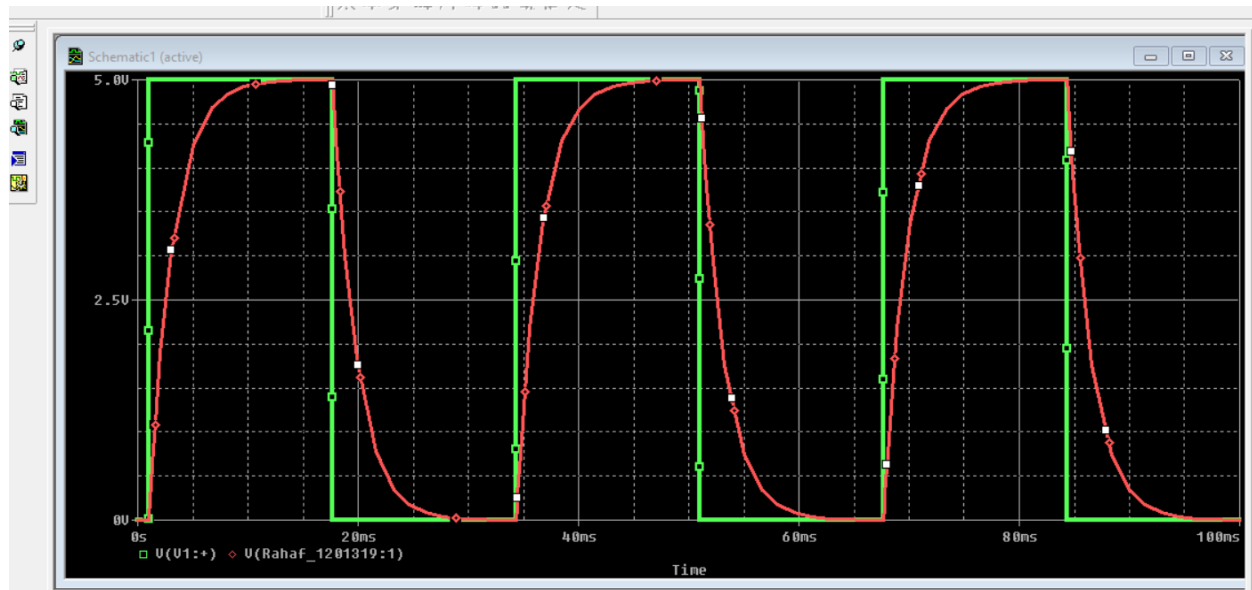

Fig(3.1.1.2)

The response is over damped since we have $\alpha > \omega$

$$\alpha = R/2L = 22K/2 * 500m = 22000 \text{ rad/s}$$

$$\omega = 1/(LC)^{0.5} = 1/(500m * 100n)^{0.5} = 4472.13 \text{ rad/s}$$


3.1.2. critical damped response

To get critically damped response we have $\alpha = \omega$.

Therefore, the value of the resistance to give critically damped response will be:


$$R/2L = 1/(L \cdot C)^{0.5} \rightarrow R/(2 \cdot 500\text{m}) = 1/(500\text{m} \cdot 100\text{n})^{0.5} \rightarrow R = 4472.13$$

Circuit using Pspice->

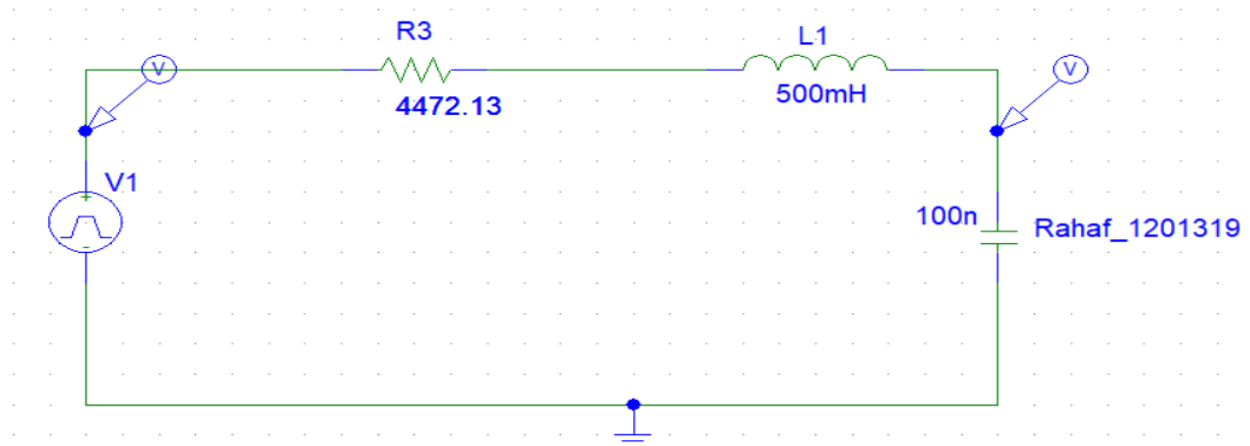

Fig(3.1.2.1)


Result->

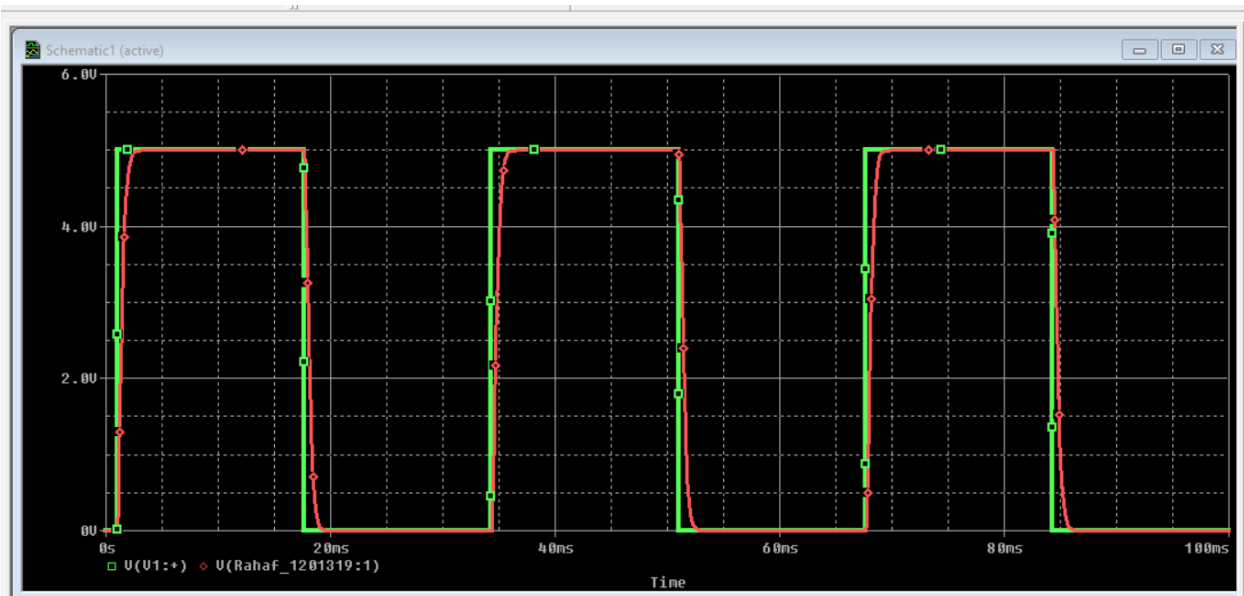

Fig(3.1.2.2)


3.1.3 under damped response:

→ Circuit using PSpice:

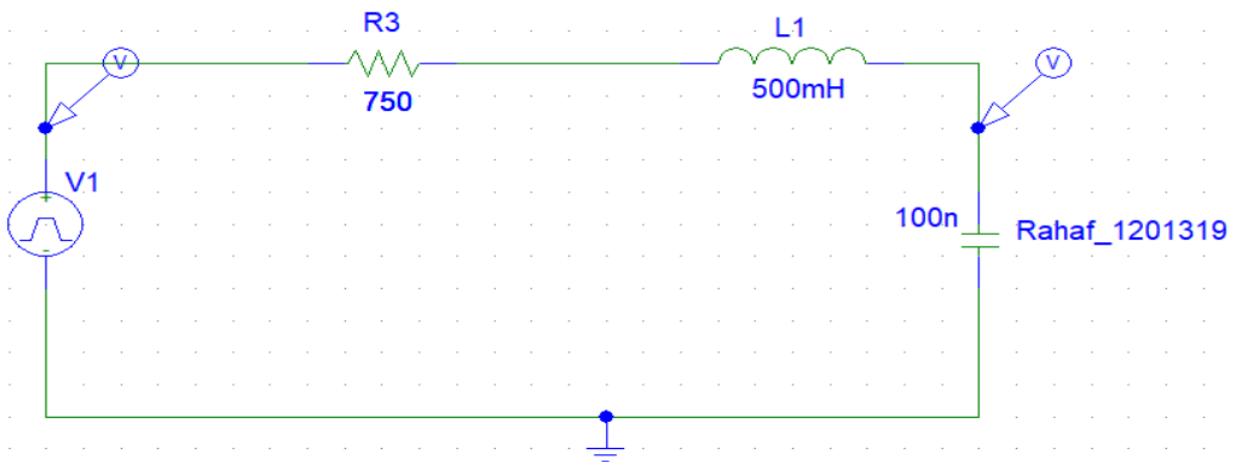

Fig(3.1.3.1)

Result->

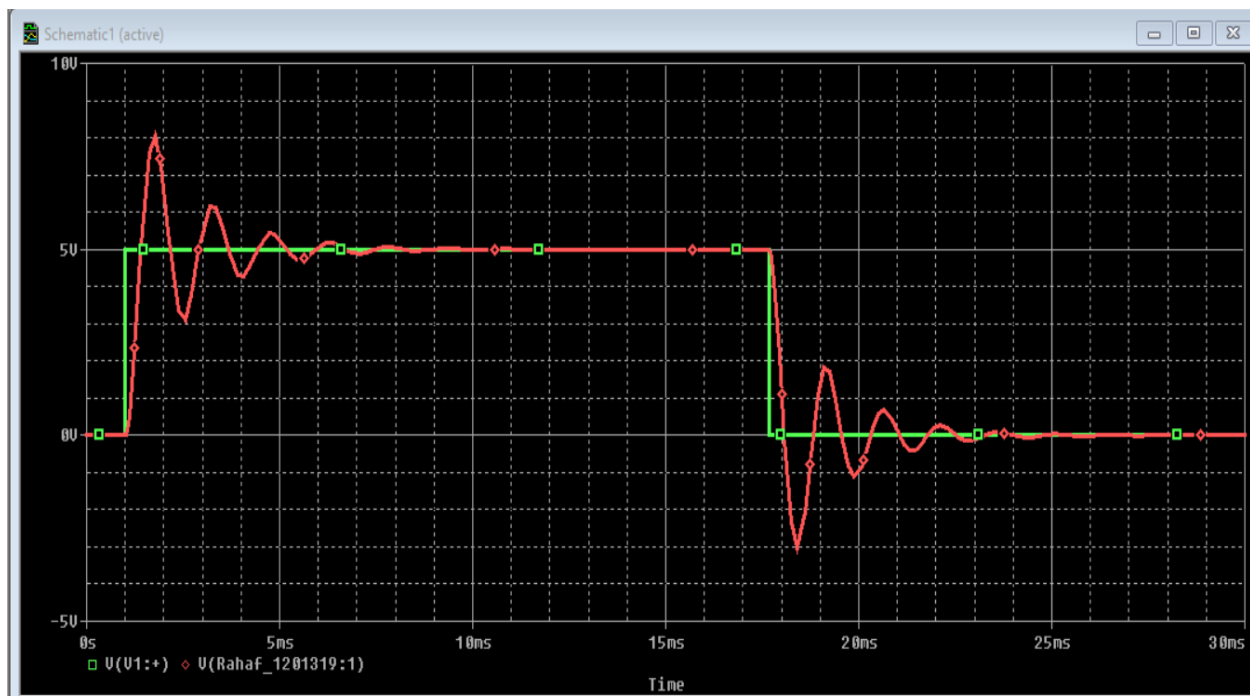

Fig(3.1.3.2)


The response is under damped since we have $\alpha < \omega$

$$\alpha = R/2L = 750\Omega / 2 * 500\text{m} = 750 \text{ rad/s}$$

$$\omega = 1/(LC)^{0.5} = 1/(500\text{m} * 100\text{n})^{0.5} = 4472.13 \text{ rad/s}$$

3.2.Response Parameters

Circuit using Pspice->

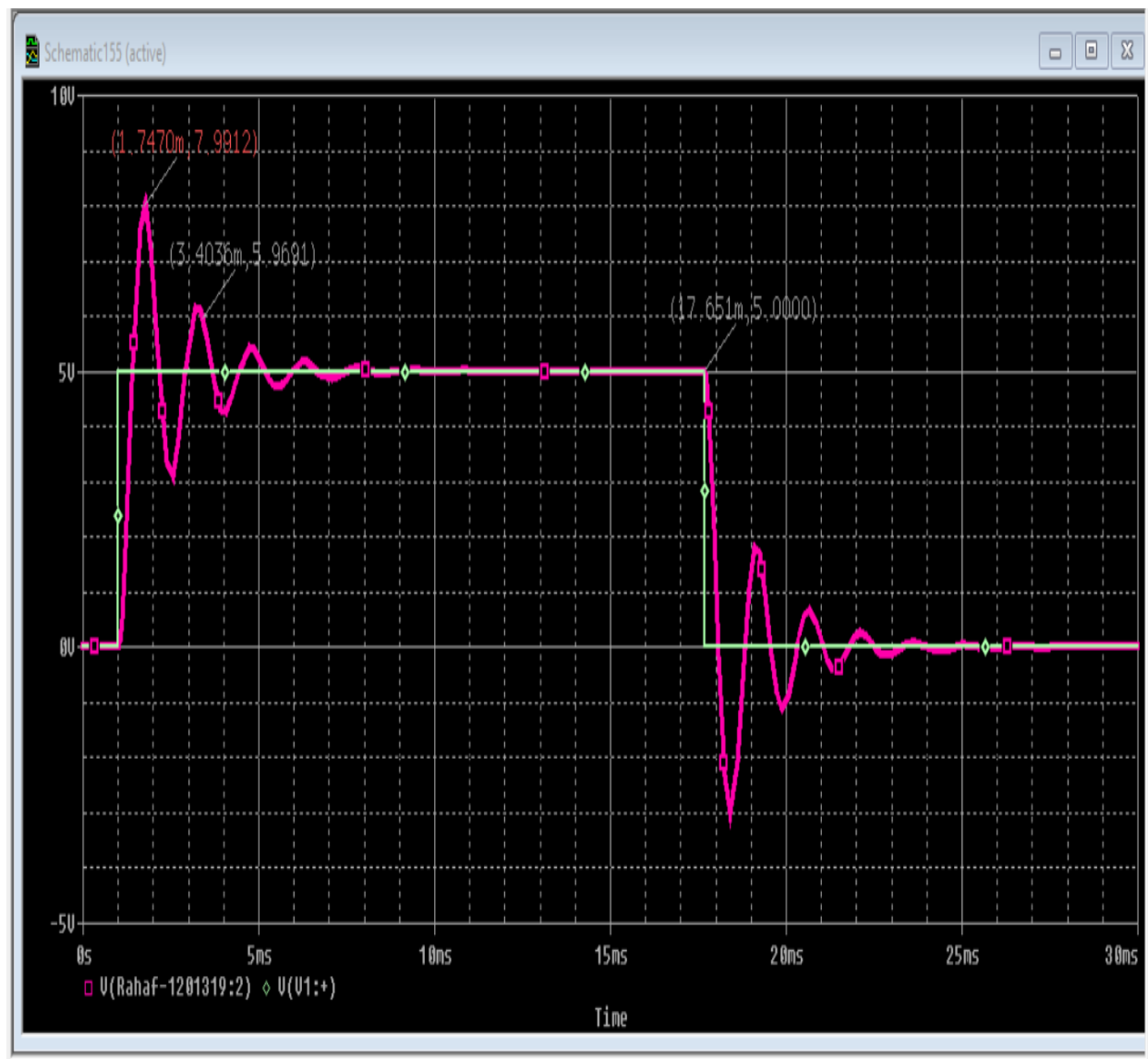

Fig(3.2.1)

$$t_a = 1,747 \text{ ms}$$

$$t_b = 3,4036 \text{ ms}$$

$$V_a = 7,9912 \text{ V}$$

$$V_b = 5,969 \text{ V}$$

$$V_o(\infty) = 5,0 \text{ V}$$

$$T = \frac{t_b - t_a}{\frac{\ln(V_a - V_o(\infty))}{(V_b - V_o(\infty))}} = \frac{3,4036 - 1,747}{\frac{\ln(7,9912 - 5,0)}{(5,969 - 5,0)}} = 1,2496 \text{ ms}$$

$$\text{damping coefficient } \alpha = \frac{1}{T} = 0,8 \text{ krad/sec.}$$

$$\text{damped radian frequency } \omega_d = \frac{2\pi}{t_b - t_a} = \frac{2\pi}{3,4036 - 1,747} = 3,8 \text{ krad/sec}$$

damped radian frequency (theoretically) ω

$$\omega_d = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{500\text{m} * 100\text{n}}} = 4,47213 \text{ krad/s}$$