



**Faculty Of Engineering and Technology**  
**Electrical and Computer Engineering Department**  
**CIRCUITS AND ELECTRONICS LABORATORY**  
**ENEE 2103**  
**Experiment #: 11**  
**Zener Diodes and Voltage Regulators**

---

**Prepared by:** Rahaf Naser 1201319

**Partners:** Sewar Abueid 1200043

Rana Deek 1201724

**Instructor:** Dr. Mahran Quraan

**Teacher assistant:** Eng. Rafah Rahhal

**Section:** 4

**Date:** 8/23/2023

## 1.Abstract

The aim of this experiment is to construct the I.V characteristic of Zener diode, and to demonstrate the use of Zener diode as voltage regulator, also to examine the operation of voltage regulator. There are many tools used in this experiment and these tools are resistors, Zener diodes, dc input voltage, BJT transistors, operational amplifiers, Digital multi meter(DMM), three terminal fixed voltage regulator(7805), and the LM317 adjustable voltage regulator.

## Table of contents

1. Abstract.....	II
2. Theory.....	1
2.1. Zener Diode.....	1
2.2. Zener Diode Applications.....	1
2.3. How Does a Voltage Regulator Work.....	2
2.4. A Regulated Power Supply.....	2
2.5. 7805 Voltage Regulator.....	3
2.6. the LM317 adjustable voltage regulator.....	3
3. Procedure & Discussion.....	5
3.1. ZENER DIODE.....	5
3.2. THE VOLTAGE REGULATED POWER SUPPLY.....	12
3.3. THREE TERMINAL FIXED VOLTAGE REGULATOR 7805.....	13
3.4. THE LM317 ADJUSTABLE VOLTAGE REGULATOR.....	13
4. Conclusion.....	16
5. References.....	17
6. Appendices.....	18

## Table of Figures

Figure 2.1: Zener diode symbol.....	1
Figure 2.2: linear regulator.....	2
Figure 2.3: regulated power supply.....	2
Figure 2.4: 7805 voltage regulator.....	3
<i>Figure 2.5 : LM317 Voltage Regulator Circuit.....</i>	<i>4</i>
Figure 3.1.1: Zener diode circuit.....	5
Figure 3.1.2: VZ and I graph.....	8
Figure 3.1.3: circuit after adding RL.....	9
Figure 3.2.1: voltage regulated power supply circuit.....	10
Figure 3.3.1: three terminal fixed voltage regulator circuit.....	12
Figure 3.4.1: LM317 adjustable voltage regulator circuit.....	13

## Table of Tables

Table1: values of $V_Z$ and $V_R$ and $I$ .....	5
Table2: values of $V_L$ after adding $R_L$ .....	9
Table3: values of $V_L$ when $E=10v$ .....	9
Table4: values of $V_o$ and $I_o$ after adding $R_L$ .....	10
Table5: values of $V_o$ when change the value of $R_2$ .....	11
Table6: values of $V_L$ and $I_L$ when $R_L$ changes.....	12
Table7: values of $V_L$ and $I_L$ when $R_L=100\text{ ohm}$ .....	13
Table8: values of $V_L$ and $I_L$ when $V_i=10v$ .....	14
Table9: values of $V_L$ and $I_L$ when $R_L=1K$ .....	14
Table10: values of $V_L$ and $I_L$ .....	15

## 2.Theory

### 2.1. Zener Diode

Zener diodes are silicone-based discrete semiconductor devices which allow current to flow bidirectionally - either reverse or forward. Diodes are comprised of a heavily-doped P-N silicone junction.

Zener diodes have a set reverse breakdown voltage. When this is reached, they start to conduct current and continue to operate unceasingly in the reverse bias direction without incurring damage. One of the main benefits of Zener diodes is that a varying range of voltages will still maintain a constant voltage drop across the diode. As a result, Zener diodes can be used for voltage regulation applications.[1]

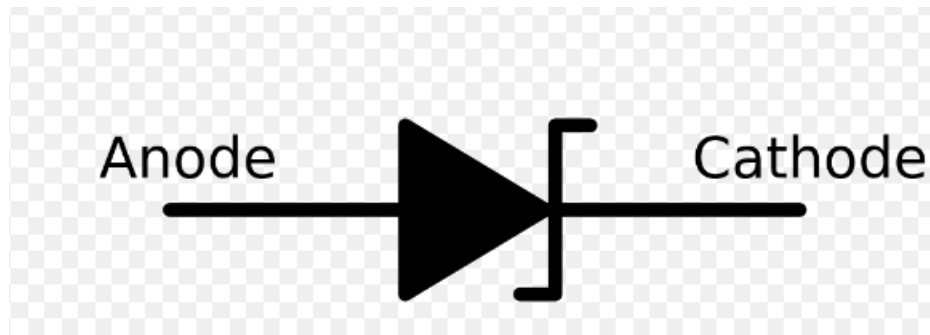


Figure 2.1: Zener diode symbol

### 2.2. Zener Diode Applications

Zener diodes are used for a range of applications, including:

- 1)Voltage regulation.
- 2)Voltage reference.
- 3)Surge suppression.
- 4)Switching applications.
- 5)Clipper circuits. [1]

### 2.3. How Does a Voltage Regulator Work

A voltage regulator is a circuit that creates and maintains a fixed output voltage, irrespective of changes to the input voltage or load conditions.

Voltage regulators (VRs) keep the voltages from a power supply within a range that is compatible with the other electrical components. While voltage regulators are most commonly used for DC/DC power conversion, some can perform AC/AC or AC/DC power conversion as well. This article will focus on DC/DC voltage regulators.[2]

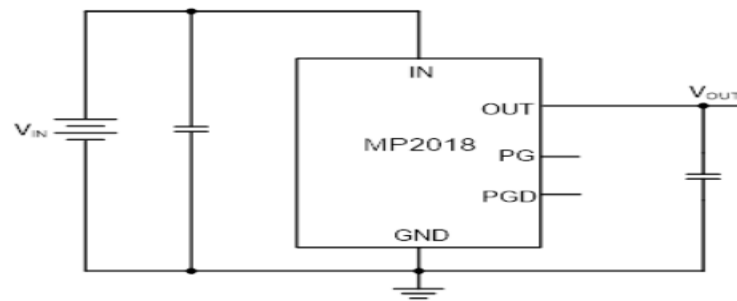


Figure 2.2: linear regulator

### 2.4. A Regulated Power Supply

Regulated power supplies have voltage regulators on their output. This means that the regulator ensures the output voltage will always stay at the rated value of the power supply, regardless of the current that the device is consuming. Any change in the input voltage will not affect the output voltage because of the regulators.

This works as long as the device is not drawing more than the rated output current of the power supply. In fancy electrical terms, a regulated power supply provides a constant output voltage, independent of the output current. A regulated power supply with multiple regulators can offer multiple output voltages for operating different devices. Regulated power supplies maintain the voltage at the desired level and are ideal for almost all types of electronic devices because of the steady supply of voltage they offer.[3]

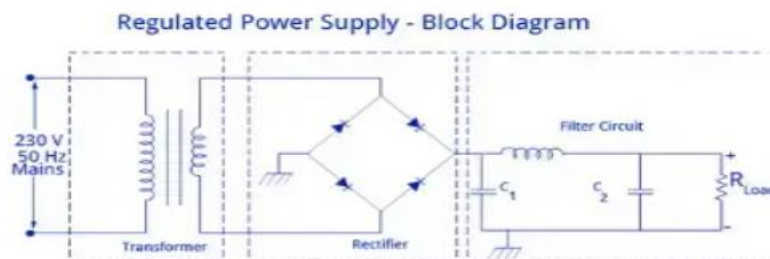


Figure 2.3: regulated power supply

## 2.5. 7805 Voltage Regulator

7805 is a three terminal linear voltage regulator IC with a fixed output voltage of 5V which is useful in a wide range of applications. Currently, the 7805 Voltage Regulator IC is manufactured by Texas Instruments, ON Semiconductor, Diodes incorporated, Infineon Technologies.

Some of the important features of the 7805 IC are as follows:

- It can deliver up to 1.5 A of current (with heat sink).
- Has both internal current limiting and thermal shutdown features.
- Requires very minimum external components to fully function.[4]

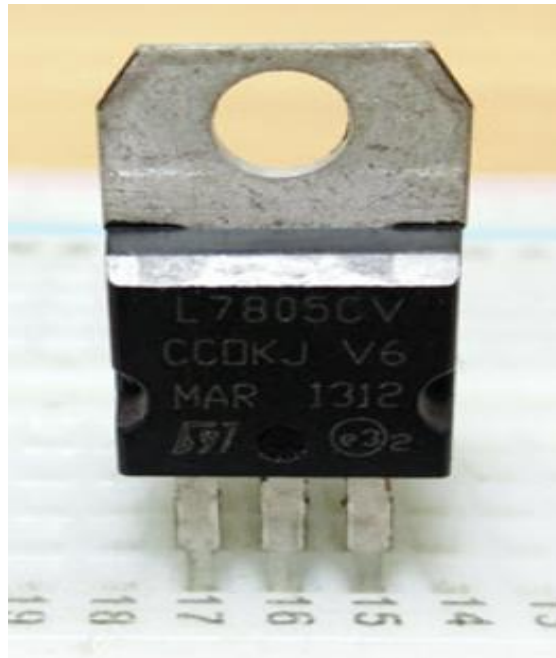


Figure 2.4: 7805 voltage regulator

## 2.6. the LM317 adjustable voltage regulator


The three terminals are input pin, output pin, and adjustment pin. The LM317 circuit is capable to provide variable DC power supply with an output of 1A and can be adjusted up to 30V. The circuit consists of a low-side resistor and high-side resistor connected in series forming a resistive voltage divider which is a passive linear circuit used to produce an output voltage.

Decoupling capacitors are used for decoupling or to prevent undesired coupling of one part of an electrical circuit from another part. To avoid the effect of noise caused by some circuit elements over the remaining elements of the circuit, the decoupling capacitors in the circuit are used for addressing the input noise and output transients. A heat sink is used with the circuit to avoid the components getting overheated due to more power dissipation.[5]



There are some special features of the LM317 regulator and a few are as follows:

- 1) It is capable of providing an excess current of 1.5A, hence it is conceptually considered as an operational amplifier with an output voltage ranging from 1.2V to 37V.
- 2) The LM317 voltage regulator circuit internally consists of thermal overload protection and short circuit current limiting constant with temperature.
- 3) Stocking many fixed voltages can be eliminated.[5]

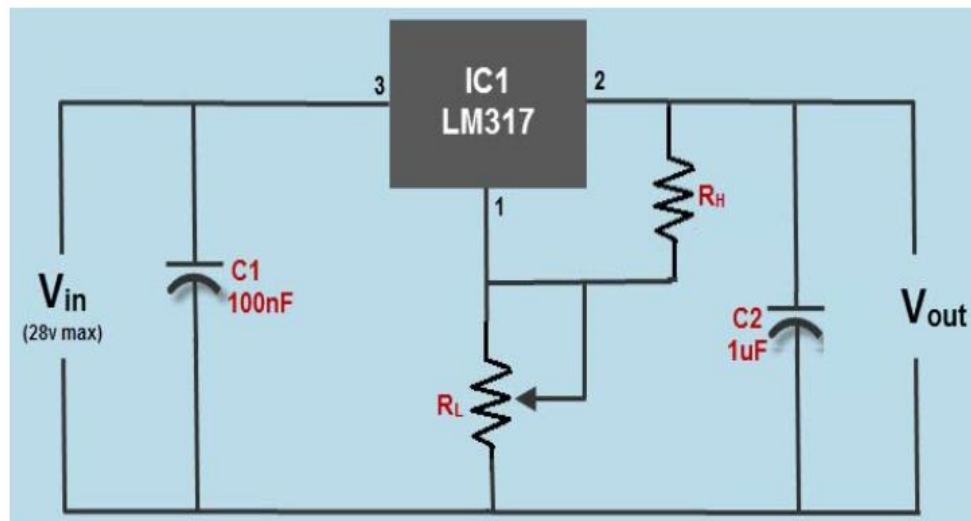

*Figure 2.5 : LM317 Voltage Regulator Circuit*

### 3.Procedure & Discussion

#### 3.1. ZENER DIODE

In this part, the circuit was connected as shown in Figure 3.1.1 below, the applied voltage E was set to (0.1, 0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1, 2, 3, 4, 5, 6)V, then the voltage across the Zener diode was measured as shown in Table1 below.


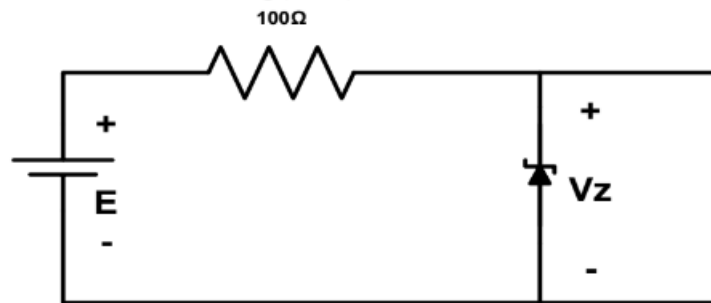


Figure 3.1.1: Zener diode circuit

Set	Measure	Calculate	
E(V)	VZ(V)	VR(V)	I(mA)
0.1	0.1	0	0
0.2	0.2	0	0
0.3	0.27	0.03	0.3
0.4	0.43	0.03	0.3
0.5	0.45	0.05	0.5
0.6	0.57	0.03	0.3
0.7	0.66	0.04	0.4
0.8	0.74	0.06	0.6
0.9	0.89	0.01	0.1
1	0.98	0.02	0.2
2	1.78	0.22	2.2
3	2.48	0.52	5.2
4	2.85	1.15	11.5
5	3.06	1.94	19.4
6	3.19	2.8	28

Table1: values of VZ and VR and I

**Calculation:**

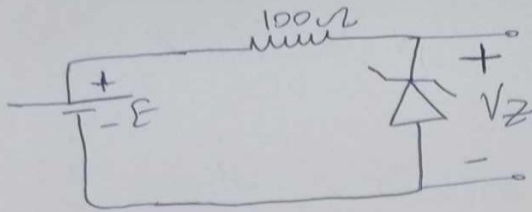

$$-E + V_R + V_Z = 0$$

1] when  $E = 0.1 \text{ V}$

$$-0.1 + V_R + 0.1 = 0$$

$$V_R = 0 \rightarrow I_R = 0$$

2] when  $E = 0.2 \text{ V}$

$$-0.2 + V_R + 0.2 = 0 \rightarrow V_R = 0 \rightarrow I = 0 \text{ mA}$$

3] when  $E = 0.3 \text{ V}$

$$-0.3 + V_R + 0.27 = 0 \rightarrow V_R = 0.03 \text{ V} \rightarrow I = \frac{0.03}{100} = 0.3 \text{ mA}$$

4] when  $E = 0.4 \text{ V}$

$$-0.4 + V_R + 0.43 = 0 \rightarrow V_R = 0.03 \text{ V} \rightarrow I = \frac{0.03}{100} = 0.3 \text{ mA}$$

5] when  $E = 0.5 \text{ V}$

$$-0.5 + V_R + 0.45 = 0 \rightarrow V_R = 0.05 \text{ V} \rightarrow I = \frac{0.05}{100} = 0.5 \text{ mA}$$

6] when  $E = 0.6 \text{ V}$

$$-0.6 + V_R + 0.57 = 0 \rightarrow V_R = 0.03 \text{ V} \rightarrow I = \frac{0.03}{100} = 0.3 \text{ mA}$$

7] when  $E = 0.7 \text{ V}$

$$-0.7 + V_R + 0.66 = 0 \rightarrow V_R = 0.04 \text{ V} \rightarrow I = \frac{0.04}{100} = 0.4 \text{ mA}$$

8] when  $E = 0.8 \text{ V}$

$$-0.8 + V_R + 0.74 = 0 \rightarrow V_R = 0.06 \text{ V} \rightarrow I = 0.6 \text{ mA}$$

9 when  $E = 0.9V$

$$-0.9 + V_R + 0.89 = 0 \rightarrow V_R = 0.01V \rightarrow I = 0.1mA$$

10 when  $E = 1V$

$$-1 + V_R + 0.98 = 0 \rightarrow V_R = 0.02V \rightarrow I = 0.2mA$$

11 when  $E = 2V$

$$-2 + V_R + 1.78 = 0 \rightarrow V_R = 0.22V \rightarrow I = 2.2mA$$

12 when  $E = 3V$

$$-3 + V_R + 2.48 = 0 \rightarrow V_R = 0.52V \rightarrow I = 5.2mA$$

13 when  $E = 4V$

$$-4 + V_R + 2.85 = 0 \rightarrow V_R = 1.15V \rightarrow I = \frac{1.15}{100} = 11.5mA$$

14 when  $E = 5V$

$$-5 + V_R + 3.06 = 0 \rightarrow V_R = 1.94V \rightarrow I = 19.4mA$$

15 when  $E = 6V$

$$-6 + V_R + 3.19 = 0 \rightarrow V_R = 2.81V \rightarrow I = 28mA$$

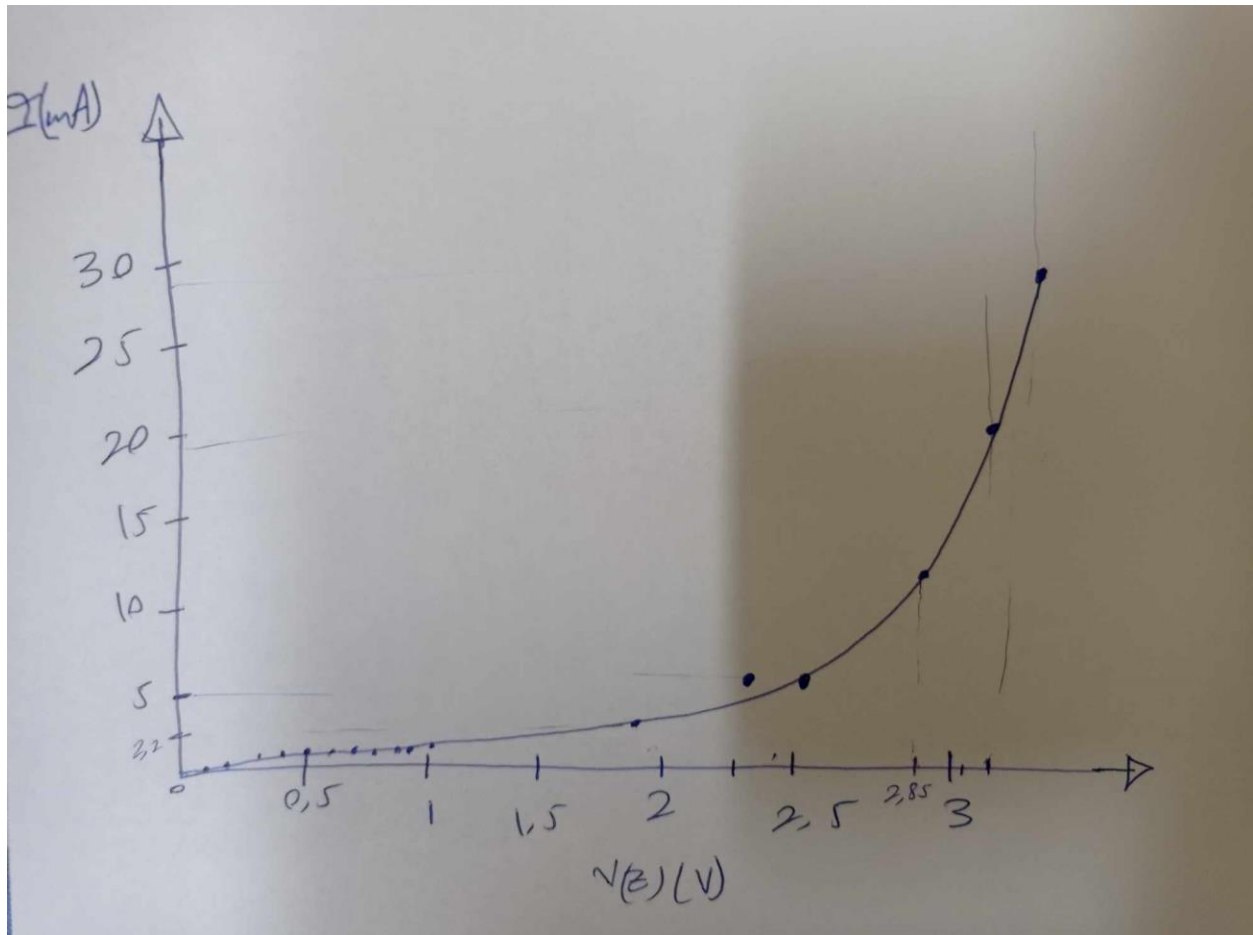


Figure 3.1.2: VZ and I graph

- The current equation  $I = \frac{V_E - V_Z}{R}$ .
- $V_R = I * R$  or  $V_R = V_E - V_Z$ .

Note that in forward bias it allows current, and in reverse bias it blocks current.

A Zener diode functions similarly to a regular diode when forward-biased. However, in reverse-biased mode, a small leakage current flows through the diode. As the reverse voltage increases and reaches the breakdown voltage ( $V_Z$ ), current begins to flow through the diode.

This current reaches a maximum level determined by the series resistor, after which it stabilizes and remains constant across a wide range of applied voltages.

After that the circuit was connected as shown in Figure 3.1.3 below by adding  $R_L$  resistor, and  $E$  was set to (10, 11, 12, 13, 14) V, then the load voltage  $V_L$  was measured as shown in Table2 below.

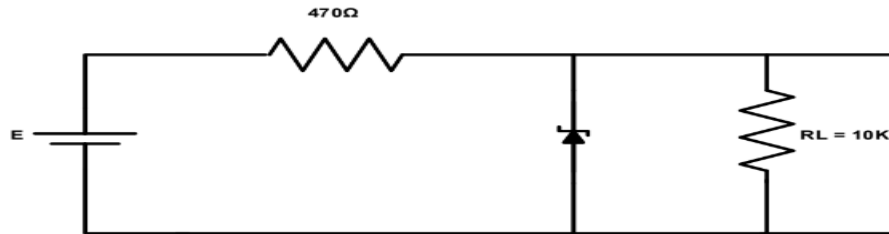


Figure 3.1.3: circuit after adding  $R_L$

E	10	11	12	13	14
$V_L$	2.92v	2.97v	3.02v	3.07v	3.11v

Table2: values of  $V_L$  after adding  $R_L$

Note that  $V_L = V_Z$  (both are in parallel).

then  $E$  was set to 10v and the load voltage  $V_L$  was measured for  $R_L = (8.2K, 6.8K, 4.7K, 2.2k)$ , as shown Table3 below.

$R_L$	8.2K	6.8K	4.7K	2.2K
$V_L$	2.92v	2.92v	2.91v	2.88v

Table3: values of  $V_L$  when  $E=10v$

Note that the zener will conduct the increase of current in  $I$ , while the load current remains constant. The output voltage remains constant irrespective of the changes in the input voltage.

- When the input voltage is constant but the load resistance  $R_L$  decreases. This will cause an increase in load current. The extra current cannot come from the source, because drop in  $R$  will not change as the zener is within its regulating range.

### 3.2.THE VOLTAGE REGULATED POWER SUPPLY

In this part the circuit was connected as shown in Figure 3.2.1 below.

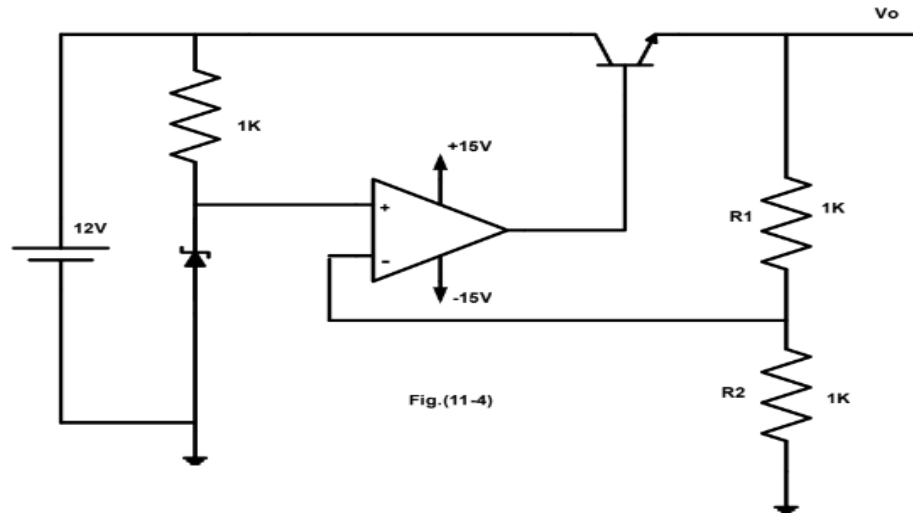


Figure 3.2.1: voltage regulated power supply circuit

Then  $V_o$  was measured  $\rightarrow V_o=5.78v$

After that a 1K load resistor( $R_L$ ) was attached to the output, and  $I_o$  and  $V_o$  was measured, then  $I_o$  and  $V_o$  was measured for  $R_L=(680, 470, 220, 100)\text{ohm}$ , as shown in Table4 below.

$R_L$	open	1k	680K	470K	220K	100	50
$V_o(v)$	5.78	5.79	5.78	5.784	5.7	5.7	5.6
$I_o(mA)$	zero	5.8	8.5	12.3	26.3	57.3	112.6

Table4: values of  $V_o$  and  $I_o$  after adding  $R_L$

Note that the main principle of the voltage regulator is a circuit that creates and maintains a fixed output voltage, irrespective of changes to the input voltage or load conditions. As shown in Table4 the voltage remained constant, while the current changes with the change of the resistor  $R_L$ .

Then  $R_L$  was set back to 1K, and the value of  $R_2$  was changed to 470 ohm then to 2.2K, and the new value of  $V_o$  was measured as shown in Table5 below.

$R_L$	$R_2$	$V_o$
1Kohm	470ohm	8.977v
1Kohm	2.2Kohm	4.19v

Table5: values of  $V_o$  when change the value of  $R_2$

Note that  $V_o = V_z * (1 + r_1/r_2)$  and  $R_1$  is fixed, then changing in  $R_2$  effects the output voltage value.



### 3.3. THREE TERMINAL FIXED VOLTAGE REGULATOR 7805

In this part the circuit was connected as shown in Figure 3.3.1 below.

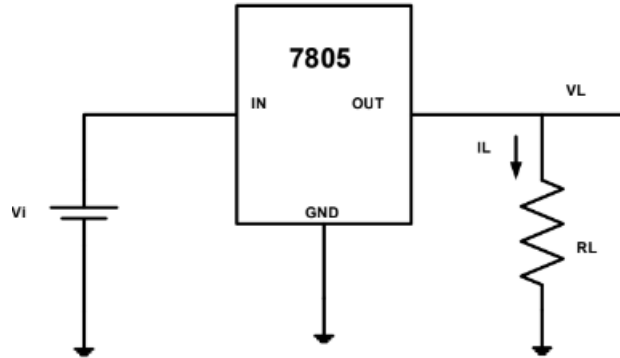


Figure 3.3.1: three terminal fixed voltage regulator circuit

First  $V_i$  was set to 10v, then  $I_L$  and  $V_L$  was measured for each value of  $R_L$  listed in Table6.

$R_L(\text{ohm})$	$V_L(\text{V})$	$I_L(\text{mA})$
25	5.01	194
50	5.01	96.6
100	5.01	49.18
200	4.96	24.8
400	4.78	12.5
600	4.57	8.21
800	4.5	6.1
1000	4.51	4.9

Table6: values of  $V_L$  and  $I_L$  when  $R_L$  changes

Note that the load regulation of the 7805 =  $\Delta V_L / \Delta I_L = 5.01 - 5.01 / 96.6 - 194 = 0$

After that  $R_L$  was set to 100 ohm and  $V_i$  was changed as listed in Table7, then  $V_L$  and  $I_L$  was measured for each value of  $V_i$ .

$V_i(V)$	$V_L(V)$	$I_L(Ma)$
8	5.01	49.4
9	5.01	49.4
10	5.01	49.4
11	5.01	49.4
12	5.01	49.4
13	5.01	49.3
14	5.01	49.3
15	5.01	49.3

Table7: values of  $V_L$  and  $I_L$  when  $R_L=100$  ohm

Note that the values of  $V_L$  and  $I_L$  still constant and not changed when we changed the  $V_i$  and set  $R_L$  to 100.

Note that the line regulation of the 7805 =  $\Delta V_L / \Delta V_i = 5.01 - 5.01 / 15 - 8 = 0$

### 3.4. THE LM317 ADJUSTABLE VOLTAGE REGULATOR

In this part the circuit was connected as shown in Figure 3.4.1 below

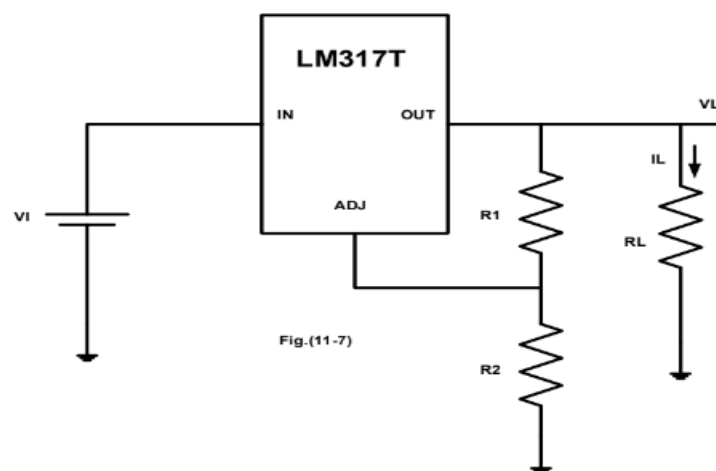


Figure 3.4.1: LM317 adjustable voltage regulator circuit

First  $V_i$  was set to 10v,  $R_1 = 100 \text{ ohm}$ ,  $R_L$  was changed as shown in Table8 below, then  $V_L$  and  $I_L$  was measured for each value of  $R_2$ .

$R_2(\text{ohm})$	$V_L(\text{V})$	$I_L(\text{mA})$
0	1.25	1.538
100	2.53	2.5
200	3.8	3.8
300	5.05	5.02
500	7.04	7.5

Table8: values of  $V_L$  and  $I_L$  when  $V_i = 10\text{v}$

The output voltage of the LM317T is determined by ratio of the two feedback resistors  $R_1$  and  $R_2$  which form a potential divider network across the output terminal as shown below.

$$V_o = 1.25 * (1 + (R_2/R_1))$$

Note that increasing the  $R_2$  values cause increasing in output voltage.

After that  $R_L$  was set to 1K,  $R_1 = 100 \text{ ohm}$ ,  $R_2 = 220 \text{ ohm}$ , and  $V_i$  was changed as shown in Table9

Then  $V_L$  and  $I_L$  was measured for each value of  $V_i$ .

$V_i(\text{V})$	$V_L(\text{V})$	$I_L(\text{mA})$
10	4.04	4.01
12	4.04	4.018
14	4.04	4.018
15	4.04	4.019
16	4.04	4.018
17	4.04	4.019

Table9: values of  $V_L$  and  $I_L$  when  $R_L = 1\text{K}$

Note that changing the input voltage has no effect on the output voltage.

Line regulation for the LM317 =  $\Delta V_L / \Delta V_i = 4.04 - 4.04 / 17 - 10 = 0$

After that  $V_i$  was set to 10v,  $R_1=100$  ohm,  $R_2=220$  ohm, then  $V_L$  and  $I_L$  was measured for each value of  $R_L$  listed in Table10 below.

$R_L$ (ohm)	$V_L$ (V)	$I_L$ (mA)
100	3.96	39
200	3.9	18.87
400	3.89	9.7
500	3.9	7.8
600	3.908	6.52
700	3.92	5.6
1000	3.93	3.93

Table10: values of  $V_L$  and  $I_L$

Note that the output voltage did not change, that means the load resistor has no effect on the output resistor. However, the output current is changed because  $I_L = V_L / R_L$ .

#### **4.Conclusion**

In conclusion, after we finished this experiment we became know the use of Zener diode as voltage regulator, and how does the voltage regulator work, and we became know the I-V characteristic of zener diode, also the difference between fixed and adjustable voltage regulator, and the meaning of load and line regulation and what do we mean by them.

## 5. References

[1] <https://uk.rs-online.com/web/content/discovery/ideas-and-advice/zener-diodes-guide>

(accessed date 8/28/2023)

[2] <https://uk.rs-online.com/web/content/discovery/ideas-and-advice/zener-diodes-guide>

(accessed date 8/29/2023)

[3] <https://uk.rs-online.com/web/content/discovery/ideas-and-advice/zener-diodes-guide>

(accessed date 8/29/2023)

[4] <https://uk.rs-online.com/web/content/discovery/ideas-and-advice/zener-diodes-guide>

(accessed date 8/30/2023)

[5] <https://uk.rs-online.com/web/content/discovery/ideas-and-advice/zener-diodes-guide>

(accessed date 8/30/2023)

## 6. Appendices

### Experiment #11

ENEE2103

### Zener Diodes and Voltage Regulators

#### Objectives:

1. To construct the I.V characteristic of a zener diode.
2. To demonstrate the use of zener diode as voltage regulator.
3. To examine the operation of the voltage regulator.

#### Pre-lab Work:

You have to apply PSPICE simulation to all practical circuits shown in the procedure below, and you have to do all necessary calculation you will need in the lab.

#### Procedure:

##### 1. ZENER DIODE.

Connect the circuit shown in Fig(11-2).


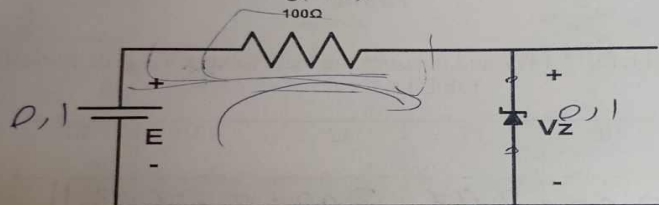


Fig. (11-2)

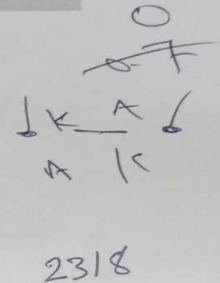

Set the applied voltage E to (0.1, 0.5, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)V. For each value of E, measure the voltage across the zener diode and calculate the current through the zener diode. (Fill in Table 11.2)

Table 11.2

Set E(V)	Measure V <sub>Z</sub> (V)	Calculate	
		V <sub>R</sub> (V)	I(m A)
0.1	0.21		
0.2	0.22		
0.3	0.27		
0.4	0.43		
0.5	0.45		
0.6	0.57		
0.7	0.66		
0.8	0.74		
0.9	0.89		
1	0.98		
2	1.78		
3	2.48		
4	2.85		
5	3.06		
6	3.19		

1. Using the results obtained in steps 3 and 6 constitute a graph of the characteristic of the zener diode.
2. Connect the circuit shown in Fig(11-3).

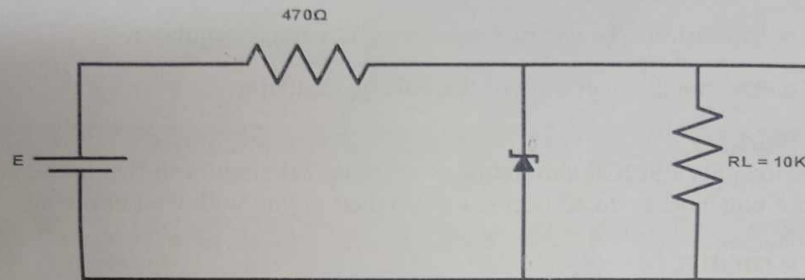


Fig.(11-3)

1. Set E to (10,11,12,13,14)V and measure the load voltage  $V_L$ . (Fill Table 11.3)

E	10	11	12	13	14
$V_L$	2,92	2,97	3,02	3,07	3,11

3. With E set to 10V measure the load voltage  $V_L$  for  $R_L = (8.2K, 6.8K, 4.7K, 2.2K)$  and Fill in Table 11.4

Table 11.4

$R_L$	8.2k	6.8k	4.7 k	2.2k
$V_L$	2,92	2,92	2,91	2,88



**II. THE VOLTAGE REGULATED POWER SUPPLY.**

1. connect the circuit of Fig.(11-4).

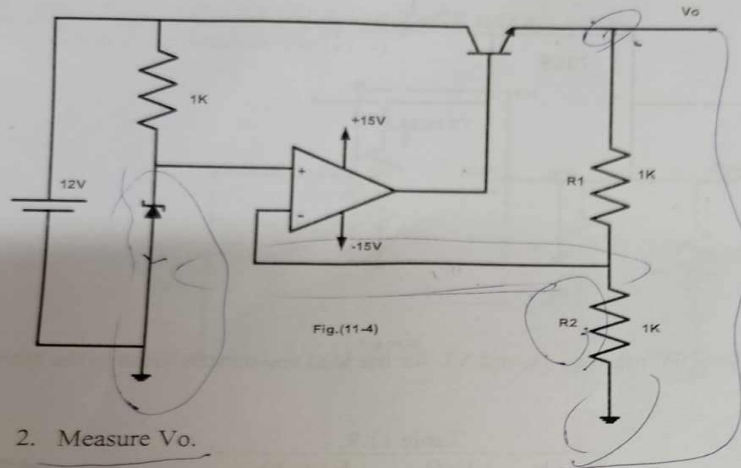
2. Measure  $V_o$ .3. Attach a 1k load resistor to the output. Measure  $I_o$  and  $V_o$ .4. Repeat step 3 for load resistance  $R_L = (680, 470, 220, 100)$  ohm.

Table 11.5

$R_L$	open	1k $\Omega$	680 $\Omega$	470 $\Omega$	220 $\Omega$	100 $\Omega$	50 $\Omega$
$V_o$	<del>10.56</del>	<del>5.31</del>	<del>70mV</del>	<del>52.8mV</del>	<del>28mV</del>	<del>13.6mV</del>	<del>7mV</del>
$I_o$	<del>Zero</del>	<del>6.8mA</del>	<del>7.0mA</del>	<del>7.8mA</del>	<del>8.4mA</del>	<del>87.8mA</del>	<del>89.3mA</del>

5. Set  $R_L$  back to 1K. Change the value of  $R_2$  to 470 ohm.

What is the new output voltage.

6. Change  $R_2$  to 2.2k. What is the output voltage now

Table 11.6

$R_L$	$R_2$	$V_o$
1k $\Omega$	470 $\Omega$	<del>125.9mV</del>
1k $\Omega$	2.2k $\Omega$	<del>137.5mV</del>

## II. THREE TERMINAL FIXED VOLTAGE REGULATOR 7805.

1. Connect the circuit of Fig (11.6).

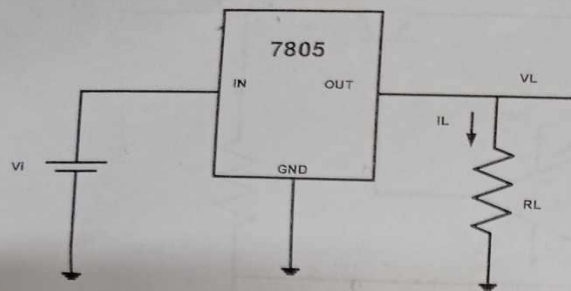


Fig.(11-6)

2. With  $V_i=10V$  measure  $I_L$  and  $V_L$  for the load resistances listed in the table 11.9.

Table 11.9.

$R_L(\Omega)$	$V_L(V)$	$I_L(mA)$
25	5.01	<del>11.9</del> 19.4
50	5.01	96.6
100	5.01	49.18
200	4.96	24.8
400	4.78	<del>12.5</del> 12.5
600	4.57	8.21
800	4.5	6.1
1000	4.51	4.9

3. Using the results of table 9.2, determine the load regulation of the 7805. knowing that load regulation =  $\Delta V_L / \Delta I_L$
4. Set  $R_L=100\text{ ohm}$ , adjust the input voltage  $V_i$  as listed in table 11.10. Measure  $V_L$  and  $I_L$  for each input voltage in the table.


Table 11.10

$V_i(V)$	$V_L(V)$	$I_L(mA)$
8	5.01	49.4
9	5.01	49.4
10	5	49.4
11		
12		
13		
14		
15		

Using the results of table 11.10 , determine the line regulation of the 7805 .  
 $\text{line regulation} = \Delta V_L / \Delta V_i$

### III. THE LM317 ADJUSTABLE VOLTAGE REGULATOR

1. Connect the circuit of Fig.(11.7).

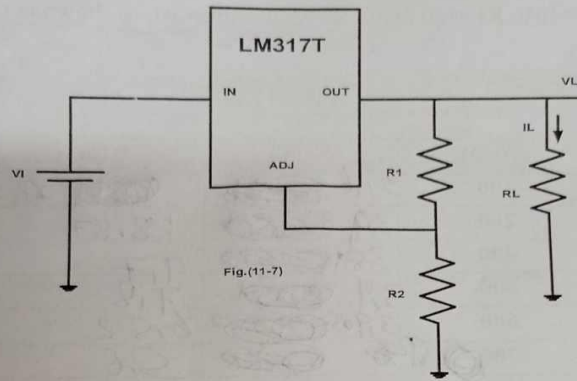

2. With  $V_i=10\text{V}$ ,  $R_1=100\Omega$ ,  $R_L=1\text{k}$  , adjust  $R_2$  as shown in table 11.11.

Table 11.11

$R_2(\Omega)$	$V_L(\text{V})$	$I_L(\text{mA})$	$V_L(\text{V})$	$I_L(\text{mA})$
0	1.27	1.538	1.27	1.538
100	2.53	2.5	2.53	2.5
200	3.8	3.8	3.8	3.8
300	5.05	5.02	5.05	5.02
500	7.04	7.15	7.04	7.15

3. Measure and record  $V_L, I_L$  for each  $R$  value.
4. With  $R_L = 1\text{k}$  ,  $R_1=100 \text{ ohm}$  ,  $R_2=220$  , adjust  $V_i$  as listed in table 11.12.

Table 11.12

$V_i(\text{V})$	$V_L(\text{V})$	$I_L(\text{mA})$
10	4.04	4.01
12	4.0	4.018
14		4.018
15		4.019
16		4.018
17		4.019

5. Measure and record the load voltage and current for each input voltage value.
6. Using your results, calculate the line regulation for the LM317T voltage regulator.
7. With  $V_i=10V$ ,  $R_1=100\ \Omega$ ,  $R_2=220$ , adjust  $R_L$  as shown in table 11.13.

Table 11.13

$R_L(\Omega)$	$V_L(V)$	$I_L(mA)$
100	3.16	39
200	3.1	18.87
400	3.89	9.7
500	3.9	7.18
600	3.908	6.52
700	3.9	5.6
1000	3.93	3.93

8. Measure and record  $V_L, I_L$  for each  $R_L$  value.

$1k \rightarrow$  بنیادی - زمینی  
 $2k \rightarrow$  زمینی - اح - اح - اح  
 $10k \rightarrow$  زمینی - بنیادی - بنیادی  
 $170 \Omega \rightarrow$  زمینی - بنیادی - بنیادی

