



Faculty Of Engineering and Technology
Electrical and Computer Engineering Department
CIRCUITS AND ELECTRONICS LABORATORY

ENEE 2103

Experiment #: 6

Diode Characteristic and Applications

Prepared by: Rahaf Naser 1201319

Instructor: Dr. Mahran Quraan

Teacher assistant: Eng. Rafah Rahhal

Date: 8/11/2023

Table of contents

1. DIODE CHARACTERISTICS.....	1
2. RECTIFICATION.....	5
2.1. Half-wave rectification.....	5
2.2. Full-wave rectification.....	9
3. OTHER APPLICATIONS.....	12
3.1. Clipping.....	12
3.2. Clamping.....	18

Table of Figures

Figure 1.1: RD series circuit implementation.....	1
Figure 1.2: RD series circuit simulation result.....	1
Figure 1.3: RD series circuit implementation– When reverse the diode.....	3
Fig 2.1.1: Half-Wave Rectification circuit implementation	5
Fig 2.1.2 : Half-Wave Rectification circuit implementation.....	5
Fig 2.1.3 :Half-Wave Rectification circuit implementation - When Reverse the diode.....	6
Fig 2.1.4 : Half-Wave Rectification circuit implementation - Reverse the diode-wave form.....	6
Fig 2.1.5 : Half-Wave Rectification circuit implementation after adding 2.2 μ F capacitor.....	7
Fig 2.1.6 : Half-Wave Rectification circuit after adding 2.2 μ F capacitor -wave form.....	7
Fig 2.1.7:: Half-Wave Rectification circuit after adding 47 μ F capacitor.....	8
Fig 2.1.8:: Half-Wave Rectification circuit after adding 47 μ F capacitor-wave form.....	8
Figure 2.2.1: Full-Wave Rectification.....	9
Figure 2.2.2: Full-Wave Rectification wave form.....	10
Figure 2.2.3: Full-Wave Rectification when adding the capacitor of 2.2 μ F voltage response....	10
Figure 3.1.1: Clipping circuit implementation when dc =0v.....	11
Figure 3.1.2: Clipping circuit implementation-wave form when dc = 0v.....	12
Figure 3.1.3: Clipping circuit implementation when dc =1.5v.....	12
Figure 3.1.4: Clipping circuit implementation -wave form when dc = 1.5v.....	14
Figure 3.1.5: Clipping circuit implementation when dc =4v.....	14
Figure 3.1.6: Clipping circuit implementation -wave form when dc = 4v.....	16
Figure 3.2.1: Clamping circuit implementation when dc=0v.....	16
Figure 3.2.2: Clamping circuit implementation- wave form when dc = 0v.....	18
Figure 3.2.3: Clamping circuit implementation when dc=1.5v.....	18
Figure 3.2.4: Clamping circuit implementation- wave form when dc = 1.5v.....	19
Figure 3.2.5: Clamping circuit implementation when dc=4v.....	21
Figure 3.2.6: Clamping circuit implementation- wave form when dc = 4v.....	21

List of Tables

Table1: Diode characteristics table.....	2
Table2: Reverse diode characteristic table.....	4

1. DIODE CHARACTERISTICS

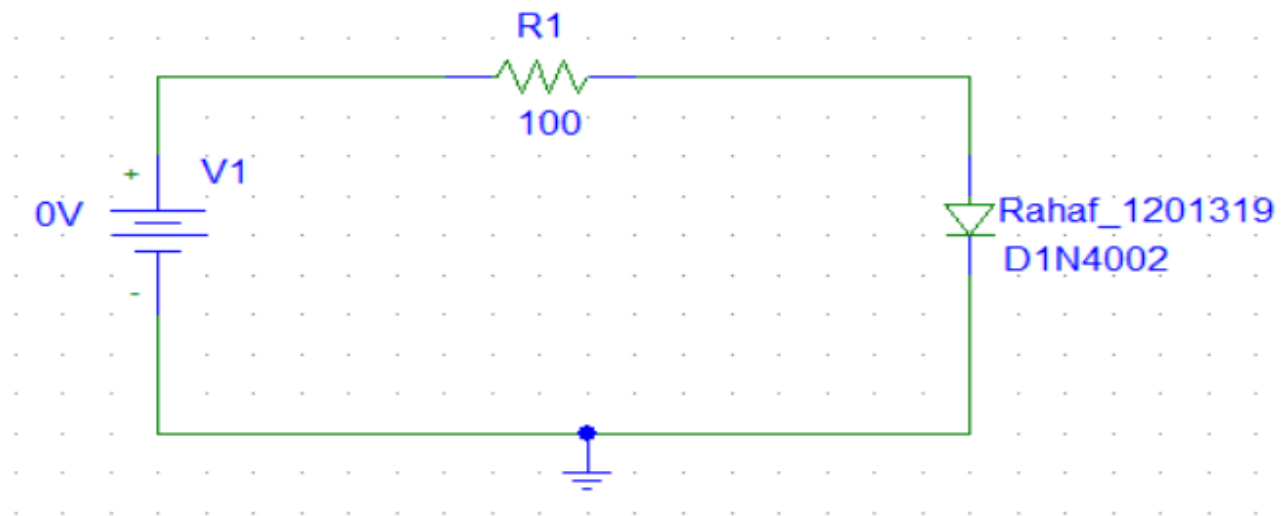


Figure 1.1: RD series circuit implementation

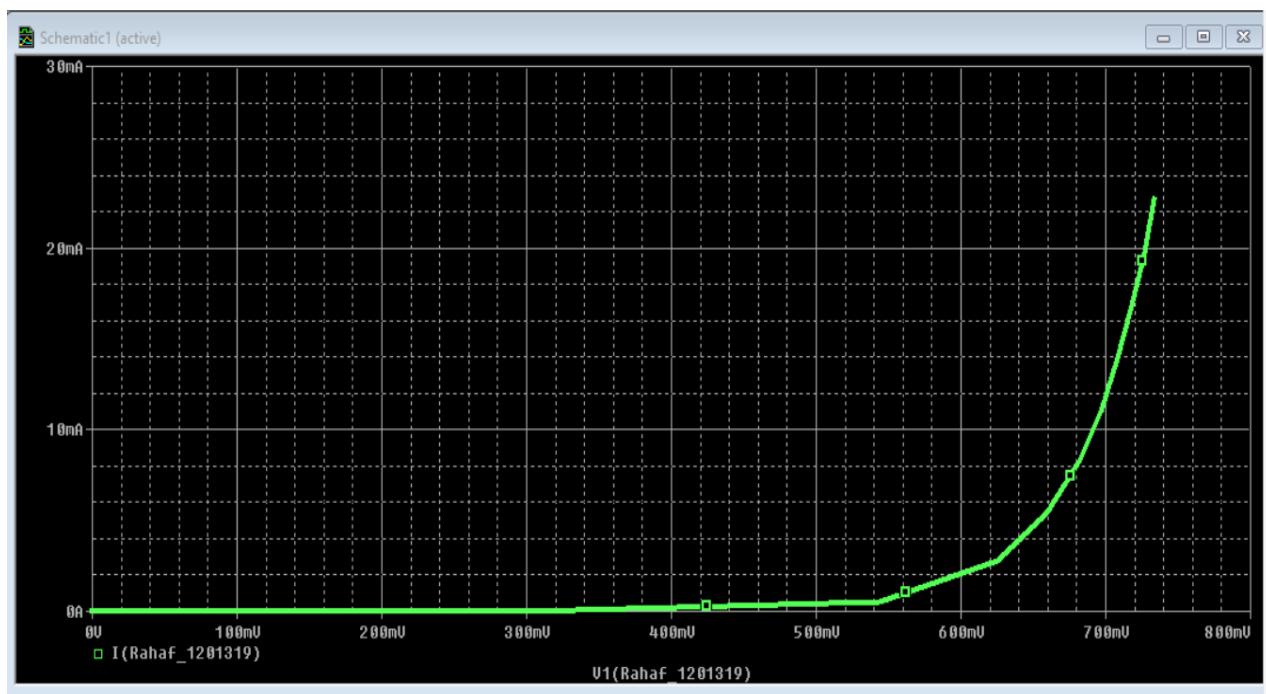


Figure 1.2: RD series circuit simulation result

VS	VR	VD	ID
0	0	0	0
0.2	0	0.2	0
0.4	0	0.4	0
0.6	0.009	0.591	0.00009
0.8	0.137	0.663	0.001
1	0.315	0.685	0.003
1.5	0.791	0.709	0.008
2	1.278	0.722	0.013
2.5	1.769	0.731	0.018
3	2.262	0.738	0.023

Table 1: Diode characteristics table

In this case $V_R = V_S - V_D$

$$I_D = V_R * R$$

Using KVL:

$$\rightarrow \text{when } V_S = 0.2 : -0.2 + 0 + V_D = 0 \rightarrow V_D = 0.2\text{v}$$

$$I_D = V_R / R = 0 / 100 = 0$$

$$\rightarrow \text{when } V_S = 0.4 : -0.4 + 0 + V_D = 0 \rightarrow V_D = 0.4\text{v}$$

$$I_D = V_R / R = 0 / 100 = 0$$

$$\rightarrow \text{when } V_S = 0.6 : -0.6 + 0.009 + V_D = 0 \rightarrow V_D = 0.591\text{v}$$

$$I_D = V_R / R = 0.009 / 100 = 0.00009\text{A}$$

->when $V_S = 0.8$: $-0.8 + 0.137 + V_D = 0 \rightarrow V_D = 0.663\text{v}$

$I_D = V_R/R = 0.137/100 = 0.001\text{A}$

->when $V_S = 1$: $-1 + 0.315 + V_D = 0 \rightarrow V_D = 0.685\text{v}$

$I_D = V_R/R = 0.315/100 = 0.0032\text{A}$

->when $V_S = 1.5$: $-1.5 + 0.791 + V_D = 0 \rightarrow V_D = 0.709\text{v}$

$I_D = V_R/R = 0.791/100 = 0.008\text{A}$

->when $V_S = 2$: $-2 + 1.278 + V_D = 0 \rightarrow V_D = 0.722\text{v}$

$I_D = V_R/R = 1.278/100 = 0.013\text{A}$

->when $V_S = 2.5$: $-2.5 + 1.769 + V_D = 0 \rightarrow V_D = 0.731\text{v}$

$I_D = V_R/R = 1.769/100 = 0.018\text{A}$

->when $V_S = 3$: $-3 + 2.262 + V_D = 0 \rightarrow V_D = 0.738\text{v}$

$I_D = V_R/R = 2.262/100 = 0.023\text{A}$

Reverse the diode:

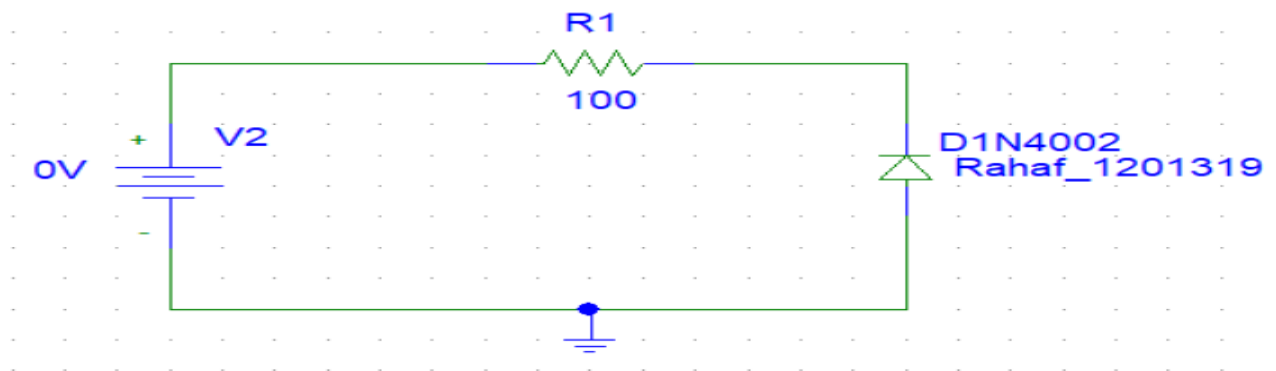


Figure 1.3: RD series circuit implementation– When reverse the diode

The diode will behave as an open circuit after being reversed since the voltage across the anode is greater than the voltage across the cathode. So, $V_D = V_S$ and $I_D = 0$ $V_R = 0$

VS	VR	VD	ID
0	0	0	0
0.2	0	0.2	0
0.4	0	0.4	0
0.6	0	0.6	0
0.8	0	0.8	0
1	0	1	0
1.5	0	1.5	0
2	0	2	0
2.5	0	2.5	0
3	0	3	0

Table 2: Reverse diode characteristic table

2. RECTIFICATION

2.1. Half-wave rectification

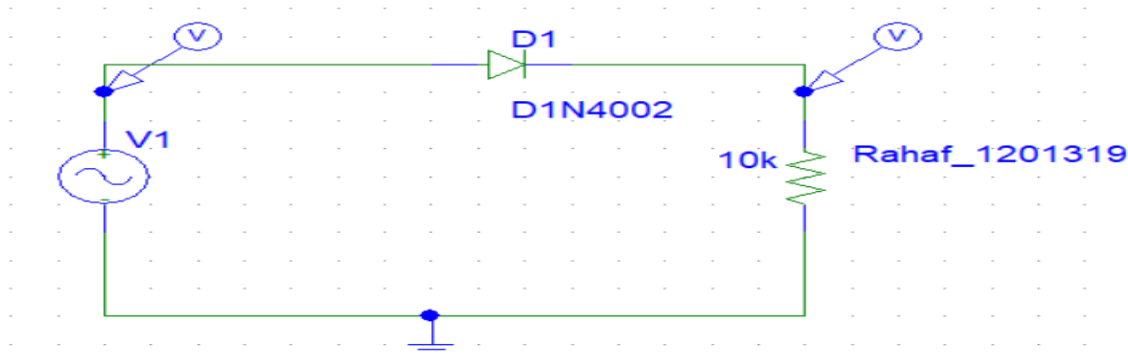


Fig 2.1.1: Half-Wave Rectification circuit implementation

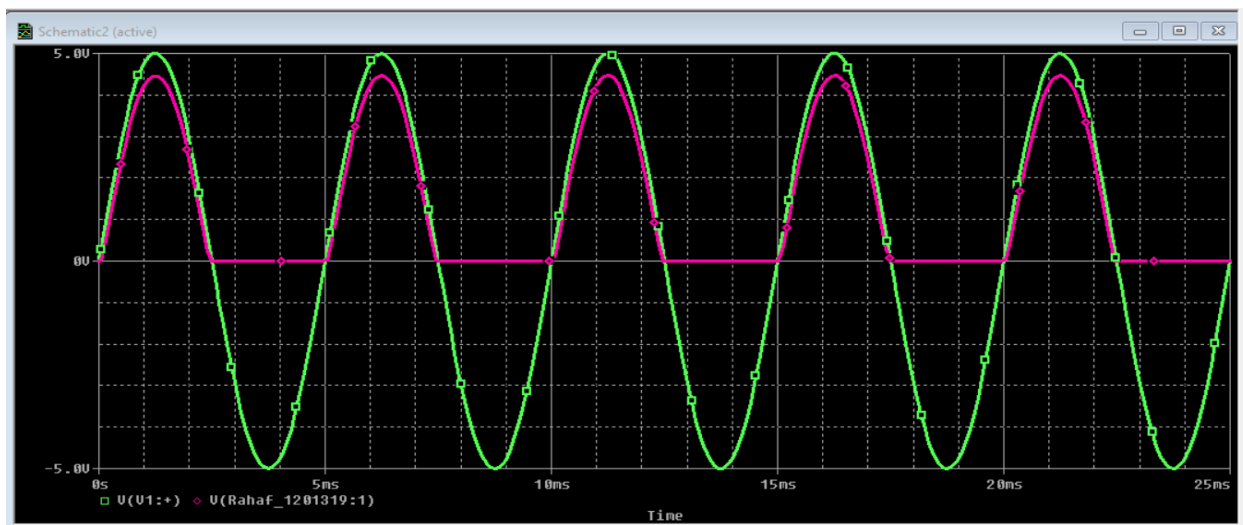


Fig 2.1.2 : Half-Wave Rectification circuit implementation

➤ Period T and dc value

$$\rightarrow T = 1 / f = 1/200 = 5 \text{ ms}$$

$$\rightarrow \text{peak value } V_{\text{peak}} (\text{experimentally}) = 4.4683\text{v}$$

$$\rightarrow \text{dc value} = V_{\text{peak}} / \pi = 1.42305\text{v}$$

When reverse the diode:

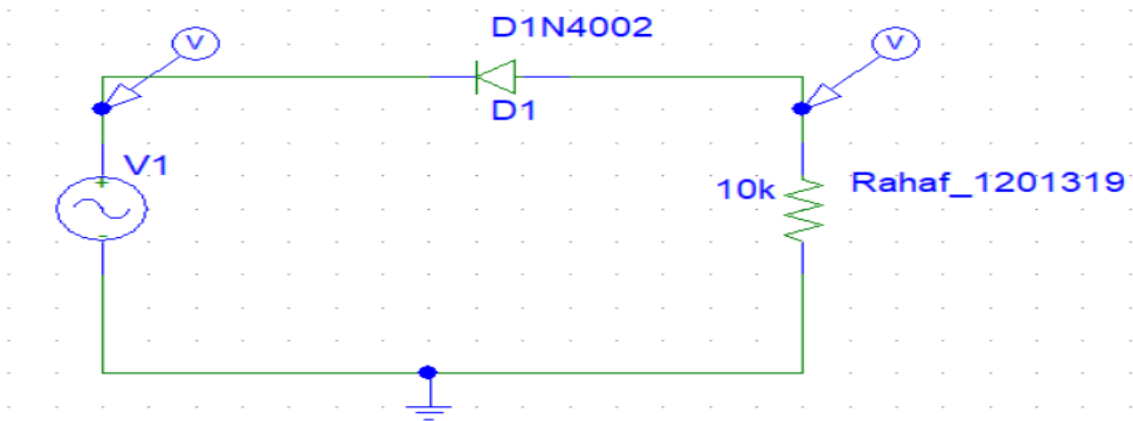


Fig 2.1.3 :Half-Wave Rectification circuit implementation - When Reverse the diode

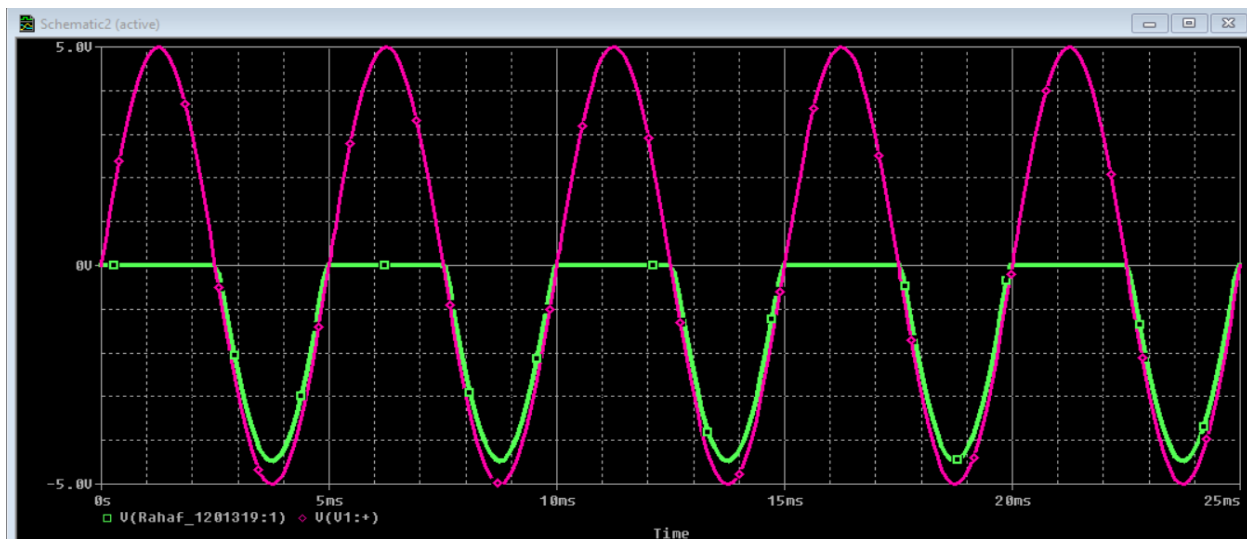


Fig 2.1.4 : Half-Wave Rectification circuit implementation - When Reverse the diode-wave form

➤ Period T and dc value

$$\rightarrow T = 1 / f = 1/200 = 5 \text{ ms}$$

$$\rightarrow \text{peak value } V_{\text{peak}} (\text{experimentally}) = - 4.4516\text{v}$$

$$\rightarrow \text{dc value} = V_{\text{peak}} / \pi = - 1.4177\text{v}$$

->When Adding $C = 2.2 \mu\text{F}$:

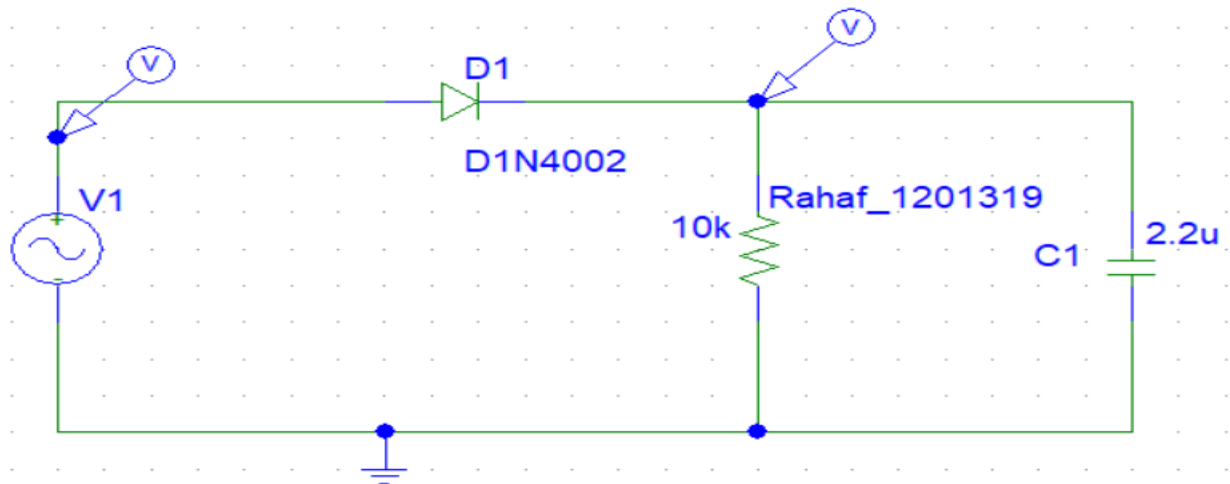


Fig 2.1.5 : Half-Wave Rectification circuit implementation after adding $2.2 \mu\text{F}$ capacitor

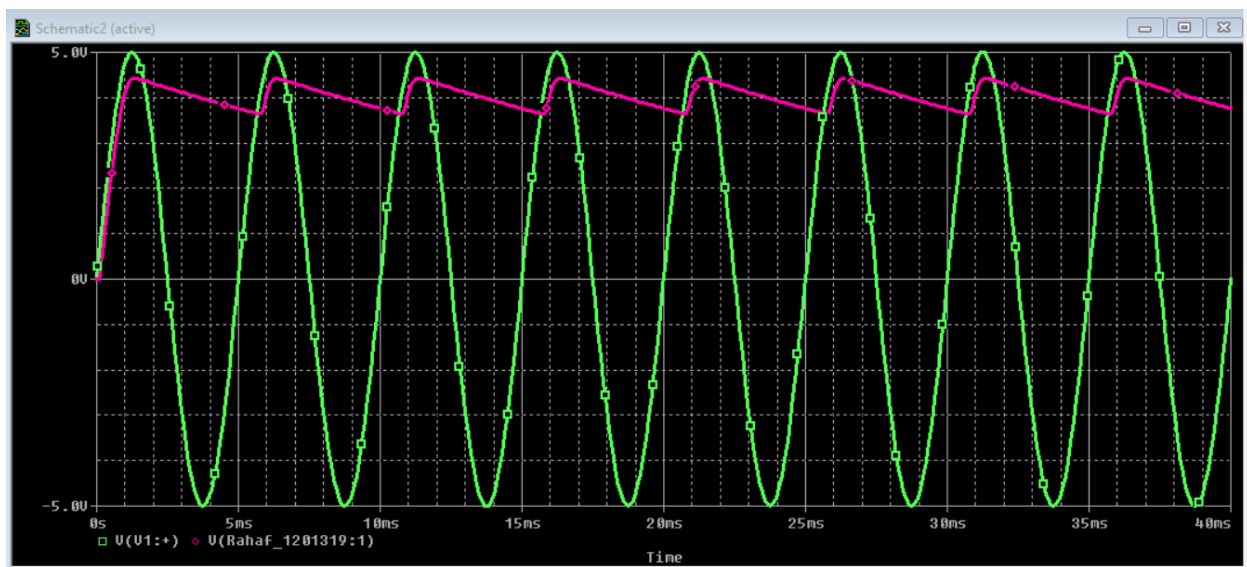


Fig 2.1.6 : Half-Wave Rectification circuit after adding $2.2 \mu\text{F}$ capacitor -wave form

▪ dc value:

-> peak value V_{peak} (experimentally) = 4.4273 v

-> $V_{\text{LR-pp}} = 4.4273 - 3.6310 = 0.7963\text{v}$

-> dc value = $V_{\text{avg}} = V_{\text{peak}} - 0.5 V_{\text{L-pp}} = 4.4273 - 0.5 * 0.7962 = 4.02915 \text{ v}$

Ripple factor:

$$r\% \text{ (experimentally)} = ((V_{LR} - PP) / (2\sqrt{3}) / V_{avg}) * 100\% = 5.7052\%$$

$$r\% \text{ (theoretically)} = (1 / \sqrt{3} [2f_0 RC - 1]) * 100\%$$

$$= (1 / ((3^{0.5}) ((2 * 200 * 10 * 100 * 2.2 * 10^{-6}) - 1))) * 100\% = 7.4019$$

->Using C = 47 μ F :

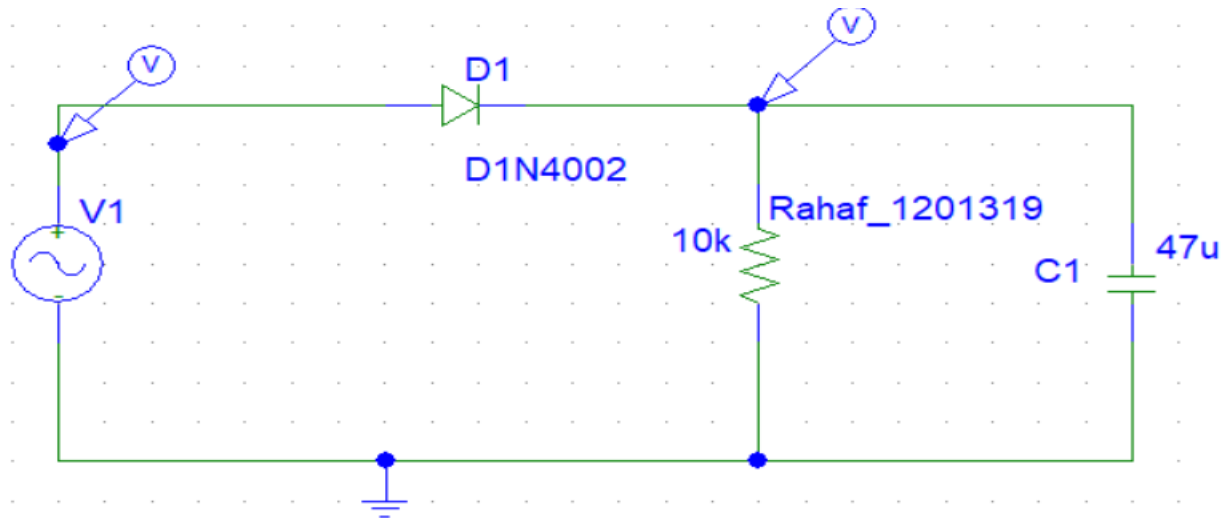


Fig 2.1.7:: Half-Wave Rectification circuit after adding 47 μ F capacitor

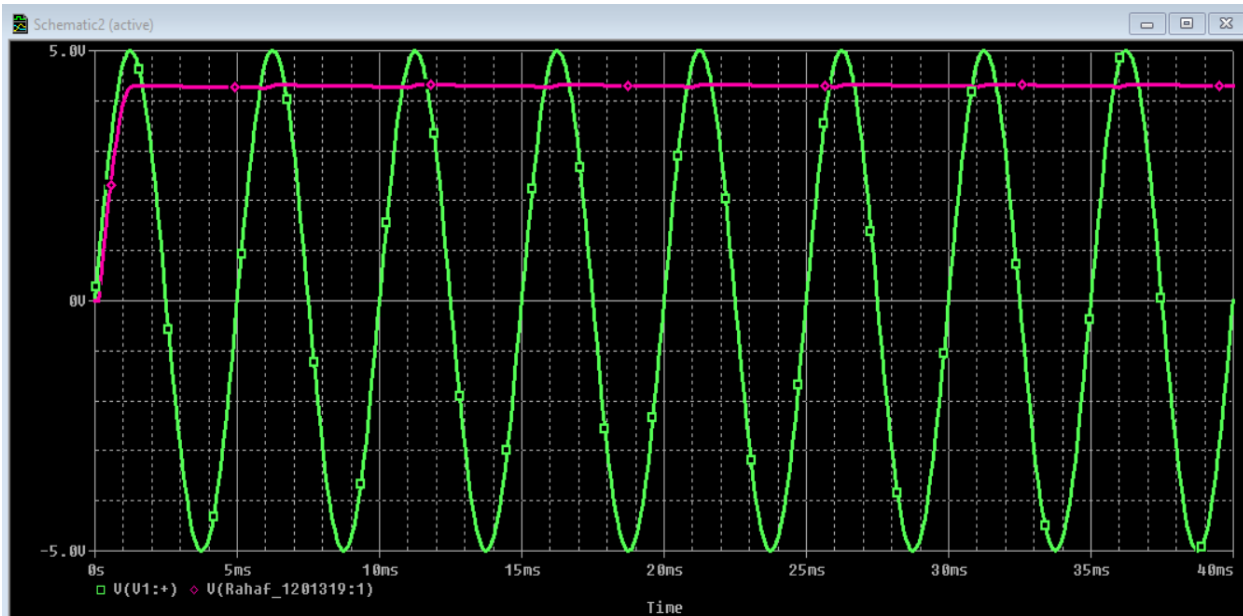


Fig 2.1.8:: Half-Wave Rectification circuit after adding 47 μ F capacitor-wave form

dc value:

-> peak value V_{peak} (experimentally) = 4.3234 v

-> $V_{\text{LR-pp}} = 4.3234 - 4.2810 = 0.0424\text{v}$

-> dc value = $V_{\text{avg}} = V_{\text{peak}} - 0.5 V_{\text{L,p-p}} = 4.3234 - 0.5 * 0.0424 = 4.3022\text{ v}$

Ripple factor:

$r\%$ (experimentally) = $\left(\frac{(V_{\text{LR-PP}}/2\sqrt{3})}{V_{\text{avg}}}\right) * 100\% = 0.2845\%$

$r\%$ (theoretically) = $\left(\frac{1}{\sqrt{3}[2f_0RC-1]}\right) * 100\%$

= $1/(\sqrt{3}[2 * 200 * 10 * 1000 * 47 * 10^{-6}]) * 100\% = 0.3087\%$

-> We note that when the capacitor value is increased, the ripple factor decreases and the value of the mean voltage increases.

2.2. Full-wave rectification

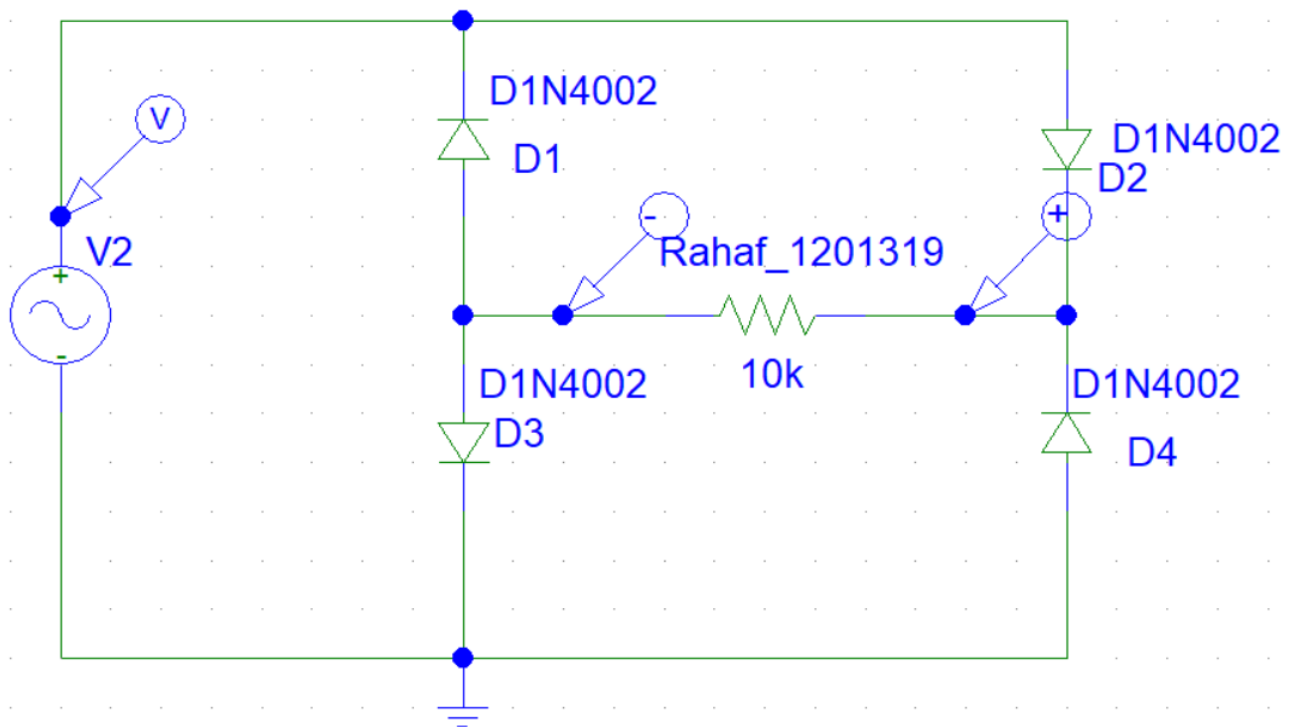


Figure 2.2.1: Full-Wave Rectification

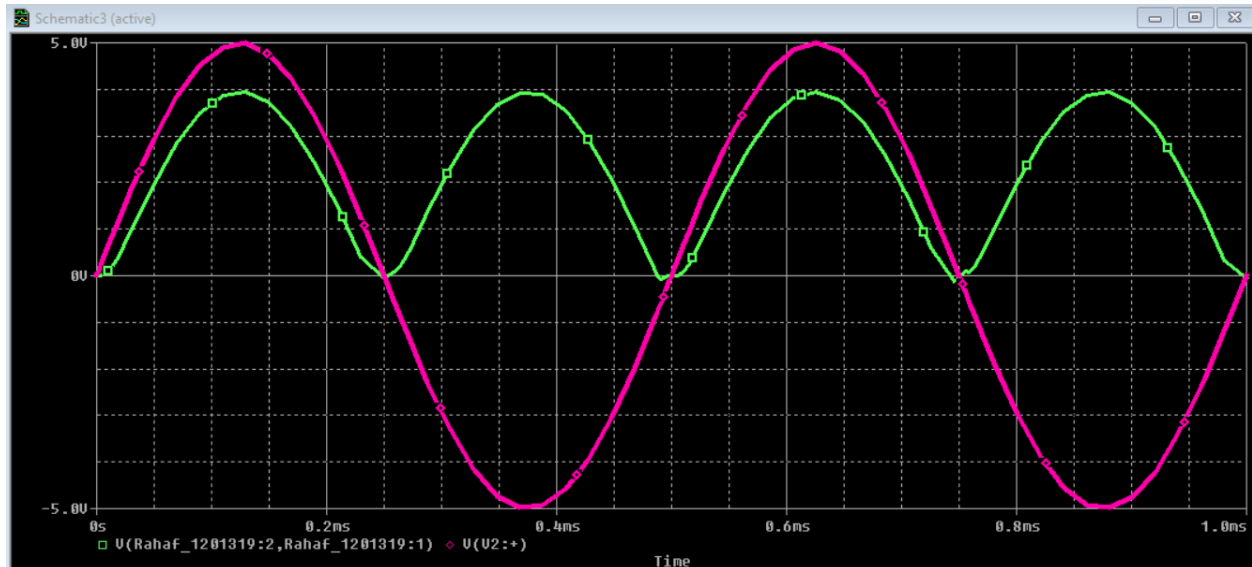


Figure 2.2.2: Full-Wave Rectification wave form

➤ Period T and dc value

-> $T = 1 / f = 1/2000 = 0.5 \text{ ms}$

-> peak value $V_{\text{peak}}(\text{experimentally}) = 3.9355\text{v}$

-> dc value $= V_{\text{peak}} / \pi = 1.2533\text{v}$

When Adding $C = 2.2 \mu\text{F}$:

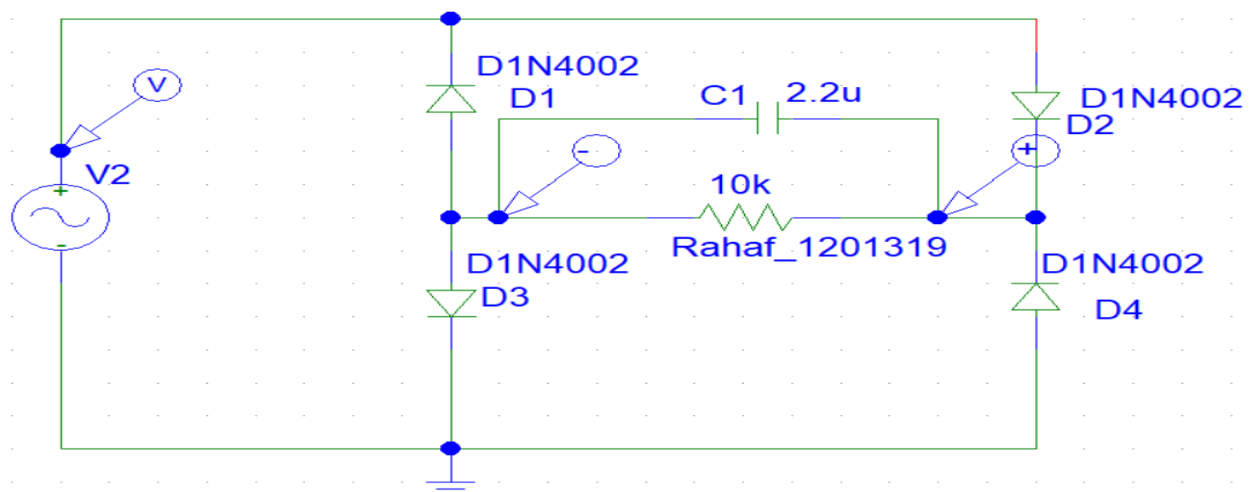


Figure 2.2.3: Full-Wave Rectification when adding the capacitor of $2.2 \mu\text{F}$ voltage response

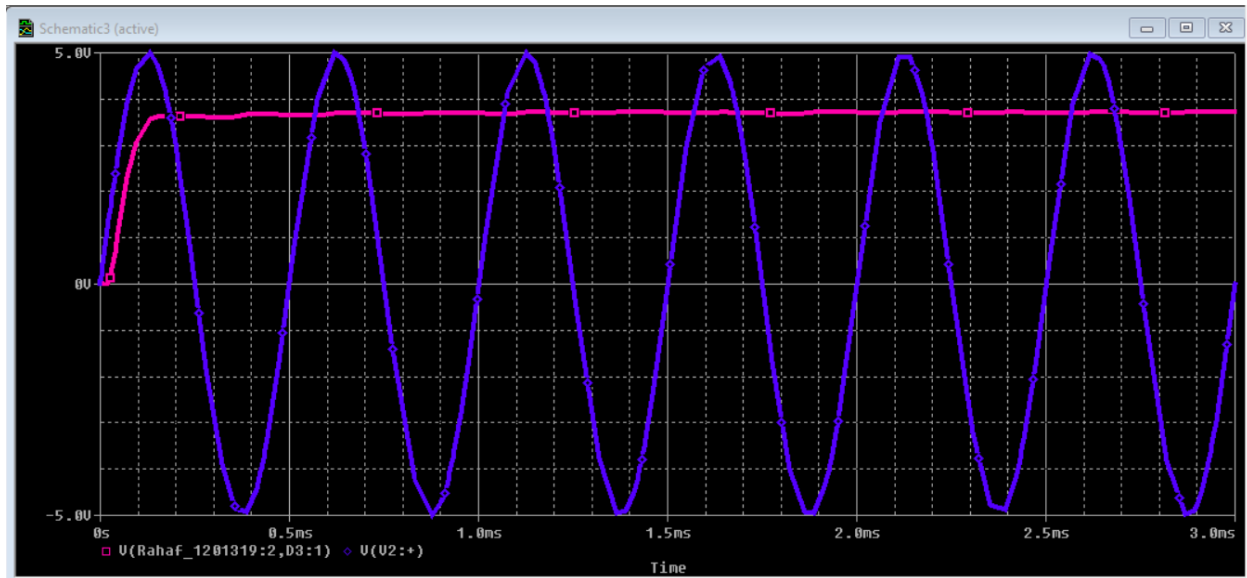


Figure 2.2.4: Full-Wave Rectification when adding the capacitor of 2.2 μF wave form

dc value:

-> peak value V_{peak} (experimentally) = 3.7431v

-> $V_{\text{LR-pp}} = 3.7431 - 3.7114 = 0.0317\text{v}$

-> dc value = $V_{\text{avg}} = V_{\text{peak}} - 0.5 V_{\text{L,p-p}} = 3.7431 - 0.5 * 0.0317 = 3.7272\text{v}$

ripple factor:

$r\%$ (experimentally) = $\left(\frac{(V_{\text{LR-PP}})/2\sqrt{3}}{V_{\text{avg}}} \right) * 100\% = 0.2455\%$

$r\%$ (theoretically) = $\left(\frac{1}{\sqrt{3} [4f_0RC - 1]} \right) * 100\%$

= $\left(\frac{1}{\sqrt{3} [4 * 2000 * 10 * 1000 * 2.2 * 10^{-6}]} \right) * 100\% = 0.3299\%$

3. OTHER APPLICATIONS

3.1. Clipping

When $dc=0v$

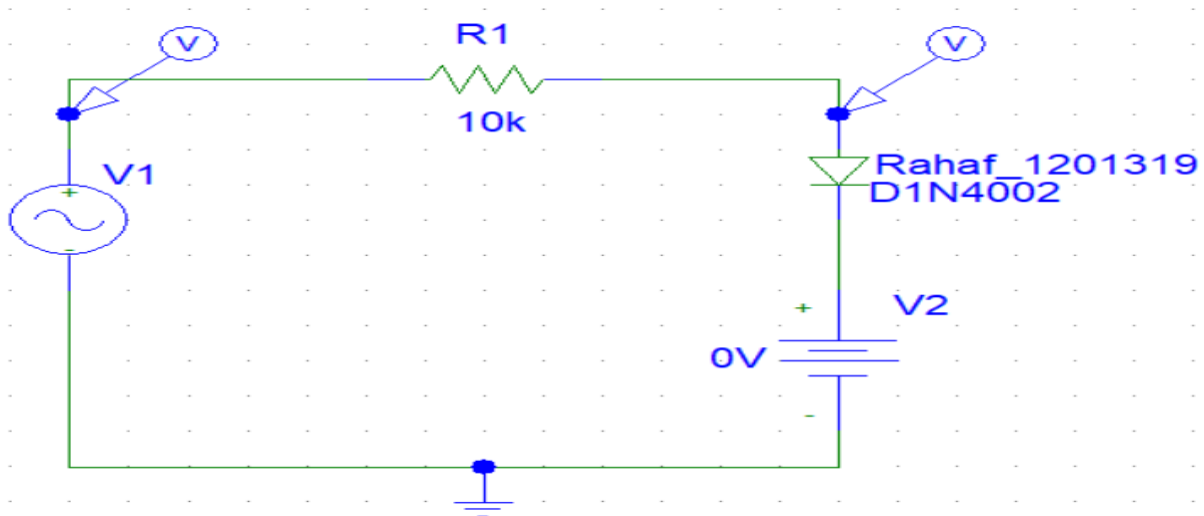


Figure 3.1.1: Clipping circuit implementation when $dc = 0v$


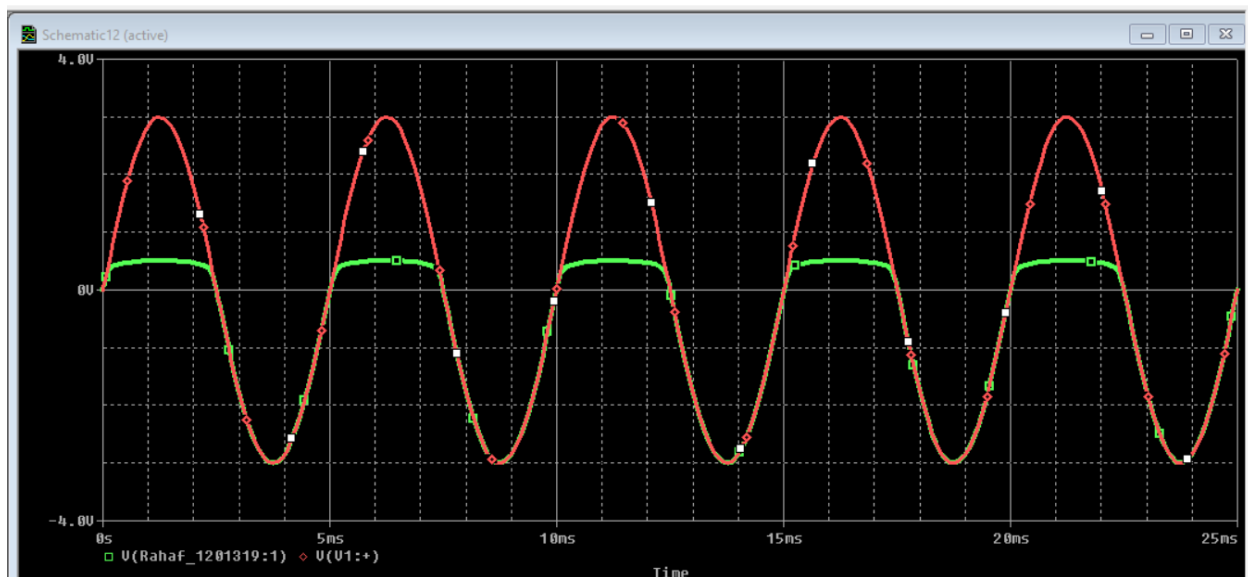



Figure 3.1.2: Clipping circuit implementation-wave form when $dc = 0v$

when $d_c = 0V$
 ① Assume diode is on

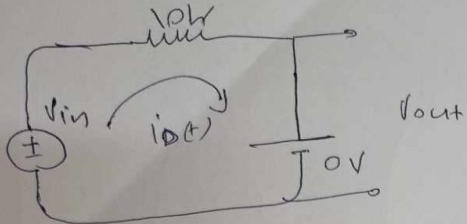


$$i_D(t) = \frac{V_{in}}{10k} > 0 \rightarrow V_{in} > 0 \rightarrow V_{out} = 0V$$

② diode is off when $V_{in} < 0$

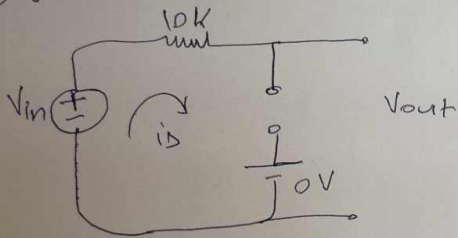

$$V_{out} = V_{in}$$

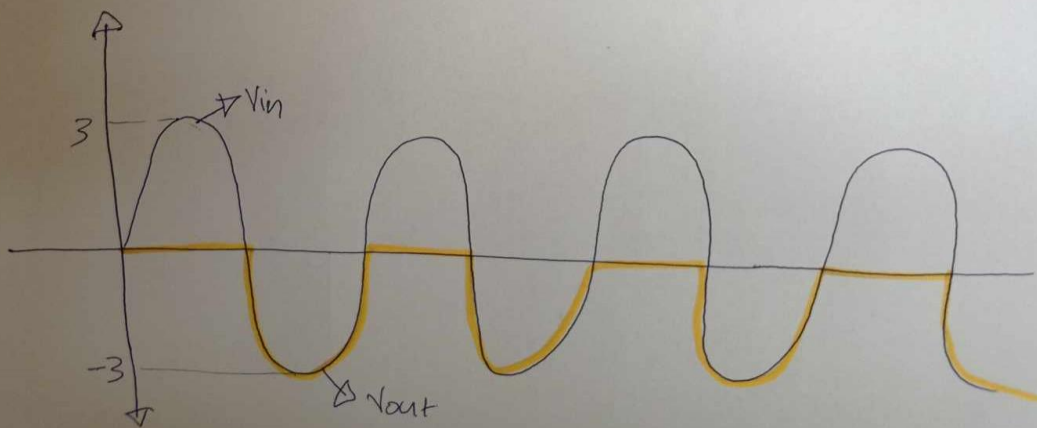

When $dc=1.5$

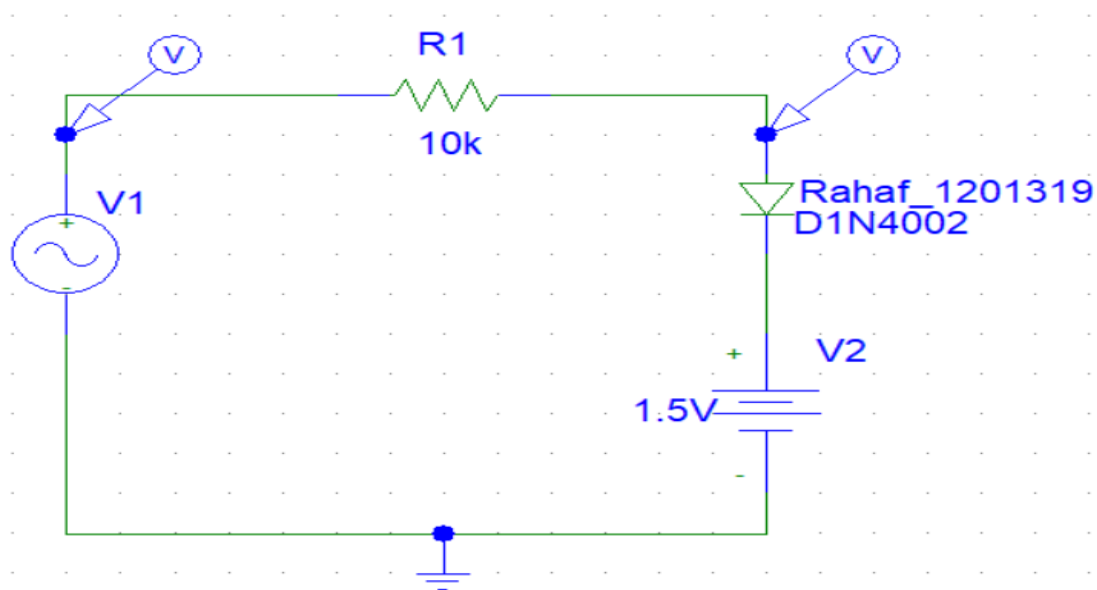


Figure 3.1.3: Clipping circuit implementation when $dc = 1.5v$


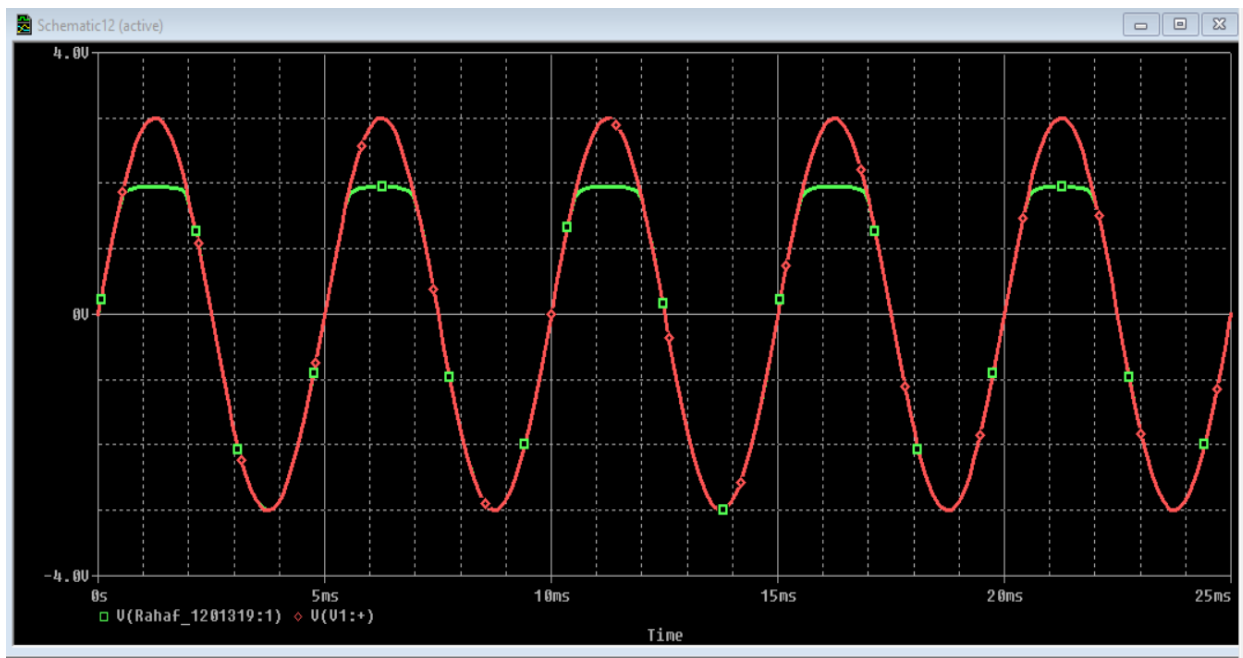


Figure 3.1.4: Clipping circuit implementation -wave form when $dc = 1.5v$

when $d_c = 1.5V$

① assume diode is ON


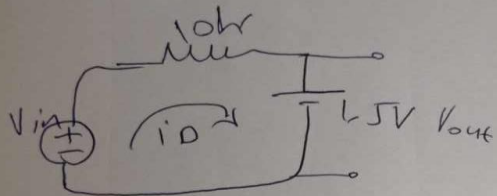


$$-V_{in} + i_D 10k + 1.5V = 0$$

$$i_D = \frac{V_{in} - 1.5}{10k} > 0 \Rightarrow V_{in} > 1.5V$$

$$V_{out} = 1.5$$

② diode is off when $V_{in} < 1.5V$

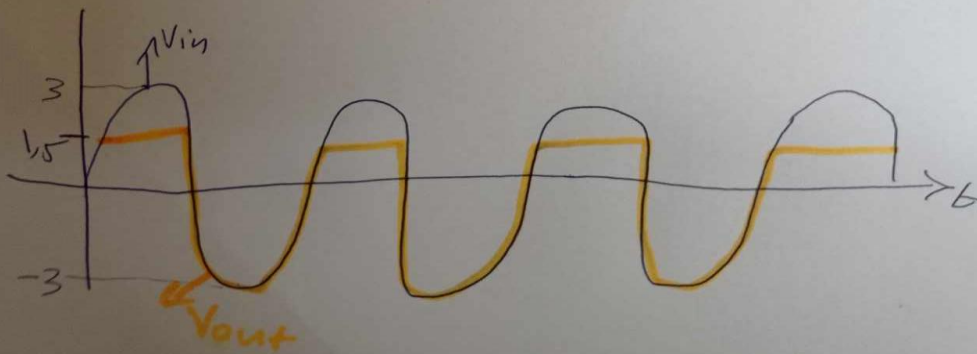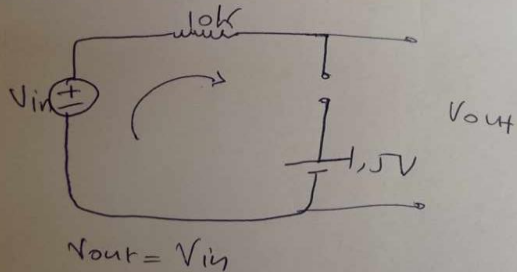

When $dc=4v$

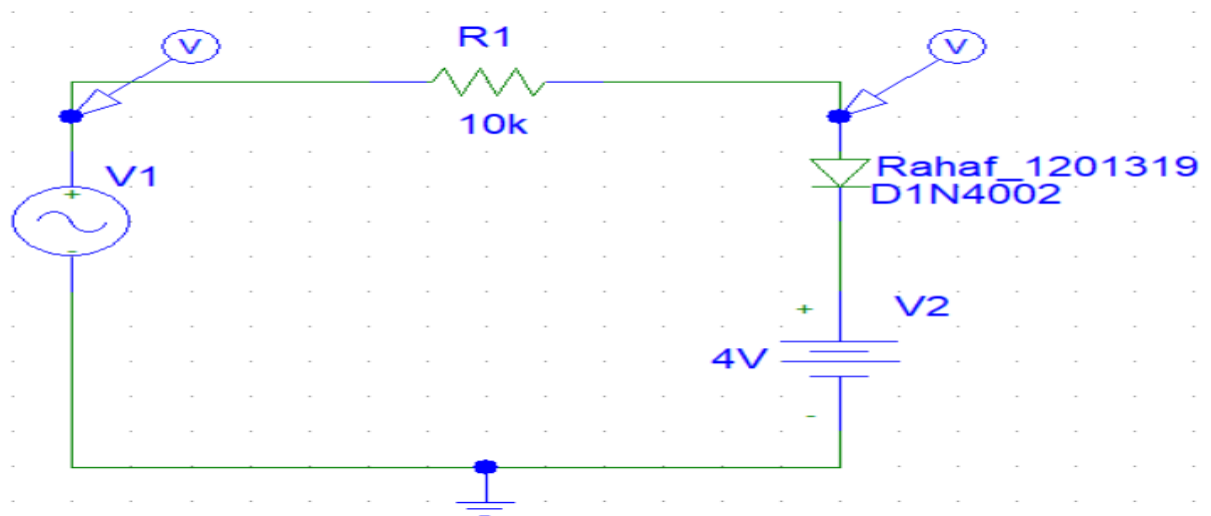


Figure 3.1.5: Clipping circuit implementation when $dc = 4v$


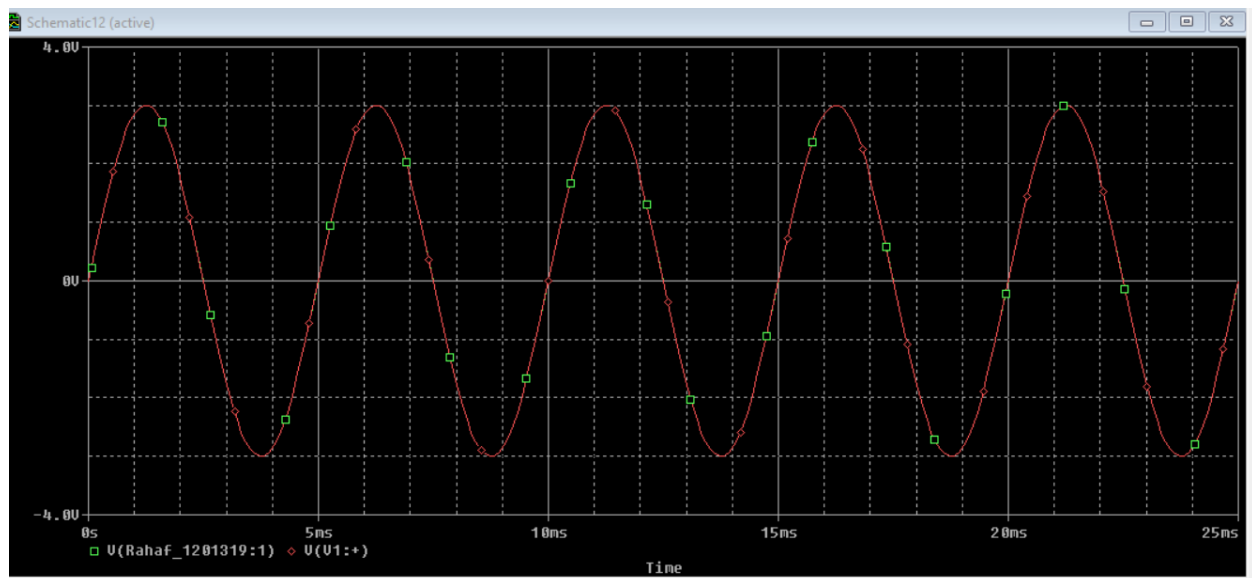


Figure 3.1.6: Clipping circuit implementation -wave form when $dc = 4v$

When $d_c = 4V$
 Assume diode is on

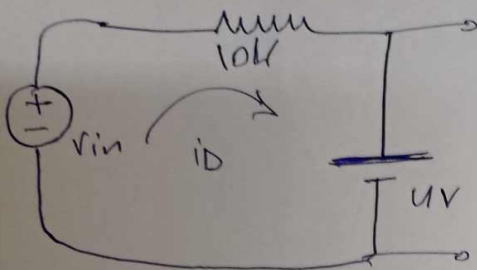


$$-v_{in} + i_D 10k + 4V = 0$$

$$i_D = \frac{v_{in} - 4}{10k} > 0 \quad v_{in} > 4$$

$$v_{out} = 4 \text{ volt}$$

② diode is off when $v_{in} < 4$

$$v_{out} = v_{in}$$

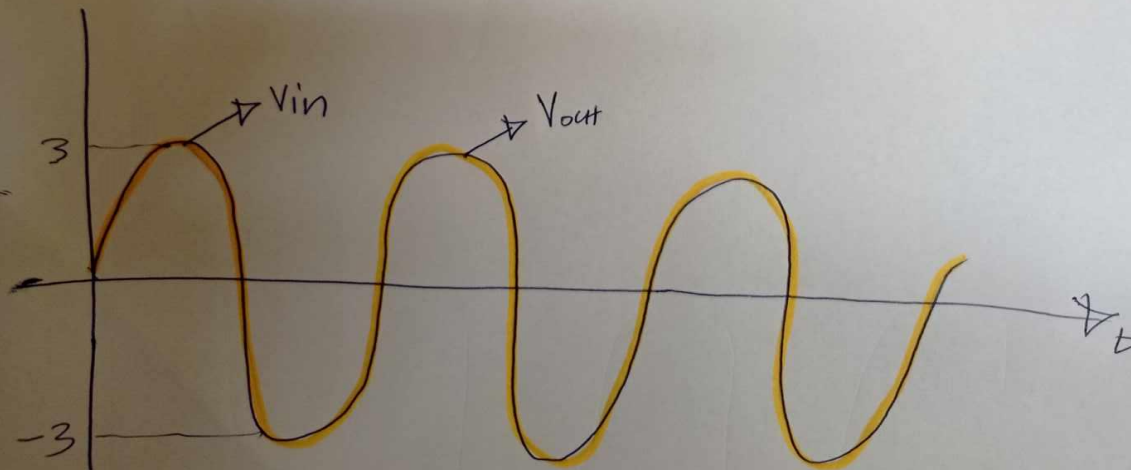

3.2. Clamping

When $dc = 0V$

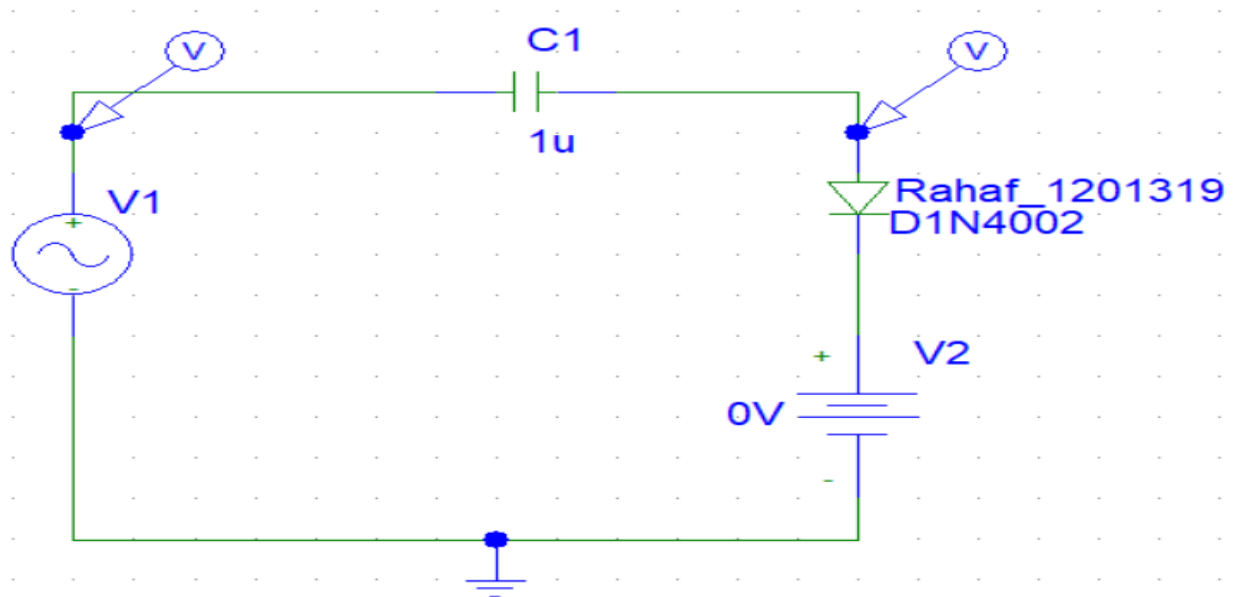


Figure 3.2.1: Clamping circuit implementation when $dc = 0V$

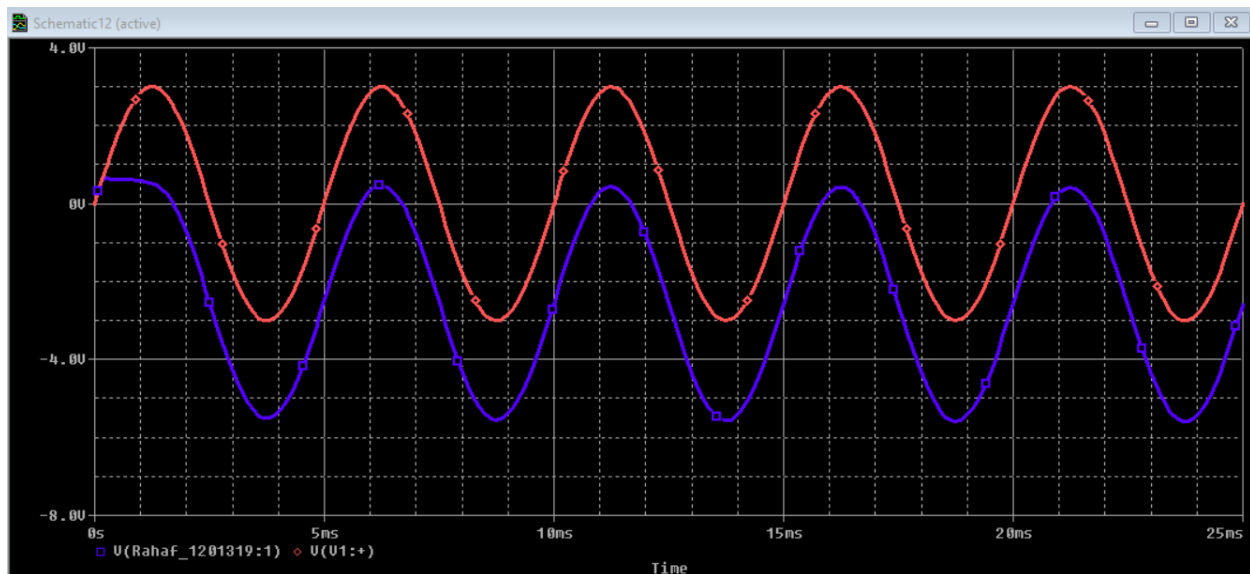


Figure 3.2.2: Clamping circuit implementation- wave form when $dc = 0V$

When $dc = 1.5v$

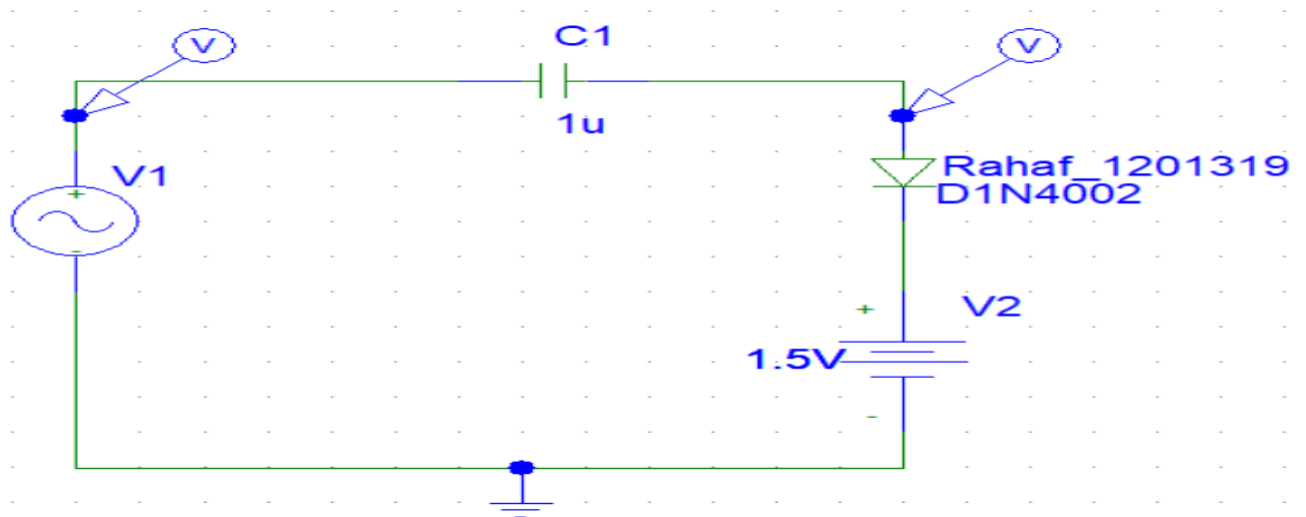


Figure 3.2.3: Clamping circuit implementation when $dc = 1.5v$


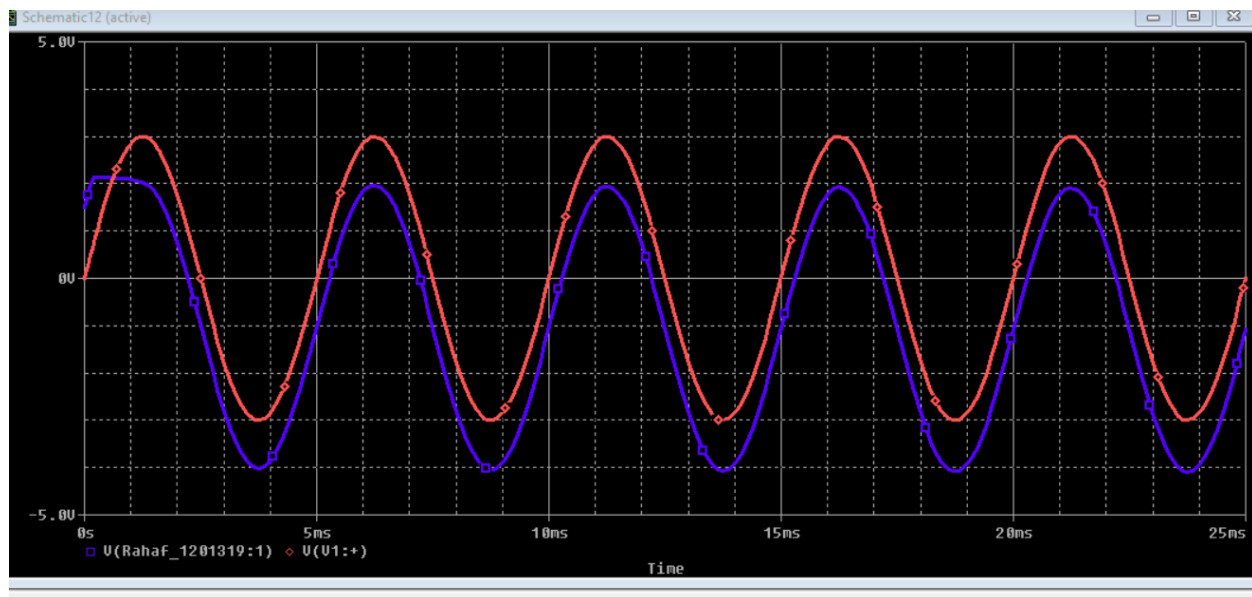
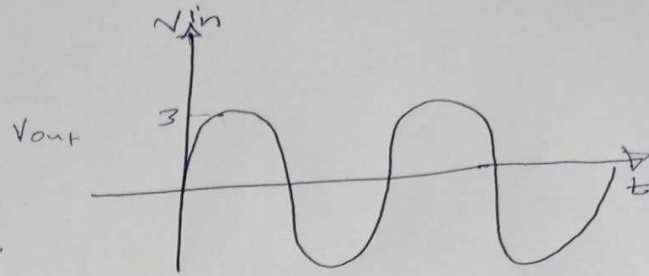


Figure 3.2.4: Clamping circuit implementation- wave form when $dc = 1.5v$

when $dc = 1,5 \text{ Volt}$

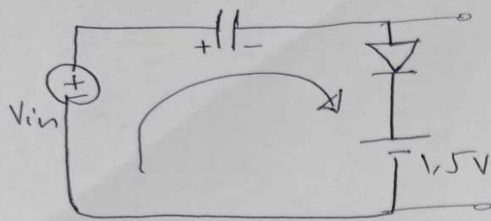

① when $v_i = 3 \text{ V}$

$$-v_{in} + V_c + 1,5 = 0$$

$$-3 + V_c + 1,5 = 0$$

$$V_c - 1,5 = 0$$

$$V_c = 1,5 \text{ V}$$

$$V_{out} = 1,5 \text{ Volt}$$


② for $v_i = -3$

$$3 + 1,5 + V_D + 1,5 = 0$$

$$V_D = -6$$

$V_D < 0$ diode is off

$$V_{out} = v_{in} - 1,5 = -4,5$$

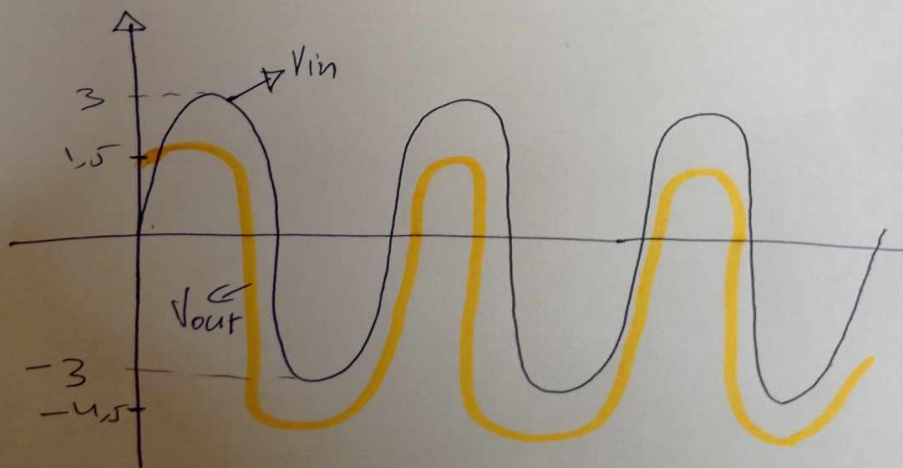

When $dc = 4v$

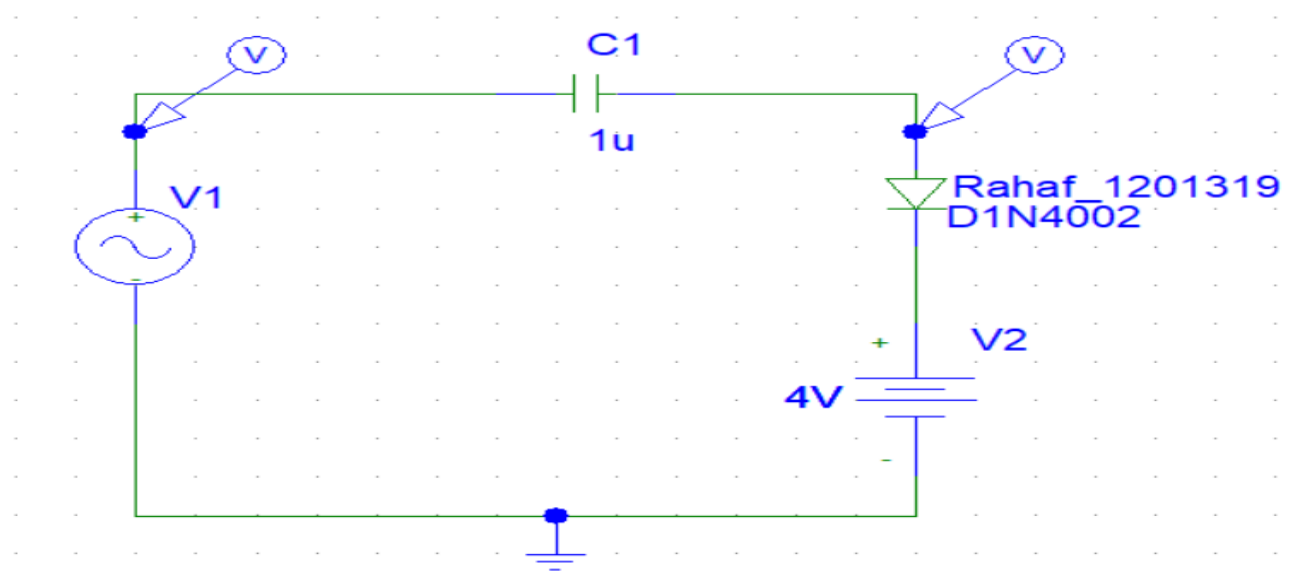


Figure 3.2.5: Clamping circuit implementation when $dc=4v$


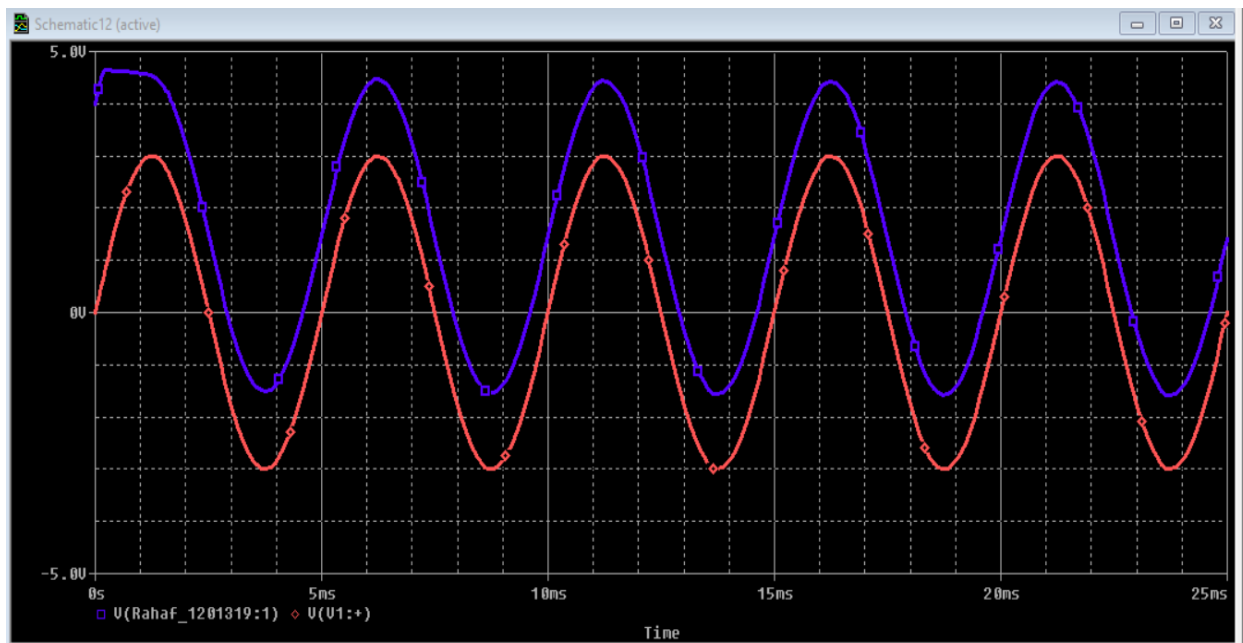
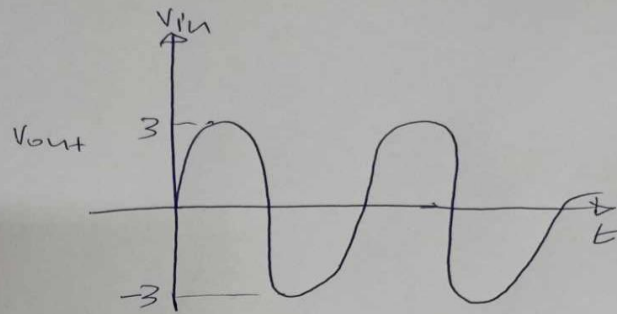


Figure 3.2.6: Clamping circuit implementation- wave form when $dc = 4v$

When $d_c = 1$ volt

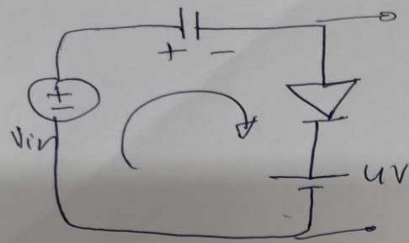

① When $V_{in} = 3V$

$$-3 + V_c + 4 = 0$$

$$V_c = -1$$

$$V_{out} = 4 \text{ Volt}$$

② When $V_p = -3$

$$3 + -1 + V_D + 4 = 0$$

$$V_D = -6$$

$V_D < 0$ diode is off

$$V_{out} = V_{in} - V_c = -3 - 1 = -2 \text{ V}$$

